

PHY132H1F Introduction to Physics II  
Class 13 – **Outline:**

- Kirchoff's Loop Law
- Charging a capacitor
- Capacitance
- Equivalent capacitance of capacitors wired in parallel and series
- Energy of a capacitor
- Dielectrics
- Electric Current



**Quick Ch. 30 reading quiz..**



**I have a capacitor whose capacitance is 1 Farad. This means**

- A. a current of 1 Amp flows through it when 1 Volt is applied across it.
- B. 1 Coulomb is separated by 1 metre.
- C. 1 Joule flows through it in 1 second.
- D. it holds 1 Coulomb when 1 Volt is applied across it.
- E. it attracts 1 Coulomb of charge with a force of 1 Newton.

**Recall from last time: Batteries and emf**

The electric potential difference between the terminals of an ideal battery is called its “emf”.

“Electric potential difference” is also known as “voltage”.

For example, a battery constructed to have an emf of 1.5V creates a 1.5 V potential difference between its positive and negative terminals.

The total potential difference of batteries in series is the sum of their individual potential differences:

$$\Delta V_{\text{series}} = \Delta V_1 + \Delta V_2 + \dots \quad (\text{batteries in series})$$

In class discussion question


**What total potential difference ( $V_B - V_A$ ) is created by these three batteries?**



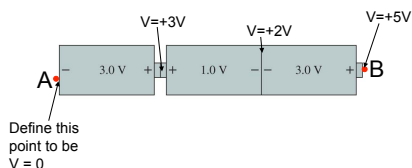- A. 1.0 V
- B. 2.0 V
- C. 5.0 V
- D. 6.0 V
- E. 7.0 V


The point:


- Electric Potential is a property of space.
- Every point has a certain value, and it must change from one side of a battery to another by its emf.
- Also, V is higher on the + side of a battery.



**As you will explore in Practicals on Friday...**

FIGURE 30.14 The geometry of the potential and the field.

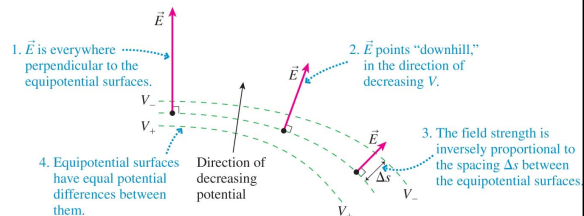

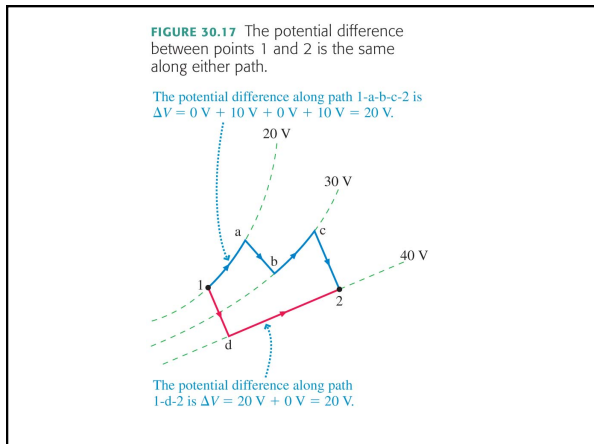

## Kirchhoff's Loop Law



For any path that starts and ends at the same point

$$\Delta V_{\text{loop}} = \sum_i (\Delta V)_i = 0$$

Stated in words, **the sum of all the potential differences encountered while moving around a loop or closed path is zero.**

This statement is known as **Kirchhoff's loop law.**

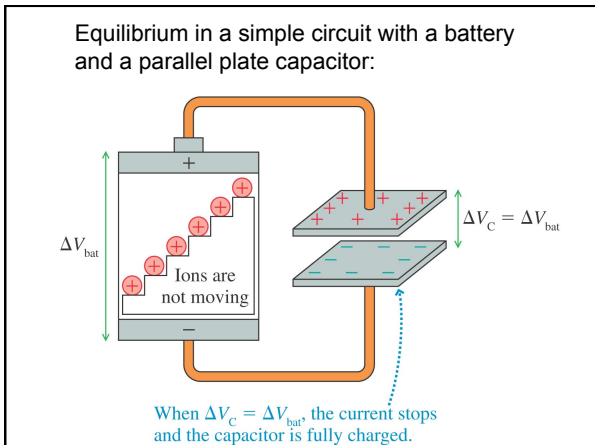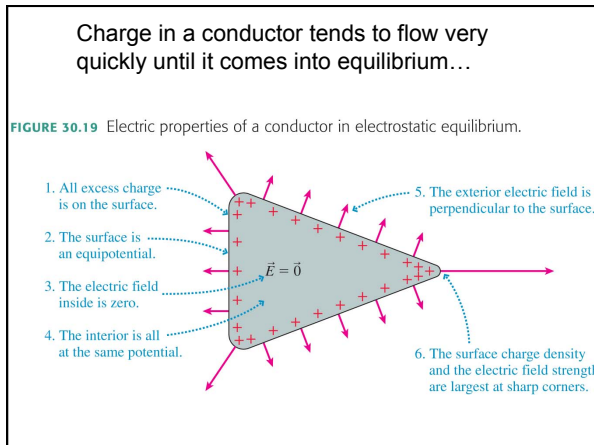(The meaning is simply that **electric potential** is a property of *space*; it doesn't matter how you got there.)



## Capacitance and Capacitors


The ratio of the charge  $Q$  to the potential difference  $\Delta V_C$  is called the **capacitance**  $C$ :



$$C \equiv \frac{Q}{\Delta V_C} = \frac{\epsilon_0 A}{d} \quad (\text{parallel-plate capacitor})$$

Capacitance is a purely *geometric* property of two electrodes because it depends only on their surface area and spacing. The SI unit of capacitance is the **farad**:

1 farad = 1 F = 1 C/V.




**The charge on the capacitor plates is directly proportional to the potential difference between the plates.**
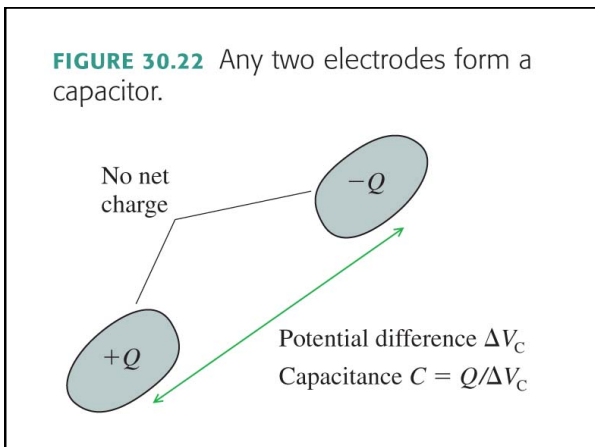
$$Q = C \Delta V_C \quad (\text{charge on a capacitor})$$

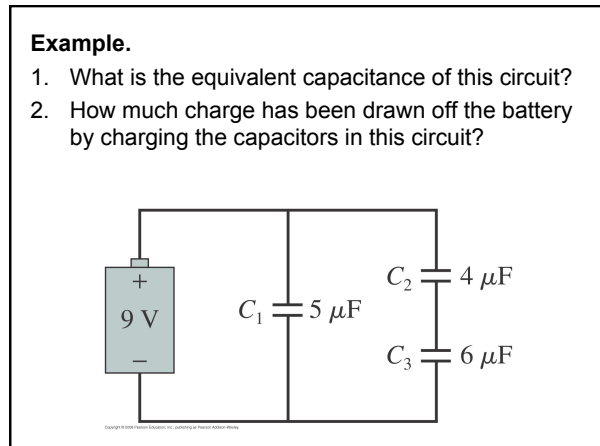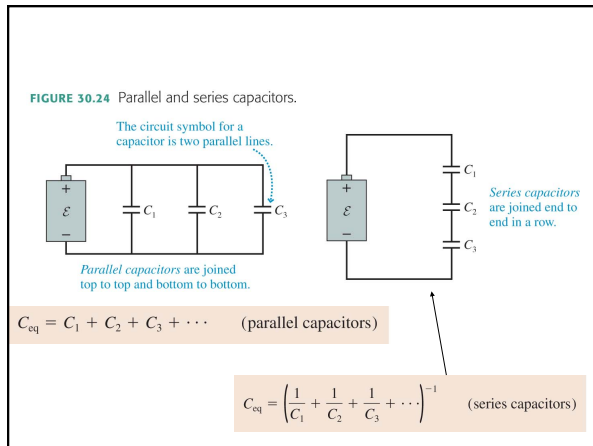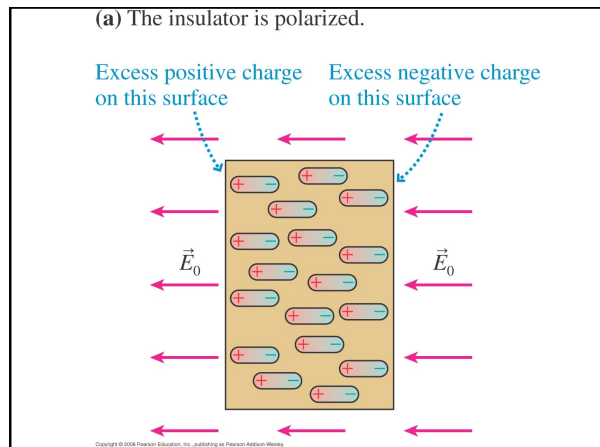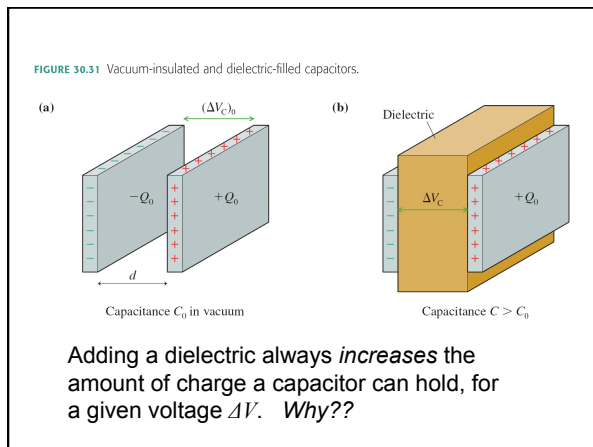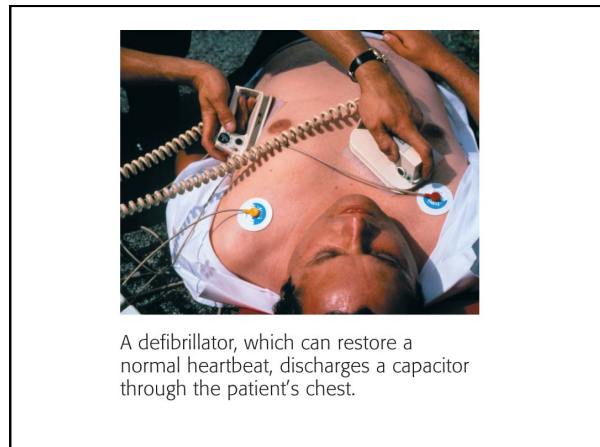
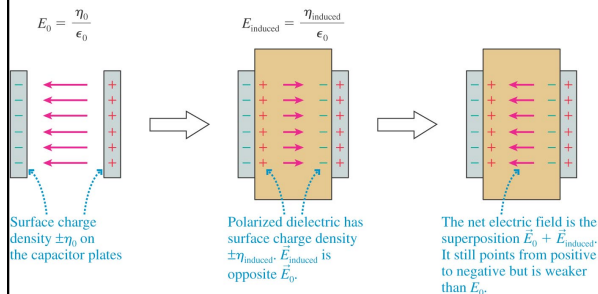


### The Energy Stored in a Capacitor

- Capacitors are important elements in electric circuits because of their ability to store energy.
- The charge on the two plates is  $\pm Q$  and this charge separation establishes a potential difference  $\Delta V = Q/C$  between the two electrodes.
- In terms of the capacitor's potential difference, the potential energy stored in a capacitor is

$$U_C = \frac{Q}{2C} = \frac{1}{2} C (\Delta V_C)^2$$


- When you add the dielectric, it reduces the electric field or voltage for the same charge.
- Therefore, it increases the amount of charge you can hold for a given voltage.



## Dielectrics

- The dielectric constant, like density or specific heat, is a property of a material.
- Easily polarized materials have larger dielectric constants than materials not easily polarized.
- Vacuum has  $\kappa = 1$  exactly.
- **Filling a capacitor with a dielectric increases the capacitance by a factor equal to the dielectric constant.**

$$C = \frac{Q}{\Delta V_C} = \frac{Q_0}{(\Delta V_C)_0/\kappa} = \kappa \frac{Q_0}{(\Delta V_C)_0} = \kappa C_0$$

## Electric Current

- Pushing on the sea of electrons with an electric field causes the entire sea of electrons to move in one direction like a gas or liquid flowing through a pipe.
- This net motion, which takes place at the **drift speed**  $v_d$ , is superimposed on top of the random thermal motions of the individual electrons.
- The **current** is proportional to the number of charge carriers *per second* that pass through a cross section of a wire or other conductor.

### In Class Discussion Question

**Why does the light in a room come on almost instantly when you flip a switch several meters away?**

- Electrons travel at the speed of light through the wire.
- The wire between the switch and the bulb is already full of electrons. Starting the flow of electrons from the switch into the wire almost immediately causes electrons to flow from the other end of the wire into the lightbulb.
- The switch sends a radio signal which is received by a receiver in the light which tells it to turn on.
- Optical fibers connect the switch with the light, so the light travels from switch to the light at the speed of light in an optical fiber.

### Before Next Class:

- Try all the suggested end-of-chapter problems for Chapter 30, posted on the Materials part of the web-site.
- Please read Chapter 31 on Current and Resistance before Monday's class. This is where we finally learn *Ohm's Law!*
- In Practicals on Friday you will be using a voltmeter to map equipotentials on special conductive paper.

*See you Monday!*