

PHY132H1F Introduction to Physics II
Class 15 – **Outline:**

- Drawing Circuit Diagrams
- Ohmic and Non-ohmic materials
- Kirchhoff's Laws
- Energy and Power in Circuits
- Buying electrical power in Ontario
- Resistors connected in Series



Quick Ch. 32 reading quiz..

What does this symbol represent in a circuit diagram?



- A. Wire
- B. Resistor
- C. Battery
- D. Capacitor
- E. Switch


Quick Ch. 32 reading quiz..

What does this symbol represent in a circuit diagram?



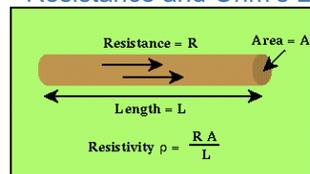- A. Wire
- B. Resistor
- C. Battery
- D. Capacitor
- E. Switch


Recall from Monday...
Resistance and Ohm's Law



The SI unit of resistance is the ohm.
1 ohm = 1 Ω = 1 V/A.
The current through a conductor is determined by the potential difference ΔV along its length:


$$I = \frac{\Delta V}{R} \quad (\text{Ohm's law})$$

Ohm's Law

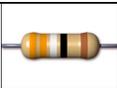

- Ohm's law is limited to those materials whose resistance R remains constant—or very nearly so—during use.
- The materials to which Ohm's law applies are called *ohmic*.
- The current through an ohmic material is directly proportional to the potential difference. Doubling the potential difference doubles the current.
- Metal and other conductors are ohmic devices.

FIGURE 31.22 Current-versus-potential-difference graphs for ohmic and nonohmic materials.

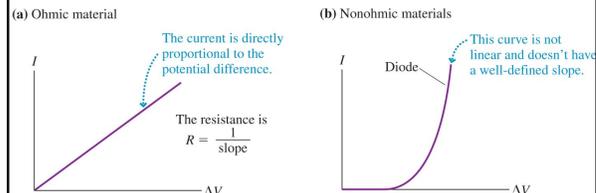

A Diode is a one-way gate for current:




LED = Light-emitting diode

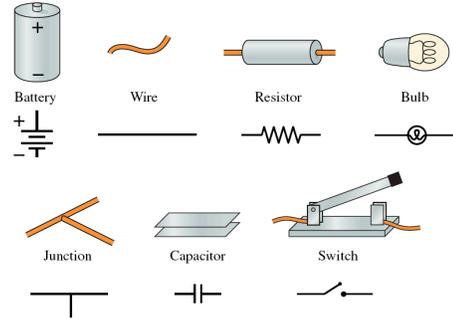- Do not create much heat – glow as electrons drop energy levels as they fall into “holes”
- High efficiency lighting

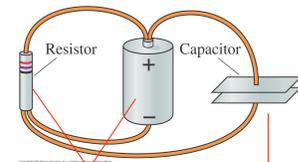


FIGURE 32.2 A library of basic symbols used for electric circuit drawings.




Circuit Diagrams

Real life:




A circuit diagram:

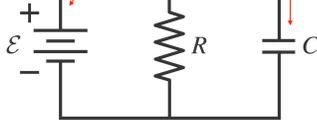


In Class Discussion Question.

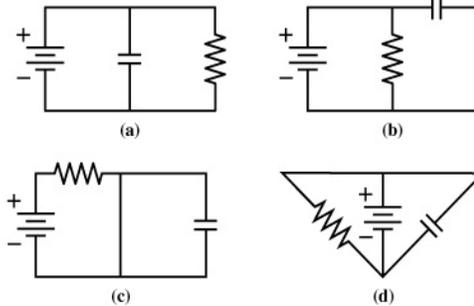Which of these diagrams represent the same circuit?



Using Kirchhoff's loop law:

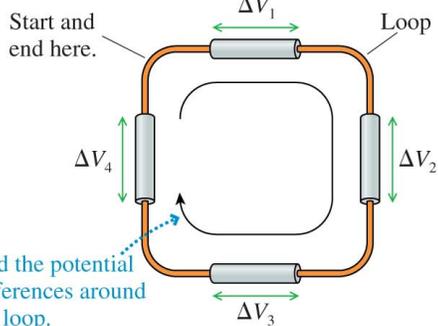


Loop law: $\Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 = 0$

In Class Discussion Question.

What is ΔV across the unspecified circuit element, in the direction of I ?

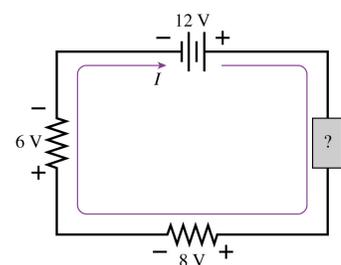- A. + 2 V
- B. - 2 V
- C. + 14 V
- D. - 14 V
- E. - 26 V



Energy and Power

- Electric Potential measures the amount of energy carried by the moving charge:
 - 1 Volt = 1 Joule per Coulomb
- Current measures the rate that charge flows:
 - 1 Amp = 1 Coulomb per second
- The change in potential, or Voltage, times the current equals the rate that energy flows, or power.
- 1 Watt = (1 J/C) × (1 C/s) = 1 Joule per second.

$$P_R = I\Delta V_R = I^2R = \frac{(\Delta V_R)^2}{R} \quad (\text{power dissipated by a resistor})$$

In Class Discussion Question.

A 60 W light bulb is plugged into an outlet that has an average voltage of 120 V. What is the average current drawn by the bulb?



- A. 0.5 A
- B. 2 A
- C. 60 A
- D. 120 A
- E. 7200 A

Energy and Power

- Ontario Hydro Power Rates:
 - on-peak rate (7-11am and 5-9pm in winter, or 11am-5pm in summer): \$0.1 per kWh
 - mid-peak rate (7-11am and 5-9pm in summer, or 11am-5pm in winter): \$0.08 per kWh
 - off-peak rate (10pm-7am all year): \$0.05 per kWh
- 1 kWh = 1000 W × 1 hour = 10³ (J/s) × 60 (m/h) × 60 (s/m)
- 1 kWh = 3.6 × 10⁶ J.
- A clothes dryer uses about 2800 Watts. If you run it for 1 hour, it consumes 2.8 kWh of energy, costing you \$0.28 at peak. (or \$0.14 if you run it at night.)




Series Resistors

- Resistors that are aligned end to end, *with no junctions between them*, are called **series resistors** or, sometimes, resistors “in series.”
- The current I is the same through all resistors placed in series.
- If we have N resistors in series, their **equivalent resistance** is

$$R_{\text{eq}} = R_1 + R_2 + \cdots + R_N \quad (\text{series resistors})$$


The behavior of the circuit will be unchanged if the N series resistors are replaced by the single resistor R_{eq} .

FIGURE 32.20 A single resistor connected to a real battery is in series with the battery's internal resistance, giving $R_{\text{eq}} = R + r$.

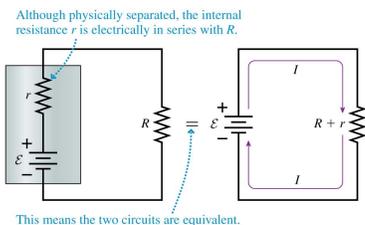

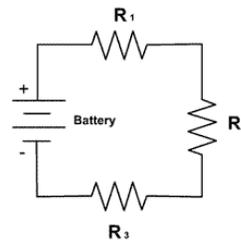Example Series circuit

A 6 Volt battery is hooked in series to 3 resistors, with $R_1 = 10 \Omega$, $R_2 = 100 \Omega$, and $R_3 = 50 \Omega$. What is the current through the circuit?



Before Next Class:

- Problem Set 6 on MasteringPhysics is due tonight by 11:59pm. It is based on Ch.31 material on capacitors.
- You will be building circuits in practicals this Friday, working on concepts from Ch. 32.
- Please finish reading Chapter 32 before next class.
- Note: U of T is closed on Monday and Tuesday, so our next class is Wed. Nov. 10

Have a great break!