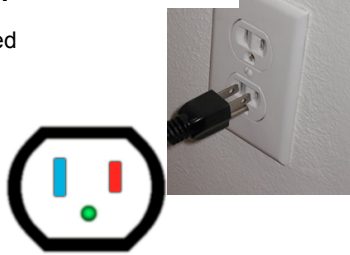


PHY132H1F Introduction to Physics II  
Class 16 – **Outline:**

- Resistors connected in Parallel
- Electric Ground
- Resistor-Capacitor (RC) Circuits



White Neutral  
Black Hot-120vac  
Green Ground

**Quick Ch. 32 reading quiz..**

In an RC circuit, “RC” stands for

- A. Right Circular
- B. Resistor Capacitor
- C. Remote Control
- D. Radio Controlled
- E. Robot Chicken

**Quick Ch. 32 reading quiz..**



The most important single property of an RC circuit is its

- A. capacitance in Farads
- B. resistance in Ohms
- C. voltage in Volts
- D. charge in Coulombs
- E. time constant in seconds

$$\tau = RC$$

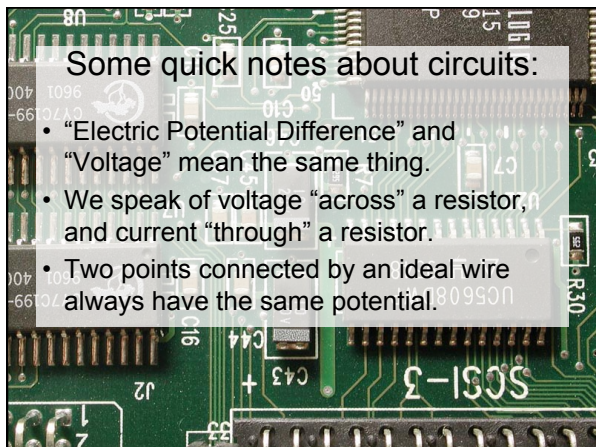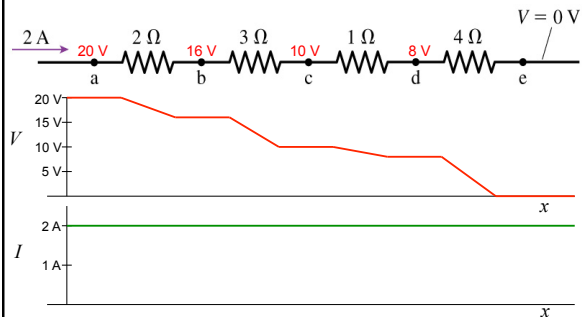**Recall discussion question from last class..**

What is the potential (current) at points a to e ?



**Some quick notes about circuits:**

- “Electric Potential Difference” and “Voltage” mean the same thing.
- We speak of voltage “across” a resistor, and current “through” a resistor.
- Two points connected by an ideal wire always have the same potential.

**Parallel Resistors**


- Resistors connected *at both ends* are called **parallel resistors** or, sometimes, resistors “in parallel.”
- The left ends of all the resistors connected in parallel are held at the same potential  $V_1$ , and the right ends are all held at the same potential  $V_2$ .
- The potential differences  $\Delta V$  are the *same* across all resistors placed in parallel.
- If we have  $N$  resistors in parallel, their **equivalent resistance** is

$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} \right)^{-1} \quad (\text{parallel resistors})$$

The behavior of the circuit will be unchanged if the  $N$  parallel resistors are replaced by the single resistor  $R_{eq}$ .

A figure from Example 32.10 in Knight.


**FIGURE 32.27** The combination is reduced to a single equivalent resistor.

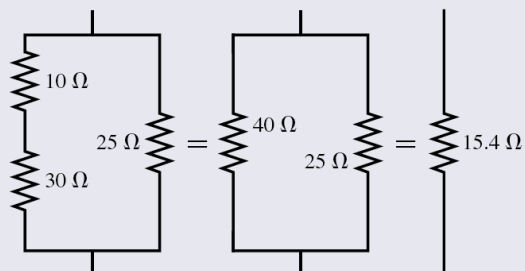

**Example**

Four identical light bulbs, each with resistance  $240 \Omega$ , are powered by a  $120 \text{ V}$  DC-Power supply, as shown.

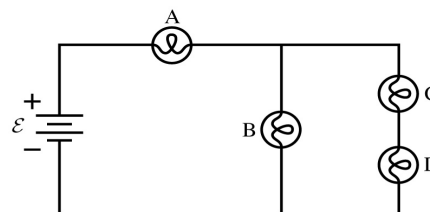1. What is the power dissipated by bulb A?
2. If bulb C is unscrewed, breaking the circuit at that point, what will be the power dissipated by bulb A?




An interesting little note, from Knight, Example 32.4:

**MODEL** Most household appliances, such as a  $100 \text{ W}$  lightbulb or a  $1500 \text{ W}$  hair dryer, have a power rating. The rating does *not* mean that these appliances *always* dissipate that much power. These appliances are intended for use at a standard household voltage of  $120 \text{ V}$ , and their rating is the power they will dissipate *if* operated with a potential difference of  $120 \text{ V}$ . Their power consumption will differ from the rating if they are operated at any other potential difference.

**Demonstration.** Two ways of wiring two different light bulbs.

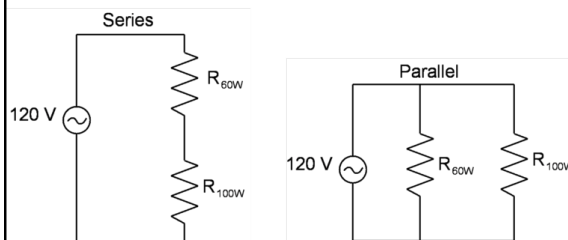
Note: A circle with a wavy line in it represents an Alternating Current (AC) power supply. It is like a battery, except the voltage flips direction 60 times per second.



**Demonstration.** In Class Discussion Question.

If the bulbs are wired in series and the  $100 \text{ W}$  bulb is unscrewed, what will happen to the  $60 \text{ W}$  bulb?

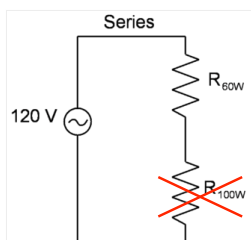
- A. It will light up.
- B. It will not light up.




**Demonstration.** In Class Discussion Question

If the bulbs are wired in parallel and the  $100 \text{ W}$  bulb is unscrewed, what will happen to the  $60 \text{ W}$  bulb?

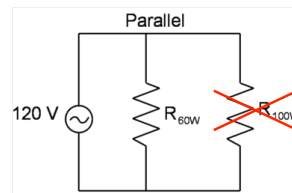
- A. It will light up.
- B. It will not light up.



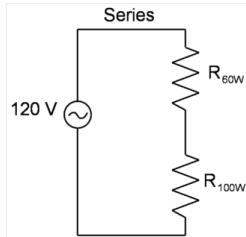
**Demonstration.** In Class Discussion Question  
 If the bulbs are wired in series, which bulb will consume more power?  
 A. The 60 W bulb.  
 B. The 100 W bulb.  
 C. both will consume the same power.



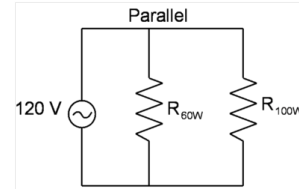**Demonstration.** In Class Discussion Question  
 If the bulbs are wired in parallel, which bulb will consume more power?  
 A. The 60 W bulb.  
 B. The 100 W bulb.  
 C. both will consume the same power.



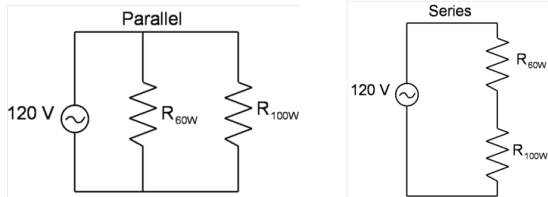**Demonstration.** The moral:  
 - The thing that is the same for resistors in parallel is voltage. Use  $P = V^2 / R$  to compare power. Higher power corresponds lower resistance.  
 - The thing that is the same for resistors in series is current. Use  $P = I^2 R$  to compare power. Higher resistance corresponds to higher power.  
 - In your house, Parallel is **always** used.



### RC Circuits

- Consider a charged capacitor, an open switch, and a resistor all hooked in series. This is an RC Circuit.
- The capacitor has charge  $Q_0$  and potential difference  $\Delta V_C = Q_0 / C$ .
- There is no current, so the potential difference across the resistor is zero.
- At  $t = 0$  the switch closes and the capacitor begins to discharge through the resistor.
- The capacitor charge as a function of time is


$$Q = Q_0 e^{-t/\tau}$$

where the time constant  $\tau$  is

$$\tau = RC$$

The figure shows the voltage as a function of time of a capacitor as it is discharged (separately) through three different resistors. Which resistor has the highest resistance?

- A.  $R_1$
- B.  $R_2$
- C.  $R_3$

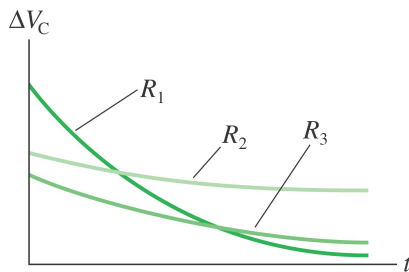

### Before Next Class:

- Problem Set 7 on MasteringPhysics is due tonight by 11:59pm. It is based on the last parts of Ch.31, and the first half of Ch. 32.
- There is also a Practice Problem Set on MasteringPhysics, based on the last half of Ch. 32, which is not for marks.
- There are NO PRACTICALS this week! Catalina and Graham may be holding extra office hours.
- I will do some review of Chs. 26, 27, and 29-32 on Monday.
- Test 2 is on Tuesday.

*See you Monday!*