

1997-1998 Physics Olympiad Preparation Program

— University of Toronto —

Problem Set 6: AC Circuits and Electronics

Due April 1, 1998

1) Misha's Mom's Medallions

Misha decided to make a big surprise for his mom's birthday: silver-plate her favourite old medallion, which had become really dark and unattractive. He took it out of the cupboard and ran to an electroplating-shop to get the job done as soon as possible. The medallion had an area $A = 57 \text{ cm}^2$ and should get $h = 50 \text{ }\mu\text{m}$ of silver. The electroplating tank used at the shop contains a solution with silver salt as electrolyte, and runs a current $I = 1.8 \text{ A}$. How much will Misha pay to the technician, if the charge is \$10/hour independent of silver used, to silverplate his mom's 1976 Olympic Bronze Medal?


Molar mass of silver $m_0 = 0.108 \text{ kg mole}^{-1}$; density of silver $d = 10.5 \times 10^3 \text{ kg m}^{-3}$; the Faraday constant $F = 9.65 \times 10^4 \text{ C mole}^{-1}$. [Lev]

2) Tesla Yes! Edison No!

An alternating current generator supplies a factory with electrical power. A cable has a resistance of $0.15 \text{ }\mu\Omega \text{ m}^{-1}$. The factory should receive 110 V and 500 A (r.m.s.) at a distance of 10 km from the generator. Find the power loss in the transmission lines and the required output voltage of the generator. Now, to get a reasonable result, let's use step-up and step-down transformers, so that the power transmission takes place at 55 kV. Calculate the power loss in this case. [Lev]

3) Analog differentiation and integration

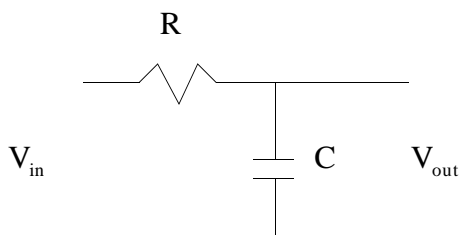a) The circuit below is known as a *differentiator*. It functions only for (periodic) input signal frequencies $\omega \ll 1/(RC)$.



Verify that this is true (find V_{out} as a function of V_{in}), and plot the output signal for an input of:

- a sine curve
- a square wave
- a triangular wave

b) Design a circuit that integrates the input wave. Prove that it works. For what frequencies is it valid? Show the output wave for:

- i) a sine curve
- ii) a square wave
- iii) a triangular wave *[Peter]*

4) What goes around, comes around

Your pal Frido runs up to you “I’m never going to need to buy electricity from Hydro again! I just got an I.C.D. — an Infinite Current Device!” Being the skeptic that you are, you ask him to explain. He shows you a strange-looking box with several sockets protruding from it. “Take a look at this. When you short out this battery and remove it from the I.C.D., current runs through the circuit forever! It’s even AC current, just like you get from a wall plug.” He shows you the ammeter that indicates a steady current of 1.0 A AC. Upon closer inspection of the interior of the box, it appears it contains only a capacitor and an inductor in series with the battery terminals. You think back to the wise words of advice you received from your physics instructor...

“...the voltage across a capacitor is proportional to the total charge on it. Current is the rate of charge flow. So the rate of voltage increase is proportional to $I(t)$.”


And inductors, what did she say about them again? Think, think!....

“....Listen up! What I am about to tell you will one day help you avoid a horrible scam that would leave you destitute. An inductor acts like a simple coil of wire which induces a magnetic field. According to Lenz’s law, it resists changes in the current running through it. Thus, the voltage across it is proportional to the rate of current change.”

- a) Now it is up to you to use these words of advice. With the battery in series with the capacitor and inductor, what is the steady-state voltage across the capacitor and inductor, and what is the current as a function of time? (This one's a no-brainer.)
- b) You short out the battery and remove it from the circuit. What is the derivative equation for current as a function of time? What equation does this remind you of? Using your experience from past problem sets, what is the current as a function of time? Think ‘Bob’!
- c) Energy seems to be leaving the capacitor and returning to it. Where is it going?
- d) Even though he does have a steady AC current like that obtainable from a wall socket, why is Frido going to be very disappointed with his I.C.D? *[James]*

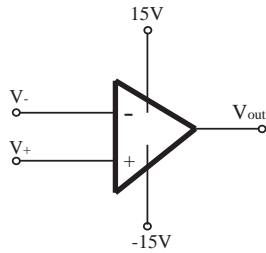5) Operation: 'Amplifier'


A standard component in an electronic circuit is the operational amplifier ('op-amp').




Operational amplifier

This device is a differential voltage amplifier: unless saturated, the output is proportional to the difference between the two voltage inputs. The bounds on V_{out} due to saturation are imposed by the power supply to the op-amp: the output voltage cannot exceed to supply voltage levels. In this case, the maximum V_{out} is 15 V and the minimum V_{out} is -15V. The magnitude of the gain is huge, and as you might not expect, is not a consideration in many applications of the op-amp.

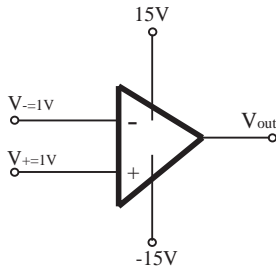
a) Let's start simple. What is V_{out} for the following op-amps?



(i)

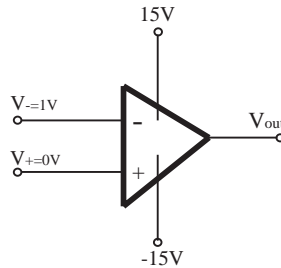

(ii)

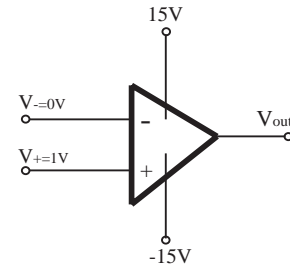


(iii)


b) One of the advantages of ideal op-amps is that they draw no current but can produce unlimited amperes (i.e., current into the $V+$ and $V-$ terminals is 0, and unlimited current can be produced on the V_{out} line). An op-amp with feedback can avoid saturation. In the circuits given at right, feedback causes $V+ \approx V-$.

What is V_{out} for these op-amps? (Remember to conserve current flow.)


[James]

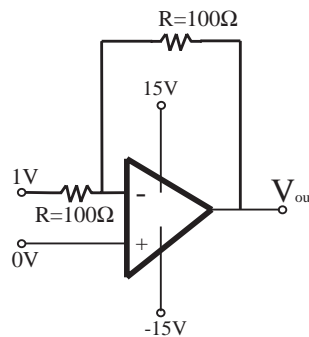


(i)

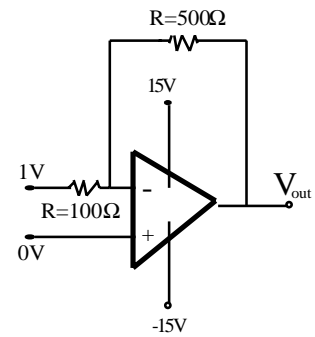

(ii)

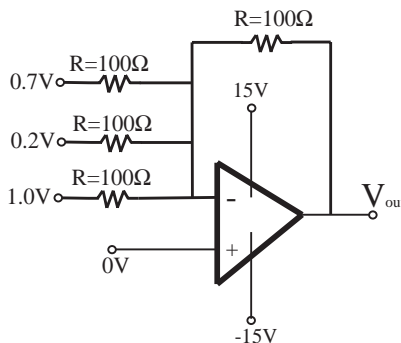


(iii)

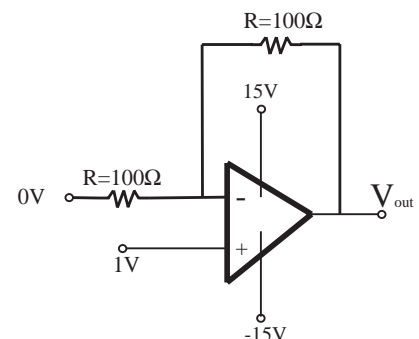

(iv)

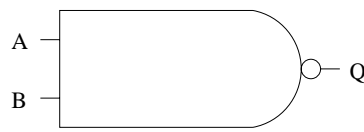6) Flip-flopping on a counter proposal


At right are the symbol and the truth table for a 'NAND gate' (NAND = 'Negated AND'; with negation being $\bar{1}=0, \bar{0}=1$; 1 = 'on', 0 = 'off'):




A	B	Q
0	0	1
1	0	1
0	1	1
1	1	0

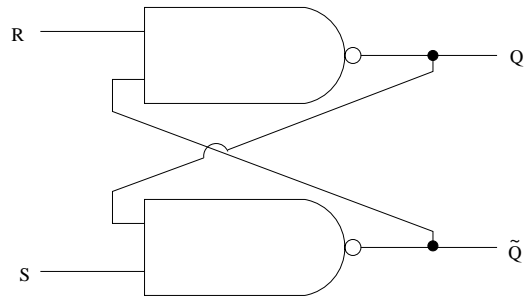a) Consider the circuit diagram below for what is called an *RS flip flop*.

If R and S are both fixed at a logical 1, what is/are the output configuration(s) for Q and \bar{Q} ? What happens if we momentarily switch R to a logical 0 and then back to a 1?



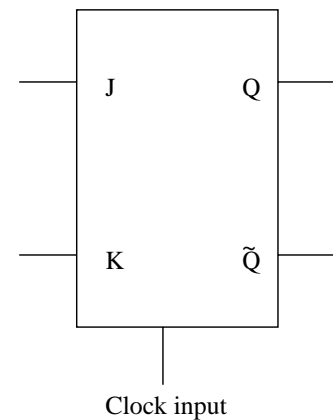b) A *JK flip flop* consists of 2 RS flip flops and a clock pulse. We show it schematically at right.



Only when there is a pulse in the clock input are the values of J and K processed by the device (a pulse is a signal that starts at zero, goes to a logical one, and then back to zero). If a clock pulse is present, the final states of the outputs, Q_f and \bar{Q}_f are dependent on J and K, and on the initial values of the output, Q_i and \bar{Q}_i . The truth table for this device (in the presence of the clock pulse) is as at left.

J	K	Q_f	\bar{Q}_f
0	0	Q_i	\bar{Q}_i
0	1	0	1
1	0	1	0
1	1	\bar{Q}_i	Q_i

Suppose now we construct the circuit shown at right.

The inputs J and K of all flip flops are kept high, and a series of pulses are entered through the clock input. Initially (with no input pulse) $Q_1 = 0$ and $\bar{Q}_1 = 1$. Make a table showing what the values at outputs A, B and C are, and of the values of each of the Q's as 1, 2, 3, and 4 pulses are input into the device. In what sense could this device be considered a digital counter? [Nipun]

