

# 1996-1997 Physics Olympiad Preparation Program

— University of Toronto —

## Solution Set 6: AC Circuits and Electronics

### 1. What's a gigawatt? Thirty of 'em??

- a) Power lost per meter, with  $P = IV$  (i.e., power and voltage are pre-set)

$$\begin{aligned} P_{\text{loss}} &= I^2 R = (P/V_{\text{rms}})^2 R = (3 \times 10^{10} \text{ W} / 110 \text{ V})^2 \cdot (1.5 \times 10^{-7} \text{ ohm} \cdot \text{m}^{-1}) \\ &= 1.1 \times 10^{10} \text{ W} \cdot \text{m}^{-1} \end{aligned}$$

- b) length for loss:  $3 \times 10^{10} \text{ W} / 1.1 \times 10^{10} \text{ W} \cdot \text{m}^{-1} = 1.1 \times 10^{10} \text{ W} \cdot \text{m} = 2.7 \text{ m}$   
(a pretty pathetic distance!)

- c) power loss by Stefan-Boltzmann law:

$$P = \sigma A T^4$$

trivial power gain from 20°C room temperature, i.e., likewise:

$$P = \sigma A (293 \text{ K})^4$$

so that net:

$$P = \sigma A [(T^4 - (293 \text{ K})^4)] \approx \sigma A T^4$$

Area of surface of 2.7 m of cable is

$$A = 2\pi r L = 2 \cdot 3.14 (0.5 \text{ m}) 2.7 \text{ m} = 8.48 \text{ m}^2$$

$$T = (P/(\sigma A))^{1/4}$$


$$= (3 \times 10^{10} \text{ W} / (8.48 \text{ m}^2 \cdot 5.670 \times 10^{-8} \text{ W m}^{-2} \text{ K}^{-4}))^{1/4}$$

$$= 15,800 \text{ K}$$


This doesn't happen, basically because of Nikolai Tesla: with AC current we can easily manage step-up transformers, so the power is delivered at much higher voltages (like 250,000 V, I recall) with smaller losses, and then stepped-down several times, the last time quite near the delivery site. As well, the total diameter of cables is far in excess of 1m.

### 2. Waffling on the issues ... the issue of waffles

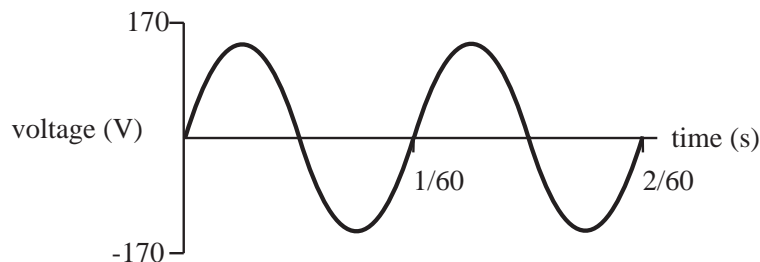
- a) Normal household voltage in about 120 V (*rms*) which corresponds to 170 V peak-to-peak



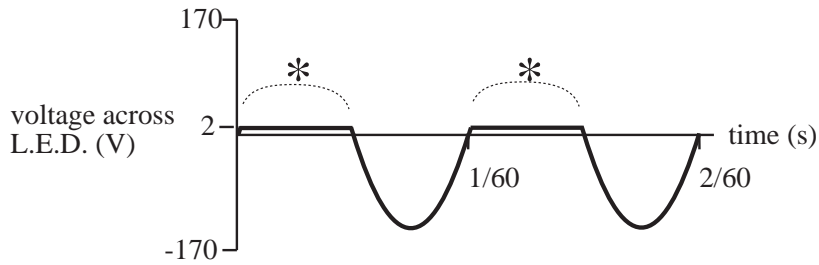b) The LED emits light only when it is forward-biased, as indicated by the asterisks in the graph below. Thus it flashes at 60 Hz.




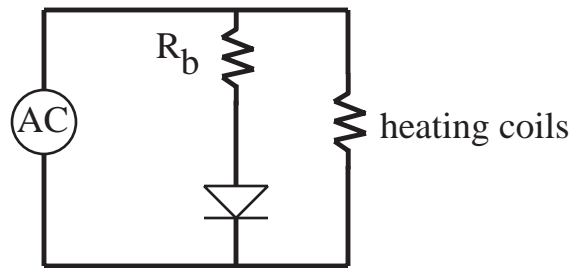c) One possible circuit is shown at right, where  $R_b$  is a large resistor. This reduces the amount of current that flows through the LED.



3.  $2B \vee (\sim 2B) \rightarrow Q!$  [... to be or not to be, that is the question!]

The circuit of this combination is

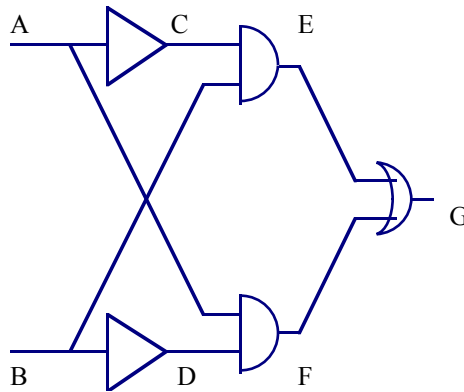


Boolean table

Input		intermediate nodes				Output
A	B	C	D	E	F	G
T	T	F	F	F	F	F
T	F	F	T	T	F	T
F	T	T	F	F	T	T
F	F	T	T	F	F	F


Clearly, this circuit is an exclusive OR gate (XOR).

4. **Connect the dots!**


a) Set voltage=4V, I=.2A

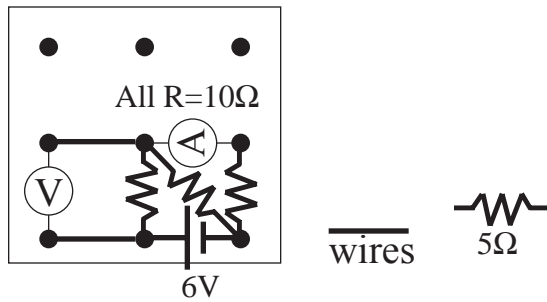

b) Set voltage=6V, I=.2A

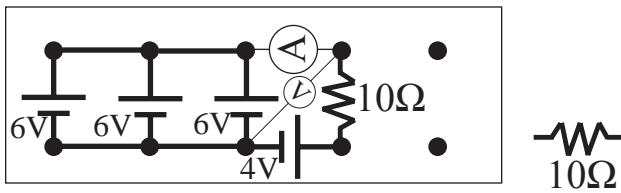

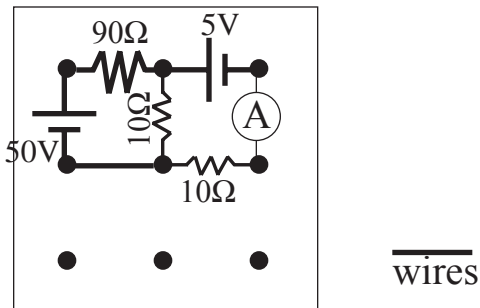c) Set current I=0A  
(note: short-circuiting batteries is baaaaaad!)



5. **Impeding one's reactance**

a) As they are seen by  $V_{IN}$ , the impedances are in series. Therefore, the total impedance is

$$Z_T = R + (i\omega C)^{-1}$$

Similarly, as seen by  $V_{OUT}$


$$Z = \frac{1}{i\omega C}$$

b) The ratio of  $V_{OUT}$  to  $V_{IN}$  is given by the ratio of the impedances.

$$\frac{V_{OUT}}{V_{IN}} = \frac{Z_T}{Z} = \frac{1}{i\omega C} \left( R + \frac{1}{i\omega C} \right)^{-1} = \frac{1}{1+i\omega CR}$$

$$\left| \frac{V_{OUT}}{V_{IN}} \right| = \left[ \frac{V_{OUT}}{V_{IN}} \times \left( \frac{V_{OUT}}{V_{IN}} \right)^* \right]^{\frac{1}{2}} = \left[ \frac{1}{1+i\omega CR} \times \frac{1}{1-i\omega CR} \right]^{\frac{1}{2}} = \left[ \frac{1}{1+\omega^2 C^2 R^2} \right]^{\frac{1}{2}}$$

$$\text{so, } |V_{OUT}| = |V_{IN}| \left[ \frac{1}{1+\omega^2 C^2 R^2} \right]^{\frac{1}{2}}$$

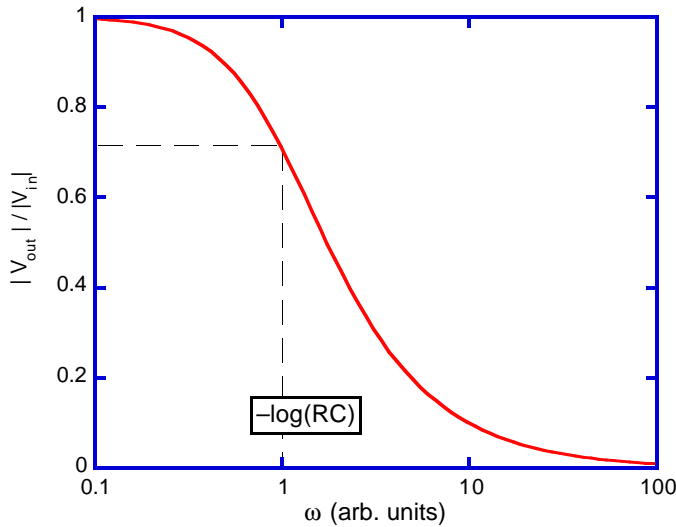

c) for  $\omega \ll \frac{1}{RC}$ , all signal is passed.

for  $\omega \gg \frac{1}{RC}$ , all voltage is dropped

So this is a filter which allows only low frequency AC signals to pass. The cutoff frequency can be changed by adjusting  $R$  and  $C$

## 6. Say 'cheese'! (... Zap !!)

a) Each element has a charge-dependent voltage associated across it:

resistor:  $\Delta V_R = IR$

capacitor:  $\Delta V_C = q/c$

inductance:  $\Delta V_L = -L \frac{dI}{dt}$

Since  $I = \frac{dq}{dt}$ , and since the potential drops around the circuit must sum to zero, we can establish a relation in terms of *charge*. Be careful about the signs:

- choose allocation of  $+q/-q$  on capacitor
- $+q$  plate is at higher potential, so sketch current direction (flow of  $+ve$  charge) consistent with dropping potential

Then the current carries charge **away** from  $+q$

so  $I = \frac{dq}{dt}$

$$q/c + L \frac{d^2q}{dt^2} + \frac{dq}{R} = 0$$

or

$$L \frac{d^2q}{dt^2} + R \frac{dq}{dt} + \frac{1}{C}q = 0 \quad \text{a 'second-order ordinary differential equation'}$$

Then

$$\Delta V_c (\text{rise}) + \Delta V_L (\text{drop}) + \Delta V_R (\text{drop}) = 0$$

$$q/c - L \frac{dI}{dt} - IR = 0$$

b) assume the form  $V(t) = V_o e^{-t/\tau}$

$$\text{so } q(t) = CV_o e^{-t/\tau}$$

and substitute into differential equation

$$\{LCV_o \left(\frac{1}{\tau}\right)^2 + RCV_o \left(-\frac{1}{\tau}\right) + V_o\} e^{-t/\tau} = 0$$

$$e^{-t/\tau} \neq 0 \text{ must mean}$$

$$LCV_o \left(\frac{1}{\tau}\right)^2 - RCV_o \left(\frac{1}{\tau}\right) + V_o = 0$$

or multiplying by  $\tau^2$  both sides

$$\tau^2 - RC\tau + LC = 0$$

then

$$\begin{aligned} \tau &= \frac{-b \pm \sqrt{b^2 - 4ac}}{2ac} && \text{quadratic formula} \\ &= \frac{+RC \pm \sqrt{R^2C^2 - 4LC}}{2} \\ &= RC \left( \frac{1 \pm \sqrt{1 - \frac{4L}{R^2C}}}{2} \right) \end{aligned}$$

The solution should be a **simple exponential**, meaning that the discriminant (root here) should be non-negative (else get imaginary numbers, which lead to cosine/sine terms — oscillations)

$$1 - \frac{4L}{R^2C} > 0 \quad \text{or} \quad 4L < R^2C$$

$$L > \frac{R^2 C}{4}$$

Then there are two solutions because of  $\pm$

$$q(t) = CV_o (a_1 e^{-t/\tau_1} + a_2 e^{-t/\tau_2})$$

$$a_1 + a_2 = 1$$

$$\tau_1 = RC \left( \frac{1 + \sqrt{1 - \frac{4L}{R^2 C}}}{2} \right)$$

$$\tau_2 = RC \left( \frac{1 - \sqrt{1 - \frac{4L}{R^2 C}}}{2} \right)$$

One of these  $\tau_1, \tau_2$  is always the longer time — the fastest decay is as  $\tau_1 \rightarrow \tau_2$ , i.e. as

$$1 - \frac{4L}{R^2 C} \rightarrow 0^+ \quad \text{i.e., from above}$$

then  $\tau_1, \tau_2 \rightarrow \frac{RC}{2}$

$$R = 1\Omega, C = 200\mu F \Rightarrow T = 100\mu s$$

c) This was rather (too?) tricky: one way to see the solution is to start with  $\tau_1, \tau_2$  and the condition

$$0 = I(t) = -\frac{dq(t)}{dt} = -CV_o \left( -a_1 \left( \frac{1}{\tau_1} \right) e^{-t/\tau_1} - a_2 \frac{1}{\tau_2} e^{-t/\tau_2} \right)$$

so  $I(t=0) = -CV_o \left( -\frac{a_1}{\tau_1} - \frac{a_2}{\tau_2} \right)$

$$a_1 \tau_2 = -a_2 \tau_1$$

but  $a_1 + a_2 = 1,$

$$\Rightarrow a_1 = \frac{\tau_1}{\tau_1 - \tau_2}$$

$$a_2 = \frac{-\tau_2}{\tau_1 - \tau_2}$$

$$I(t) = +CV_o \left( \frac{1}{\tau_1 - \tau_2} e^{-t/\tau_1} - \frac{1}{\tau_1 - \tau_2} e^{-t/\tau_2} \right)$$

$$= \frac{CV_o}{(\tau_1 - \tau_2)} (e^{-t/\tau_1} - e^{-t/\tau_2})$$

as  $L \rightarrow \frac{R^2 C}{4}$  and  $\tau_1 \rightarrow \tau_2$  this gives a  $\frac{0}{0}$  indeterminacy, which we can work with l'Hôpital's rule:

$$\begin{array}{l} \text{numerator} \\ \text{denominator} \end{array} \quad \begin{array}{l} \frac{d}{d\tau_1} (e^{-t/\tau_1} - e^{-t/\tau_2}) = e^{-t/\tau_1} \left( -t \left( -\frac{1}{\tau_1^2} \right) \right) \\ \frac{d}{d\tau_1} (\tau_1 - \tau_2) = 1 \end{array}$$

So the answer

$$I(t) = CV_o \frac{t}{\tau_2} e^{-t/\tau_2}$$

$$= \frac{CV_o}{(RC)^2} t e^{-t/RC} \quad (\text{close enough})$$

$$I(t) = \frac{V_o}{R^2 C} t e^{-\frac{t^2}{RC}}$$

$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} 200\mu\text{F} (2.5 \times 10^3 \text{ V})^2$$

$$= 625 \text{ J of energy.}$$