

# PHY405-L07


Currents and amplifiers:  
Transistors

# Logistics -- Final project

- 3 more regular labs to go, final project afterwards.
  - See the [project guidelines](#) for more information.
- Coordinate with [this OneNote page](#)
- We'll follow the steps of
  1. Conceptual design -- due Mar. 6th
    - a. Please discuss and come up with a project
  2. Technical design -- due Mar 13th
    - a. Try to use in-house components as much as possible
    - b. Part list finalized by the end of this day
    - c. Order will go out on Friday. Usually takes a week to get back
  3. Realization -- the two weeks following
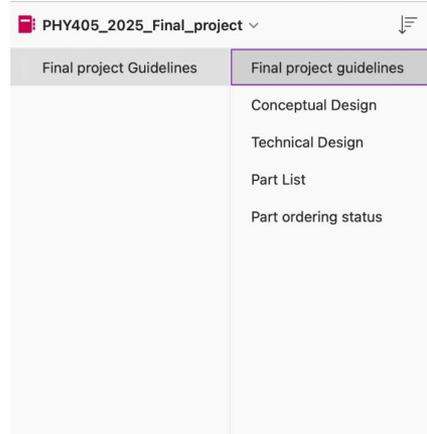
# Project coordination

- New section with your name
- Add pages of
  - Conceptual design
  - Technical design
  - Part list
  - Etc.
- I'll collect part list by the end of Mar. 13



## Final project guidelines

Tuesday, February 28, 2023 4:31 PM

<https://www.physics.utoronto.ca/apl/405/ProjectGuidelines.html>

We'll attempt to use this OneNote to coordinate the projects, especially the part lists in case new components need to be purchased.

Please create a new section with your names

Create pages like "conceptual design", "technical design", "part list", etc.

Timeline:

Mar. 6, Thursday : Conceptual design posted. Discussions and refinement is allowed in the week following.

Investigation of new parts needed, vs can we build the project with in-house components.

Mar. 13, Thursday: Technical design posted. Part list needs to be finalized by the end of the day.

Mar. 14, Friday: Purchase order sent out for parts required.

Mar. 21/24: Building final project

# Breadboard housekeeping

- From this lab, we will enforce stricter breadboard housekeeping rules


## Exercises

You will be asked for photos of some of your circuits.

- You will lose points if your hook-up wire colours do not follow a clearly specified **sensible convention**, e.g. as described in the previous lab.
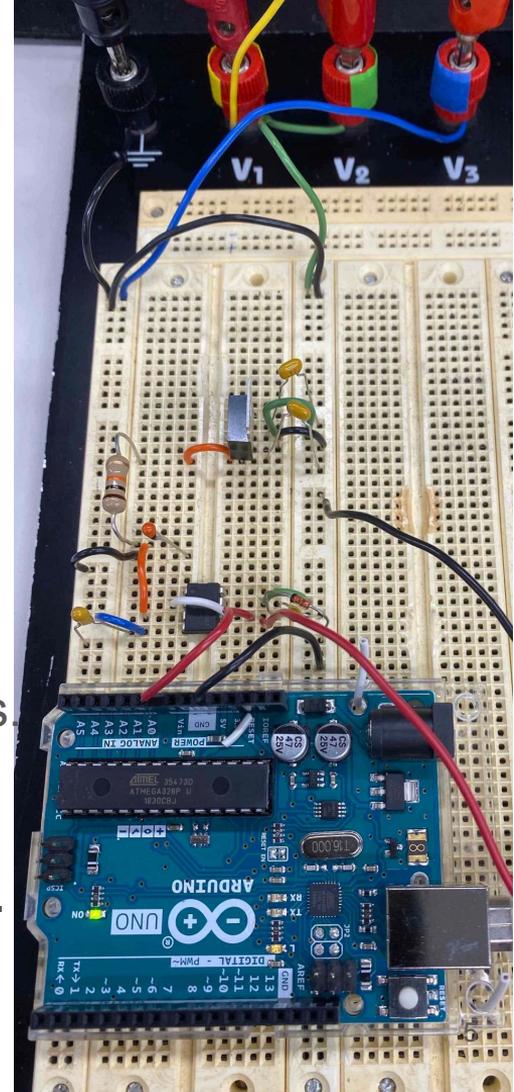
# Reminder: Breadboard Organization

- Use consistent colour wires. For example:
  - Black wires→Common.
  - Yellow wires→DC Power Supply Output 1.
  - Green wires→DC Power Supply Output 2 (V+supply)
  - Blue wires→DC Power Supply Output 3 (V-supply).
  - White or Orange wires→internal connections.
  - Red wires are Input or Output
  - Use power rails columns for V+supply and V-supply.
  - Create Common rows or columns to provide easy access
    - In general best to only have a single Common connection for any circuit.
- Some short white wires hold Arduino on the board.



# Voltage vs Current Sources

- The simplest power supplies are voltage, not current, sources
  - Batteries have voltages determined by chemical potentials
  - Electrical generators have an EMF voltage determined by

$$\varepsilon = -N \frac{d\phi_B}{dt}$$

- Output currents are determined by the total impedance


$$I = \frac{V}{Z_{load} + R_{internal}}$$

- So unless power supply internal resistance is huge - which makes it hard to provide much current - the output current will vary with the load impedance.
- If we want a controlled output current, we use active devices with feedback.
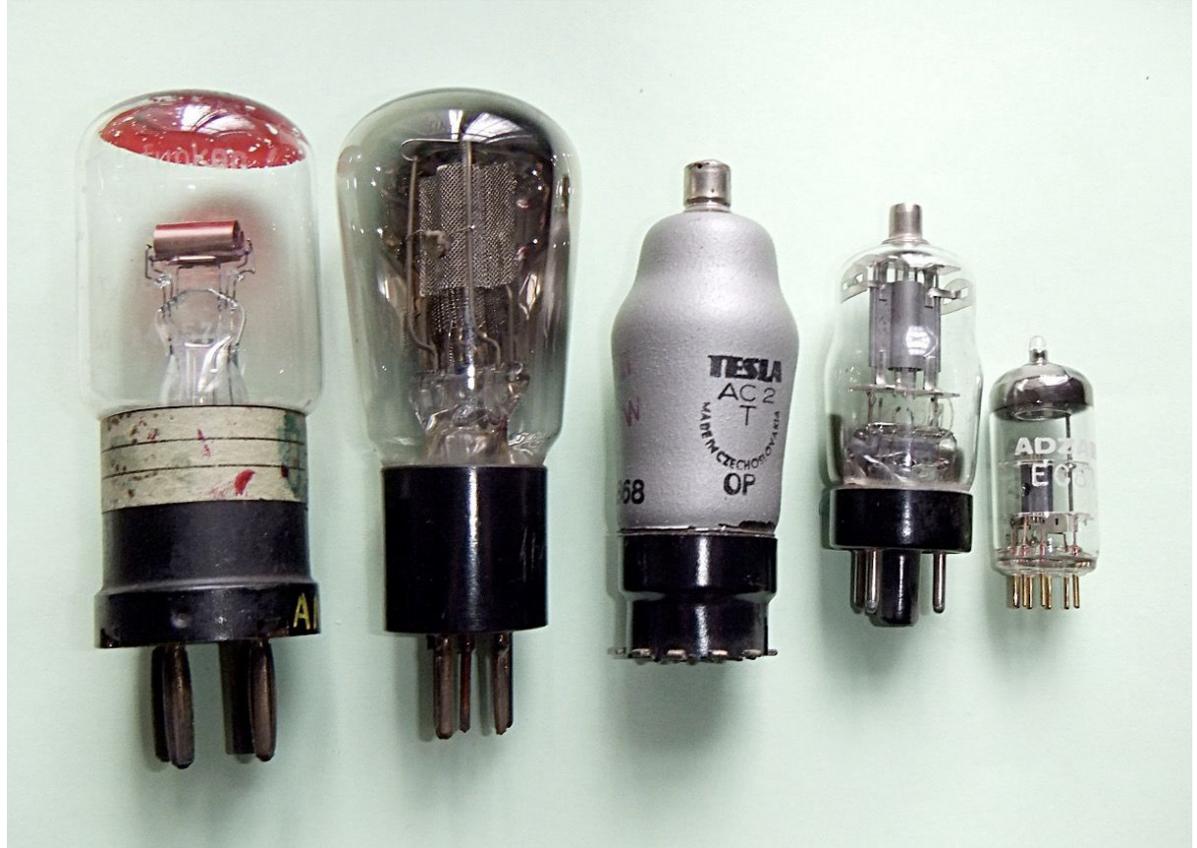
# Real Triodes


Vacuum tubes

(source: [wikipedia](https://en.wikipedia.org))


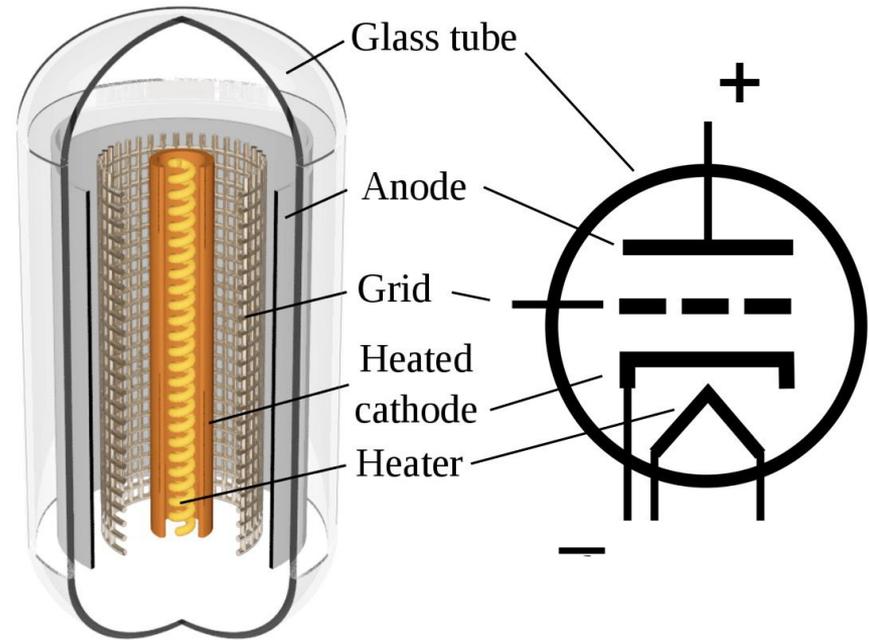
# Ideal Triodes

- Heater bake cathode to get electrons popping out
- Apply a high voltage between cathode and anode
- A voltage on the grid controls whether electrons get accelerated to anode



# Vacuum tubes are still used nowadays



Eg. Headphone audio amplifier


<https://a.co/d/9HqKmHB>

^^ A reference, not a commercial ad..

# Transistors


- The simplest semiconductor active components that can act as amplifiers or switches.

## BJT


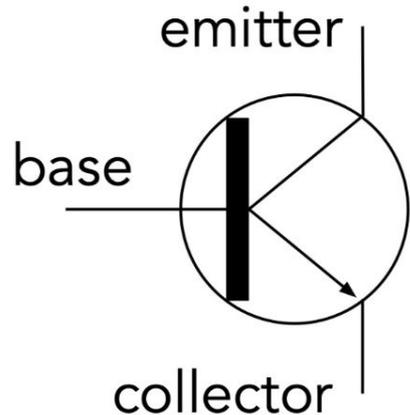


Current controlled


## MOSFET

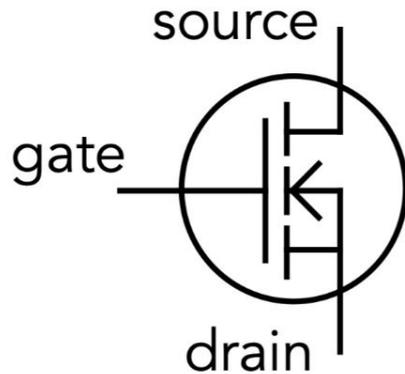

Voltage controlled

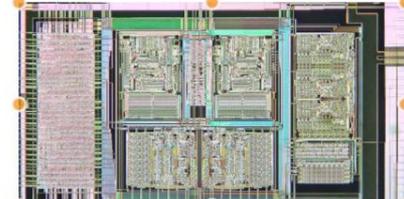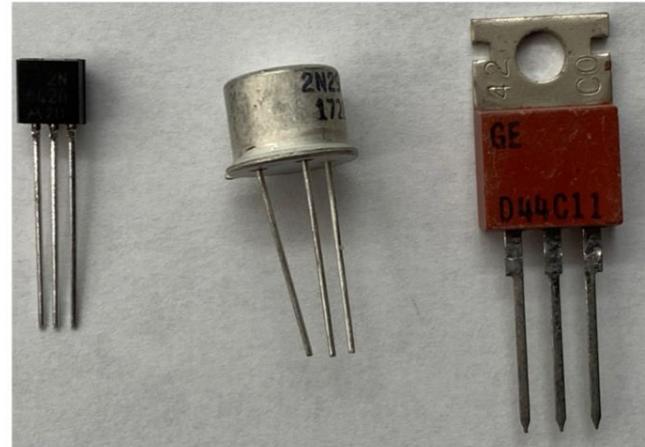


# Reminder: PN junction and Diode

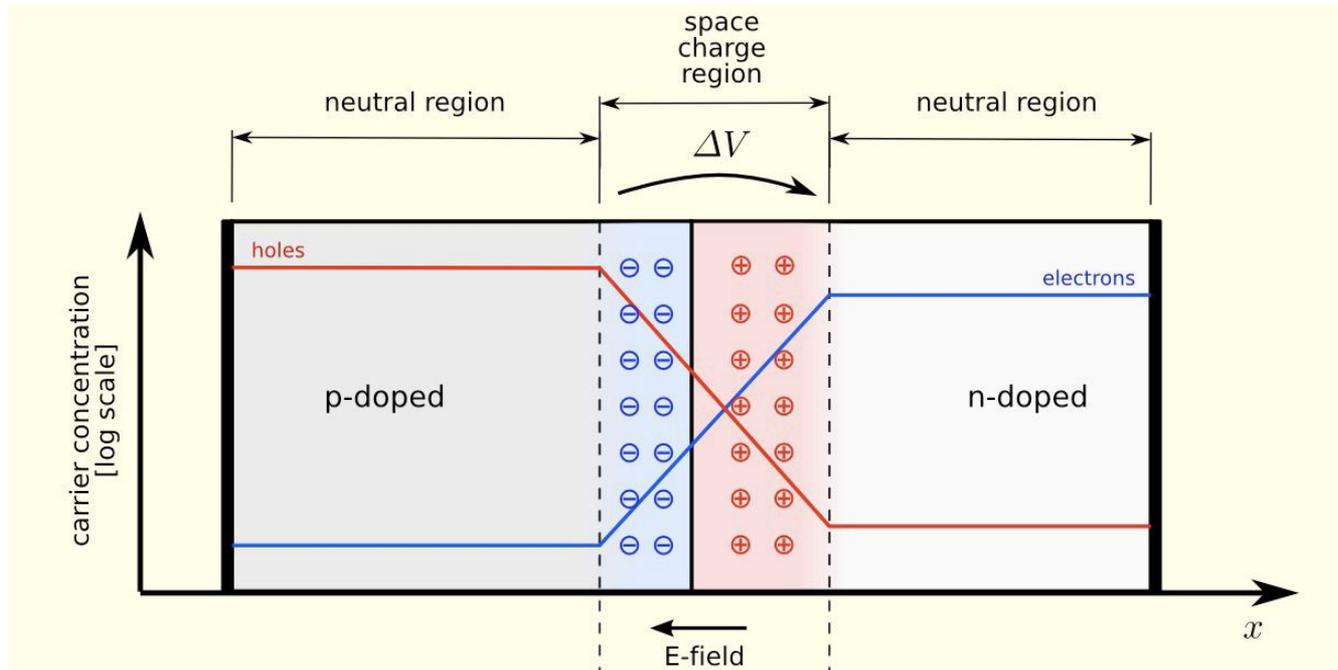


(credit: [Wikipedia](#))

# Bipolar Junction Transistor (BJT)

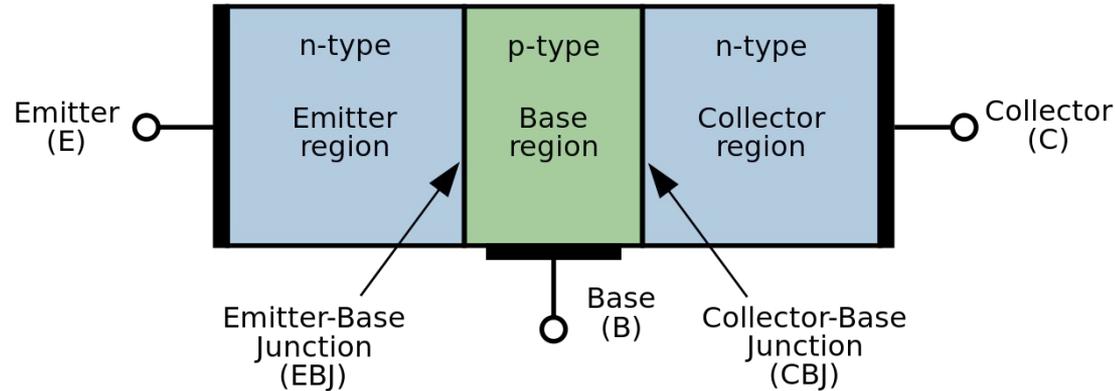


- Ideal npn Bipolar Junction Transistor (from [wikipedia](https://en.wikipedia.org/wiki/Bipolar_junction_transistor)).
  - This is not to scale.
  - The base region is usually  $\sim 0.1 \mu\text{m}$  thick, at least an order-of-magnitude less than the electron diffusion length (the average distance an electron can travel in the p-type material before recombining with a hole).
- Emitter is heavily doped, Base is lightly doped, Collector is in between.

# npn BJT

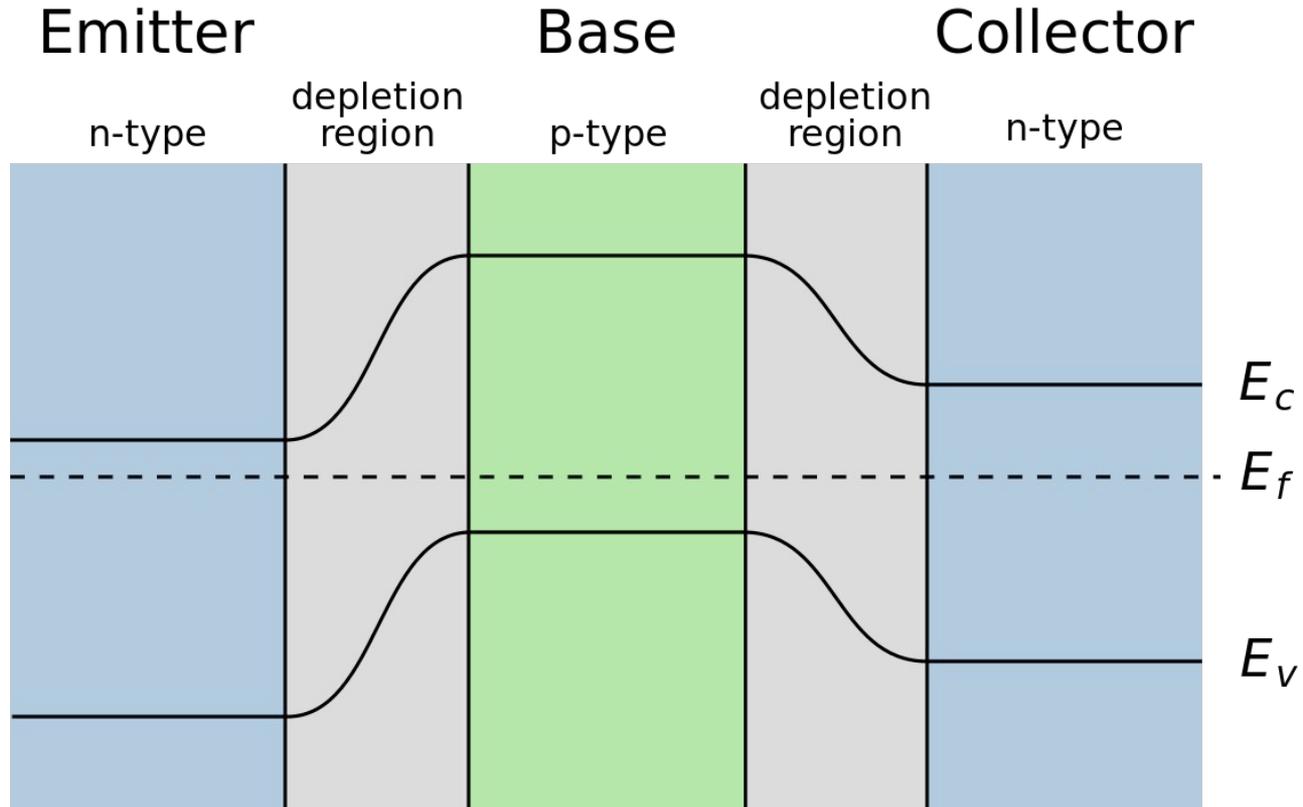




npn BJT energy bands with no applied voltage (from [wikipedia](#))

# npn BJT with voltage

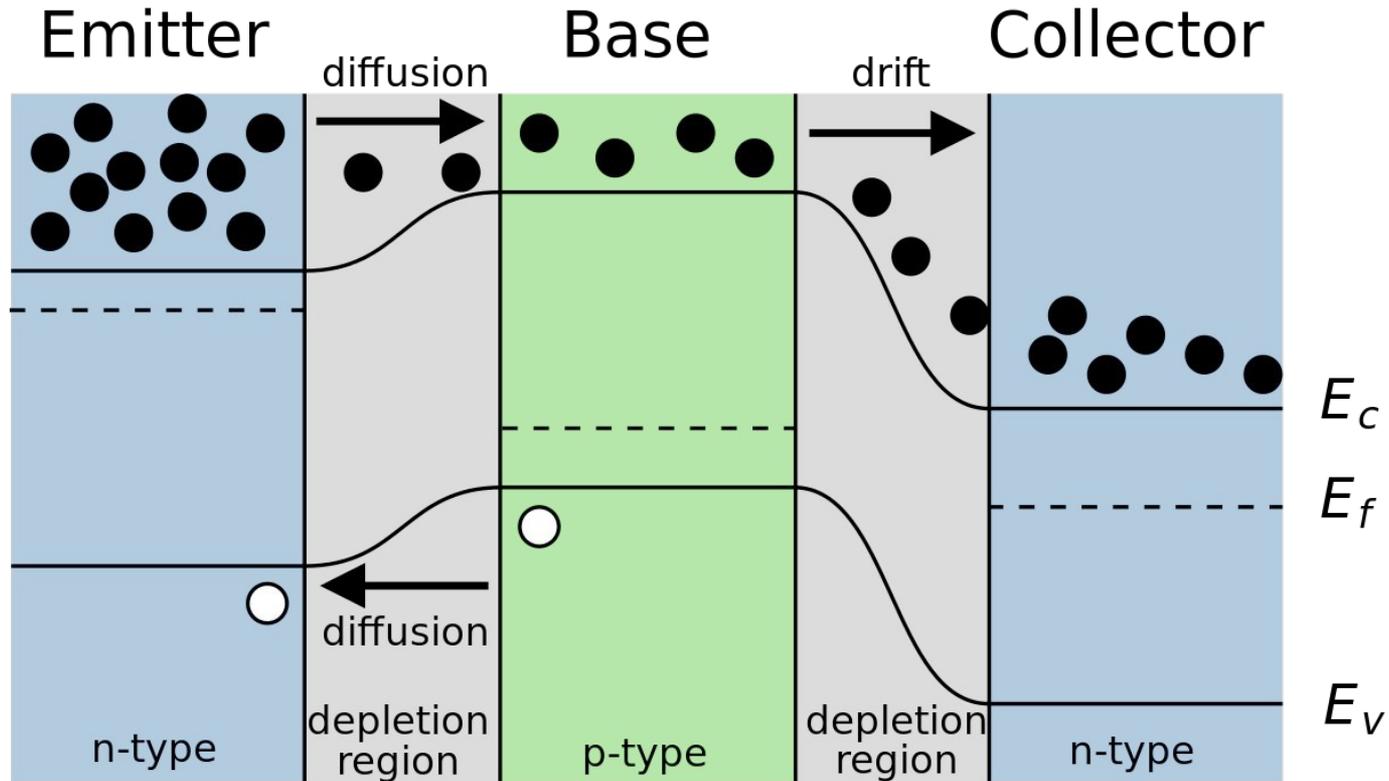

npn BJT energy bands with applied voltage (from [wikipedia](#))

# Vacuum tube vs BJT

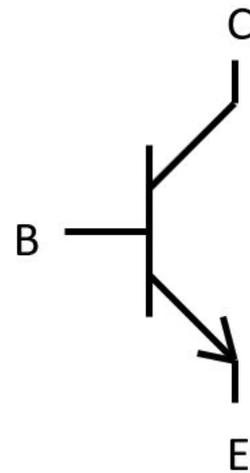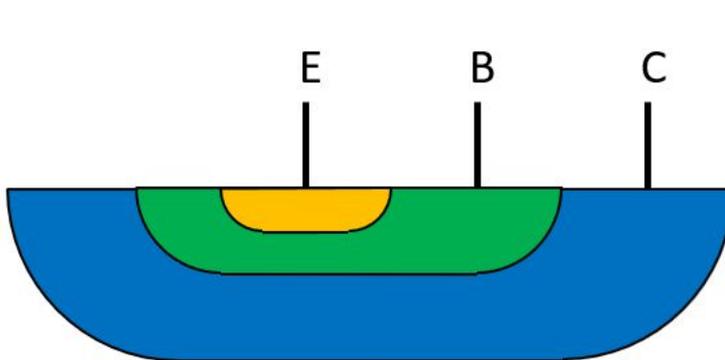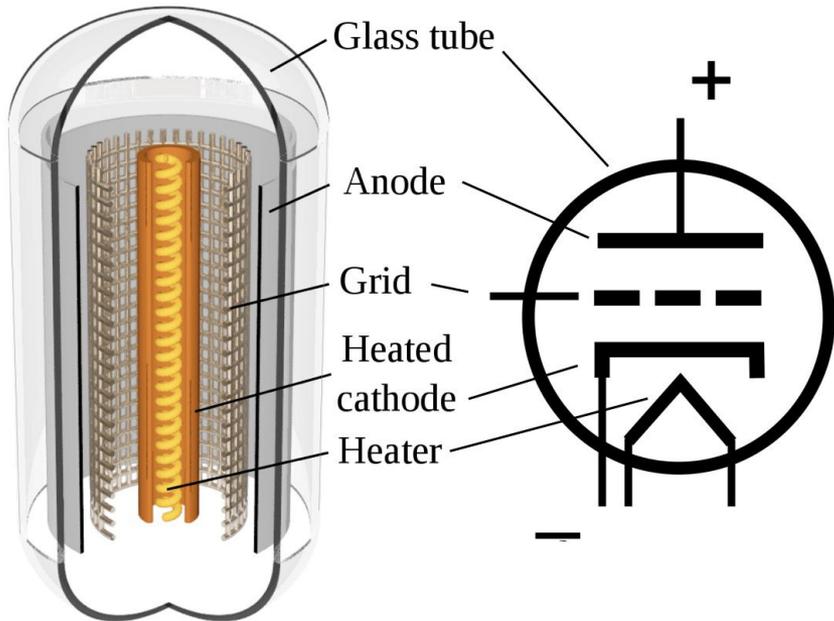



# Transistor gain

- Gain parameter for a bipolar transistor:

$$\beta = \frac{I_{\text{Collector}}}{I_{\text{Base}}}$$

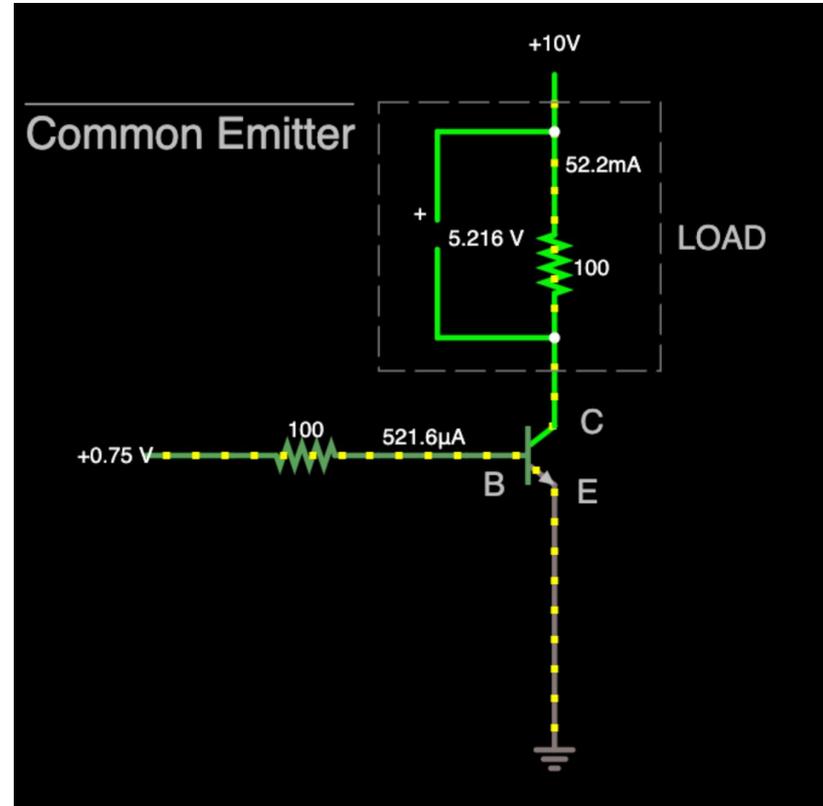- This is measured in the Common Emitter mode.
- $\beta$  is also known as the hybrid forward transfer characteristic  $h_{fe}$
- Usually  $\beta \sim 100$




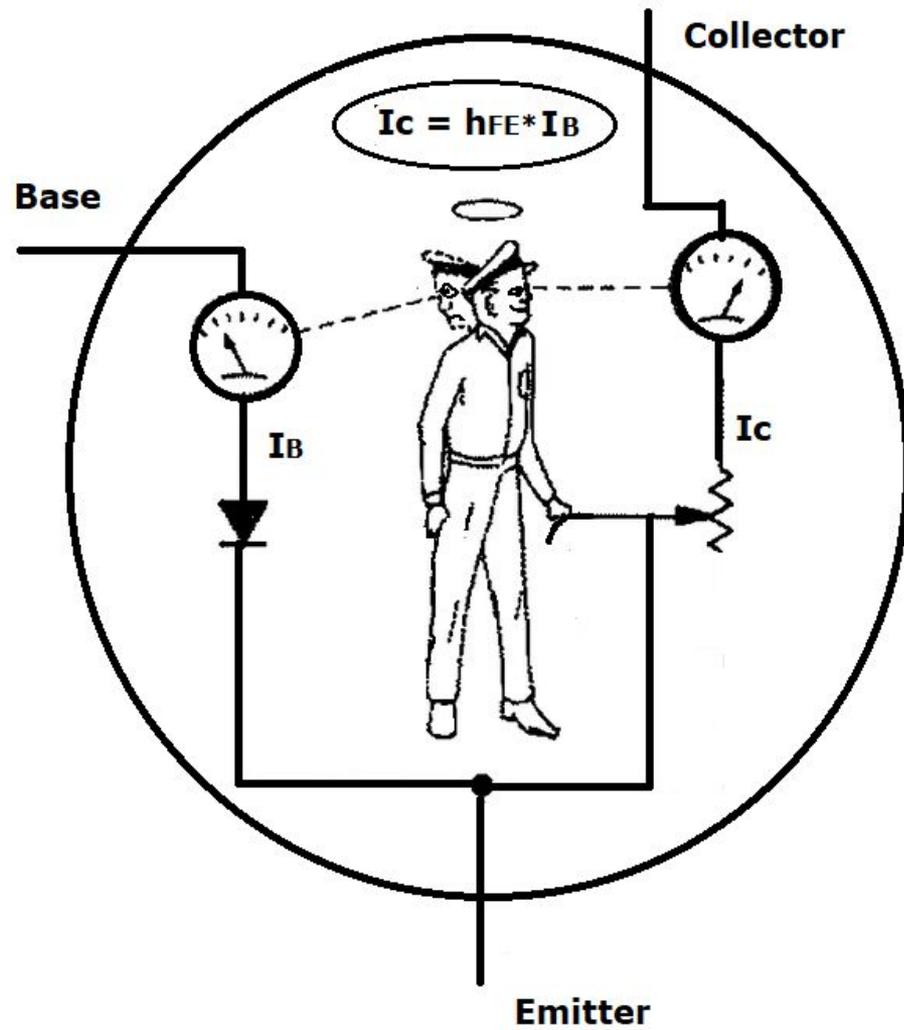


# Transistor connections

Common	Gain
<u>Base</u>	V
<u>Emitter</u>	V & I
<u>Collector</u>	I


Common Base

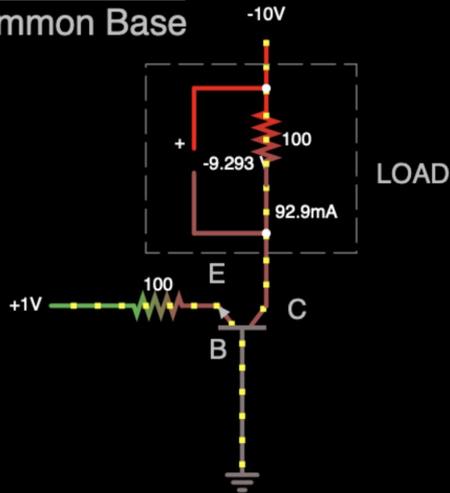


Common Emitter

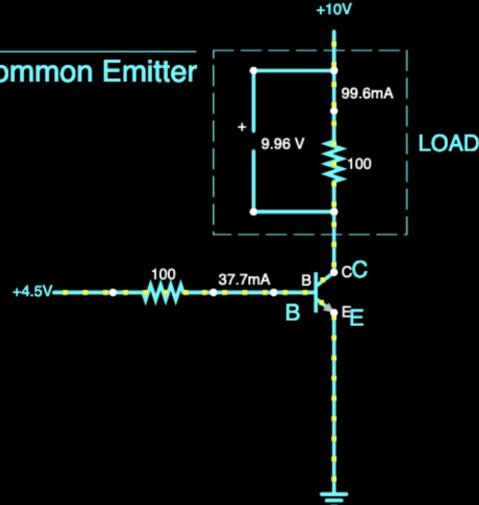

Common Collector

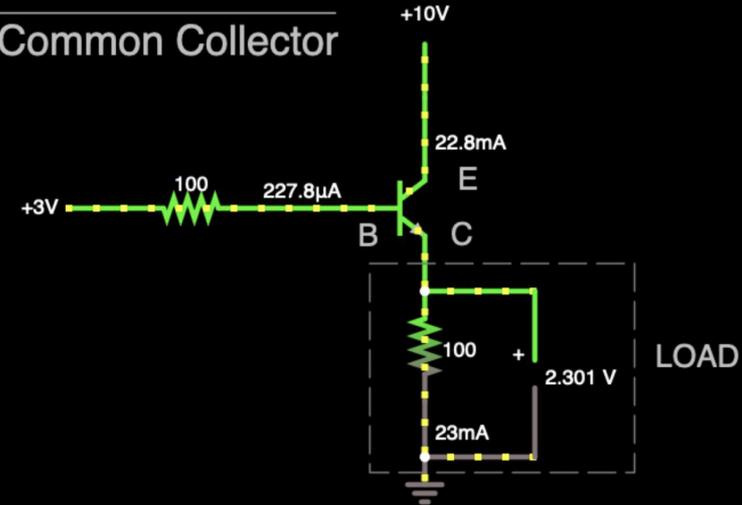


# Field Effect Transistor (FET)

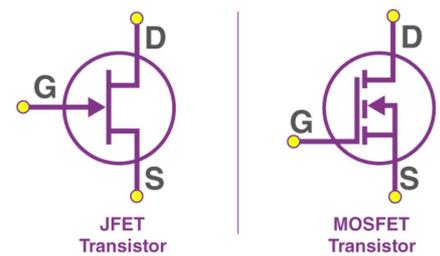

- Field Effect Transistor control currents using voltage
- The common types are
  - MOSFET (Metal Oxide Semiconductor Field-Effect Transistor)
    - typical input impedance  $\sim 10^{14}\Omega$
    - depletion and enhancement types
    - lowest power requirements, so can be more densely packed
    - also known as “Magically Obliterated, Smoke and Fire Emitting Transistor”
  - JFET (Junction Field-Effect Transistor)
    - typical input impedance  $\sim 10^9 \Omega$
    - depletion type only
    - cheaper and more robust


# Enhancement-mode MOSFET

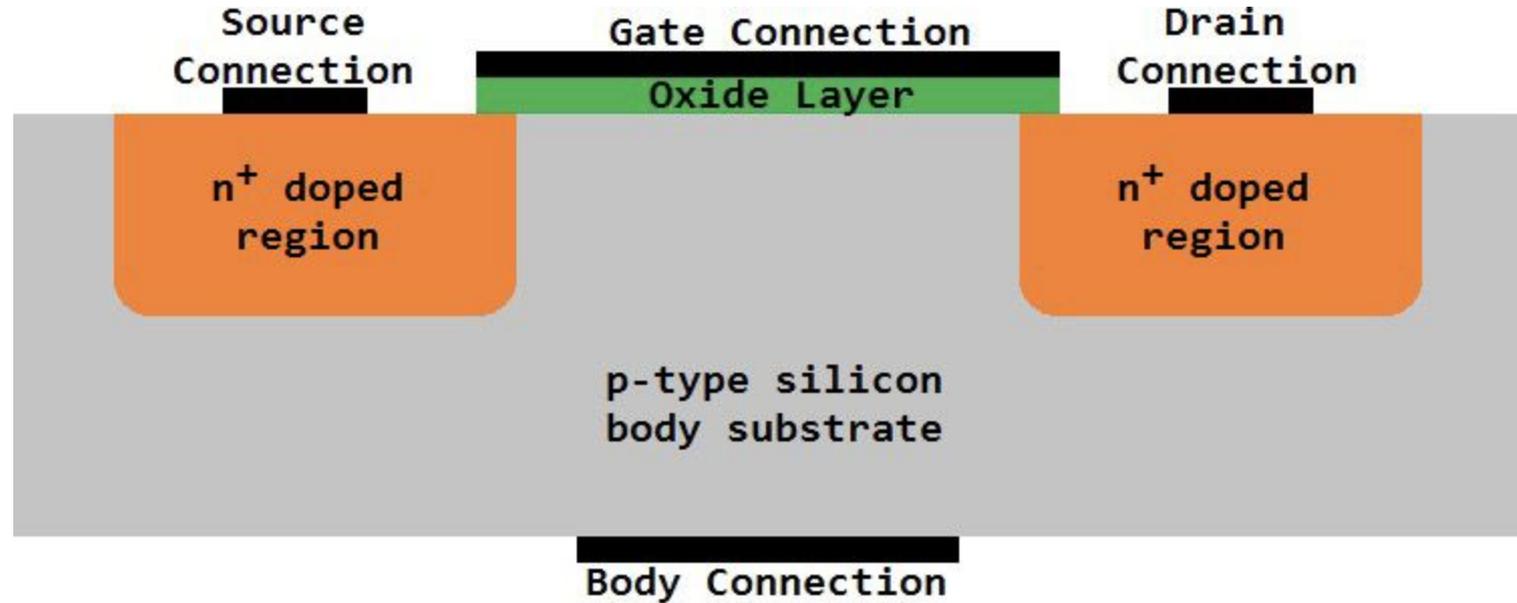


n-channel enhancement-mode MOSFET (source: [DigiKey](#)).
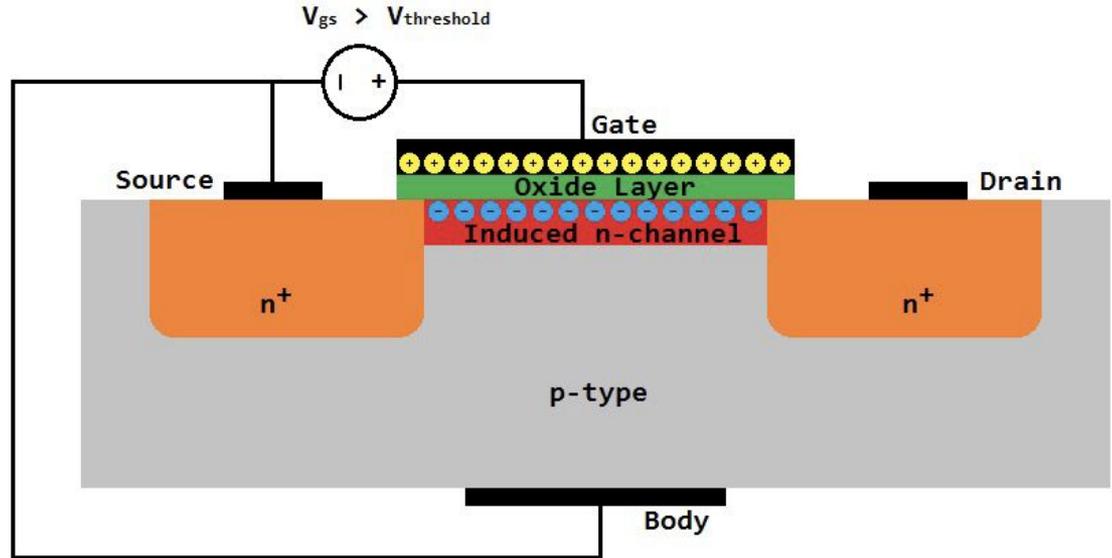
# Enhancement MOSFET Current Flow

- Current only flows when positive voltage applied to gate
  - Attracts electrons and creates an effective n-type conductive channel between the Source and Drain.
  - The oxide layer is very thin and can easily be ruptured by voltage surges. (source: [DigiKey](#)).




# Depletion-mode MOSFET

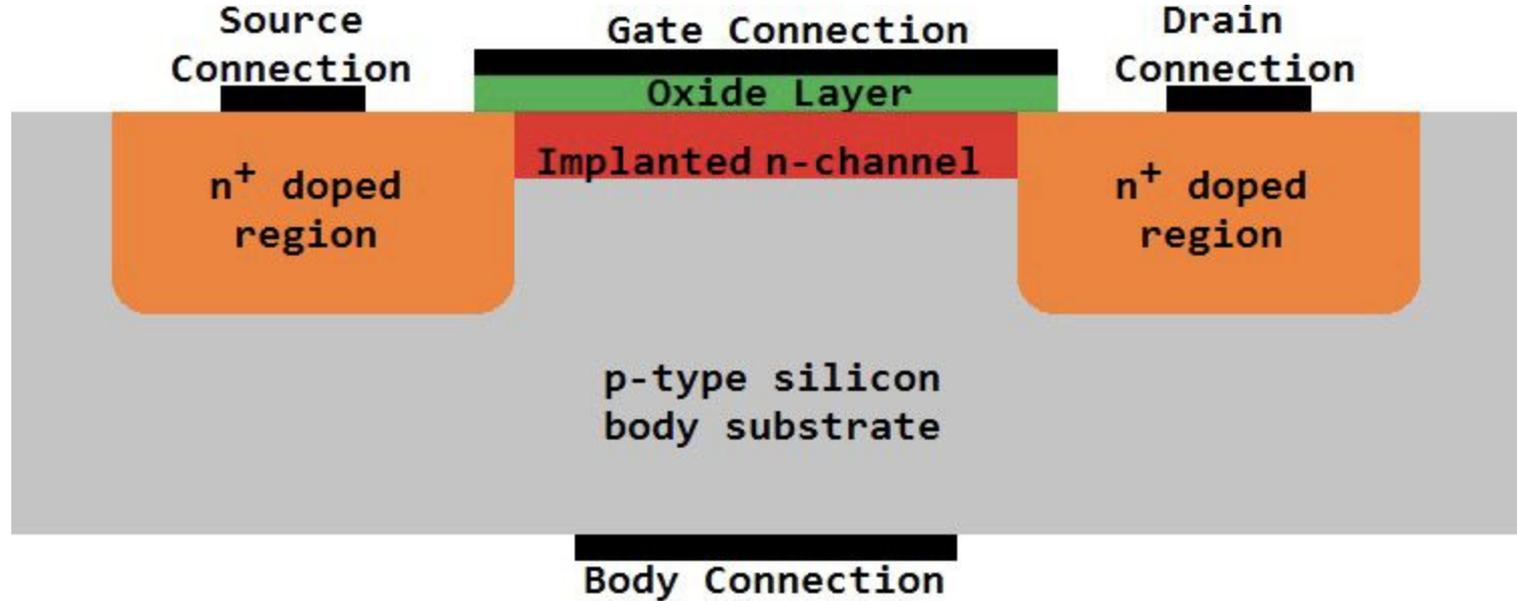


n-channel depletion-mode MOSFET. Current can normally flow through the n-type connection between Source and Drain. (source: [DigiKey](#)).

# Depletion MOSFET Current Flow

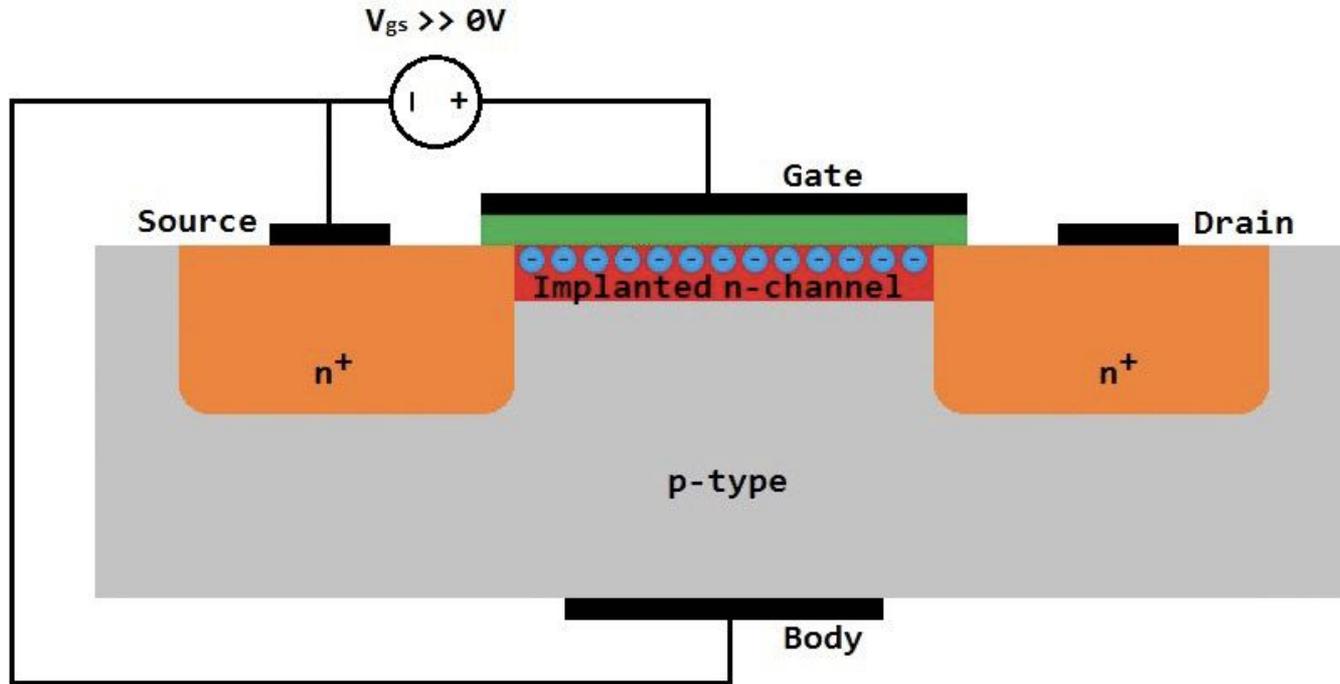

Current increases when positive gate voltage attracts electrons and enhances the conduction channel. (source: [DigiKey](#)).

# Depletion MOSFET Current Blocked

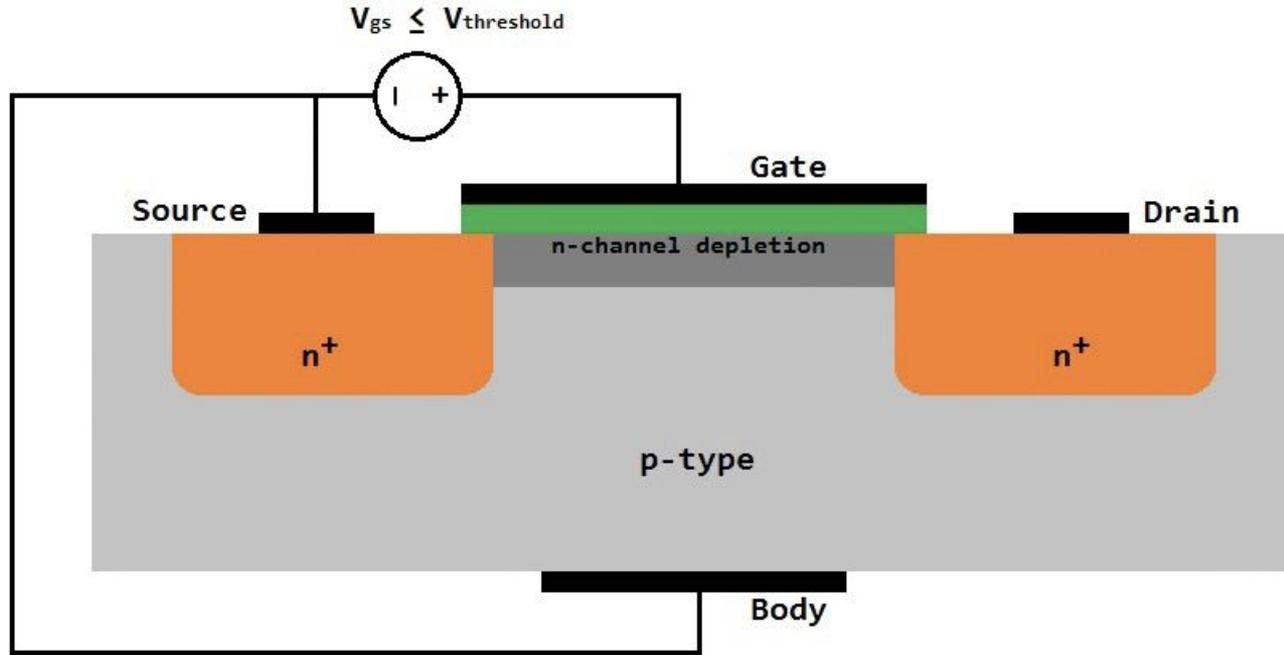


Current is blocked when a negative Gate voltage repels electrons from the connection, turning it effectively into p-type. (source: [DigiKey](#)).

# Bipolar Junction Transistor (BJT) vs Field Effect Transistor (FET)

	Bipolar Junction	Field Effect
Carriers	bipolar ( $e$ and $h$ )	unipolar ( $e$ or $h$ )
Controlled by	current	voltage
Terminals	<b>E</b> mitter, <b>B</b> ase, <b>C</b> ollector	<b>S</b> ource, <b>G</b> ate, <b>D</b> rain
Input Impedance	$\sim k\Omega - M\Omega$	Extremely high ( $10^9 - >10^{14} \Omega$ )
Strengths	Highest $I$ , $V$ ; robust	Faster, Higher gain, $I_{\text{switch}}=0$ , Small

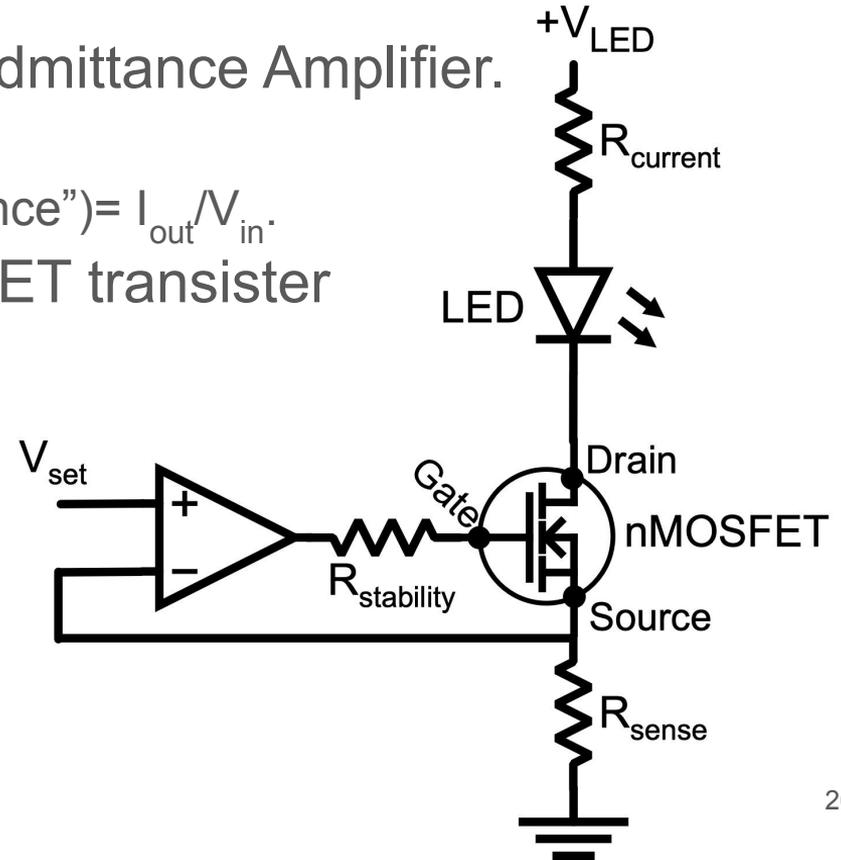
# Voltage Controlled Current Source (VCCS)

- Occasionally known as a Transadmittance Amplifier.
  - Admittance is  $1/\text{impedance}$ .
  - Transadmittance ("transfer admittance") =  $I_{\text{out}}/V_{\text{in}}$ .
- Uses an op-amp and an nMOSFET transistor to drive a current
- $I_{\text{LED}} = V_{\text{set}}/R_{\text{sense}}$  through an LED
- The optional series resistor,  $R_{\text{stability}}$ , improves the stability of the feedback loop.



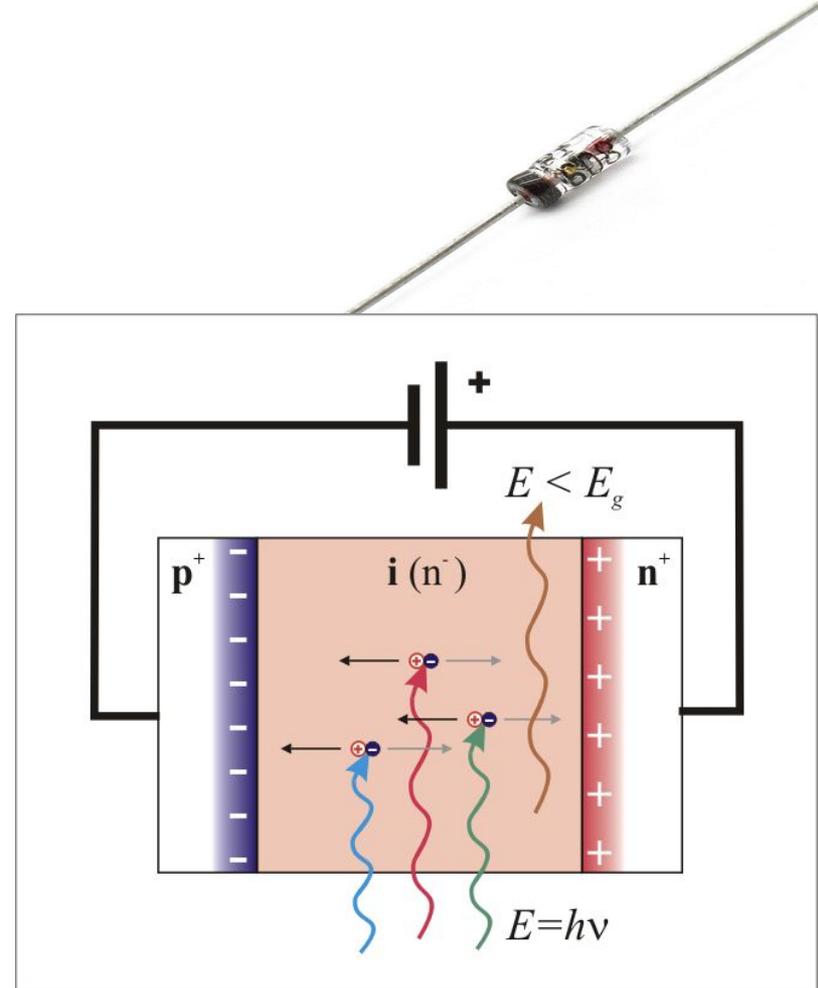
# PIN Photodiode

- PIN (p-type – intrinsic – n type) photodiode.
- When light produces electron hole pairs in the intrinsic region, a current flows. (source: [Wikipedia](#)).
- Often used as a photon detector



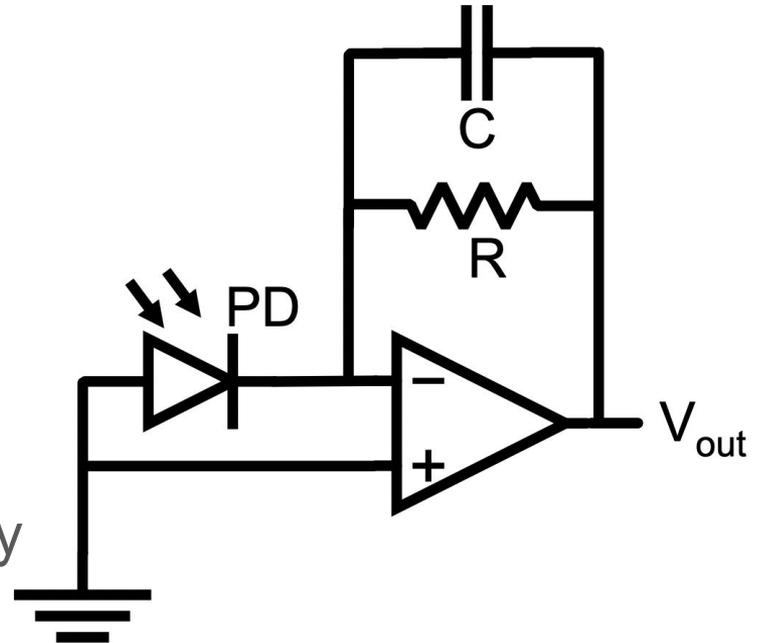
# Current Controlled Voltage Source

- Also referred to as transimpedance amplifier
  - Transimpedance is short for transfer impedance, which is the ratio of the output voltage of a circuit to its input current.
- A transimpedance amplifier uses an op-amp, with a feedback resistor ( $R \sim 1-10 \text{ M}\Omega$ ) and a feedback capacitor ( $C \sim 10-100 \text{ pF}$ ).
- $V_{\text{out}} = R * I_{\text{PD}}$
- Capacitor shorts out high frequency noise



# Arduino Controlled Light Communication

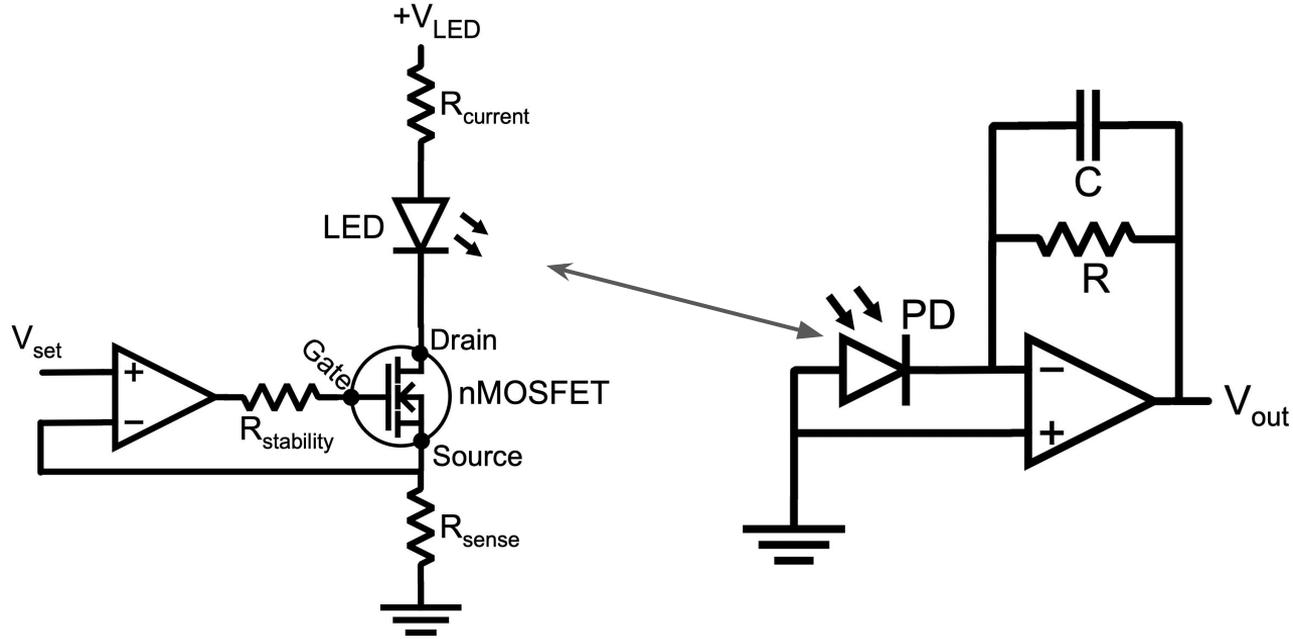

Control  $V_{set}$  with Arduino digital pin, detect LED output with photodiode, observe signal on scope

Questions?

