



# Laser Offset Lock

**Michael Sprague**  
Thywissen Lab

# Overview

- Why frequency locking?
- How to do it?
  - Frequency/filter method
  - Phase lock loop
- What we have done
- What we could do better/future work

# Laser locking

- Absolute frequency:

Spectroscopy (Saturation, polarisation)

- Relative frequency:

Offset lock, phase and frequency

Why? Replace AOMs, flexible

- **Goal:** Address  $F = 11/2$  to  $F = 9/2$   $^{40}\text{K}$  hyperfine transition for imaging, 0 to 225 G

: 820 to 1130 MHz offset from  $^{39}\text{K}_{3/2} \ ^2\text{S}_{1/2}$  to  $_{3/2} \ ^2\text{P}_{3/2}$

# Definition of Terms

**Linewidth:** Frequency fluctuations less than measurement time ( $< \text{ms}$ )

**Drift:** Frequency fluctuations greater than measurement time ( $> \text{seconds}$ )

# Phase vs Frequency Lock

Phase is time integral of frequency


Phase fluctuations cause frequency sidelobes

Can frequency locking give same performance as phase locking? Practically, no..

What makes a PLL so special?

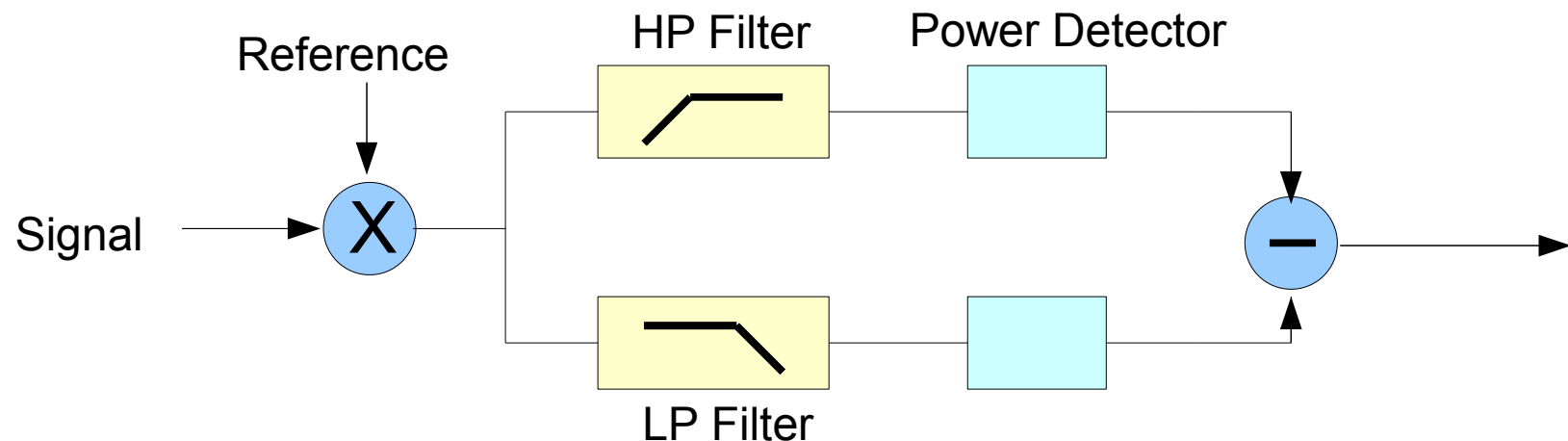
# Frequency/Filter Lock Method

- Convert Frequency to voltage
  - Buy Frequency to voltage converter (max = 1 MHz)
  - Make one, filter method (MIT/Harvard group)


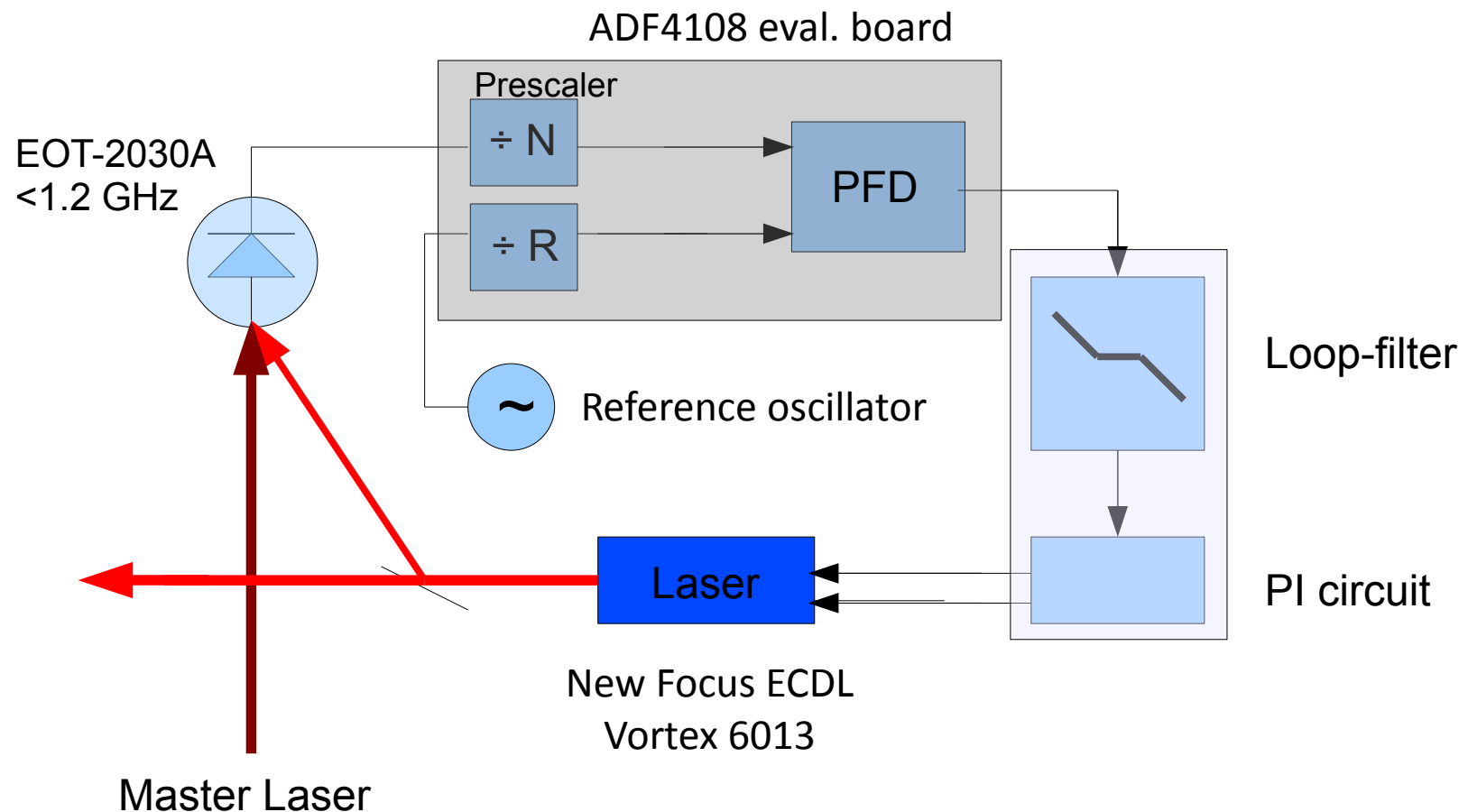
# Optical Phase Lock Loop

Prescaler, Phase Frequency Detector/Charge Pump,  
Loop Filter/Servo circuit, Laser controller




# Prescaler

- Divides down beat signal from GHz to 10s MHz
- Simple pulse counter:  $f_{\text{out}} = f_{\text{in}} / (A * P)$ ,  $A = 1, 2, \dots$
- Dual modulus:  $f_{\text{out}} = f_{\text{in}} / (A * P + B)$ ,  $B < A$ ,  $P = 2^n$
- Example:  $f_{\text{in}} = 1 \text{ GHz}$ , want  $f_{\text{out}} = 20 \text{ MHz}$ ,  $P$  (set by prescaler) = 8  
 $A=6$ ,  $B=2$ . Count  $(P+1)*B$  pulses (pulse swallower), then count  $(P)*(A-B)$  pulses, then outputs one pulse.



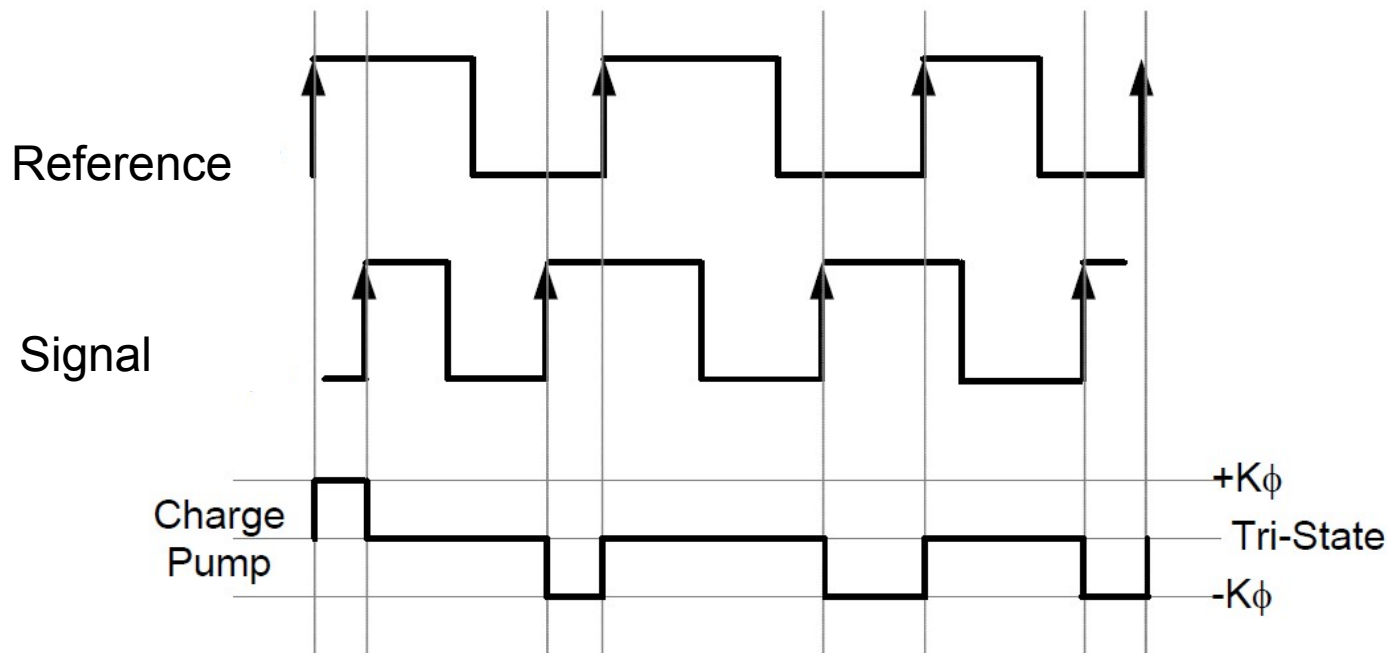
# Phase Frequency Detector (PFD)

- Have two signals (Reference and Beat Signal), need to detect phase/frequency difference
- Options: I) Mixer II) PFD
- PFD implemented with XOR or JK Flip-flops




# Phase Frequency Detector

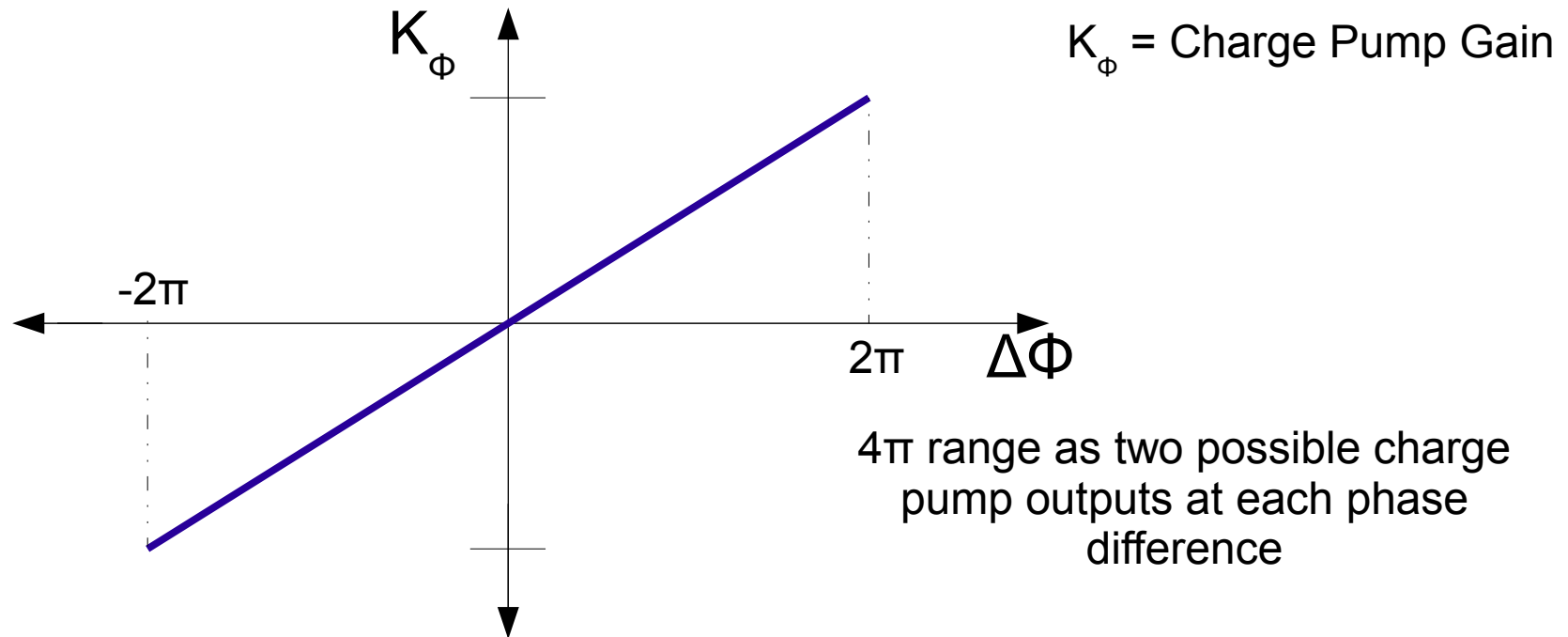

$$\Delta\Phi = 0$$

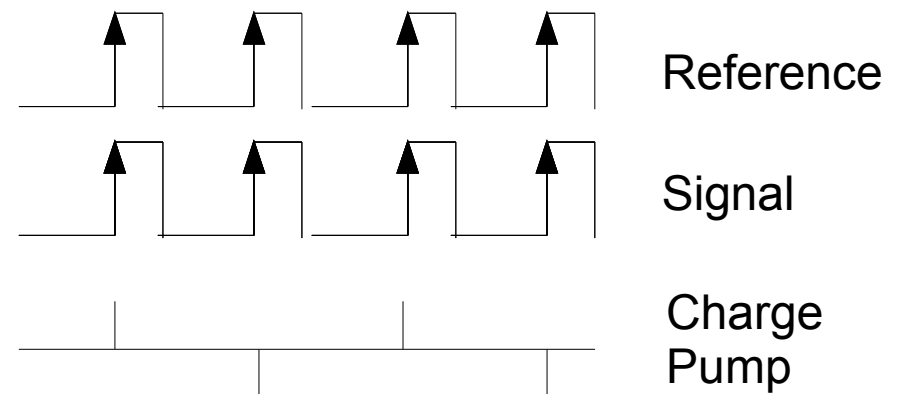
- Spurs at divided down reference frequency


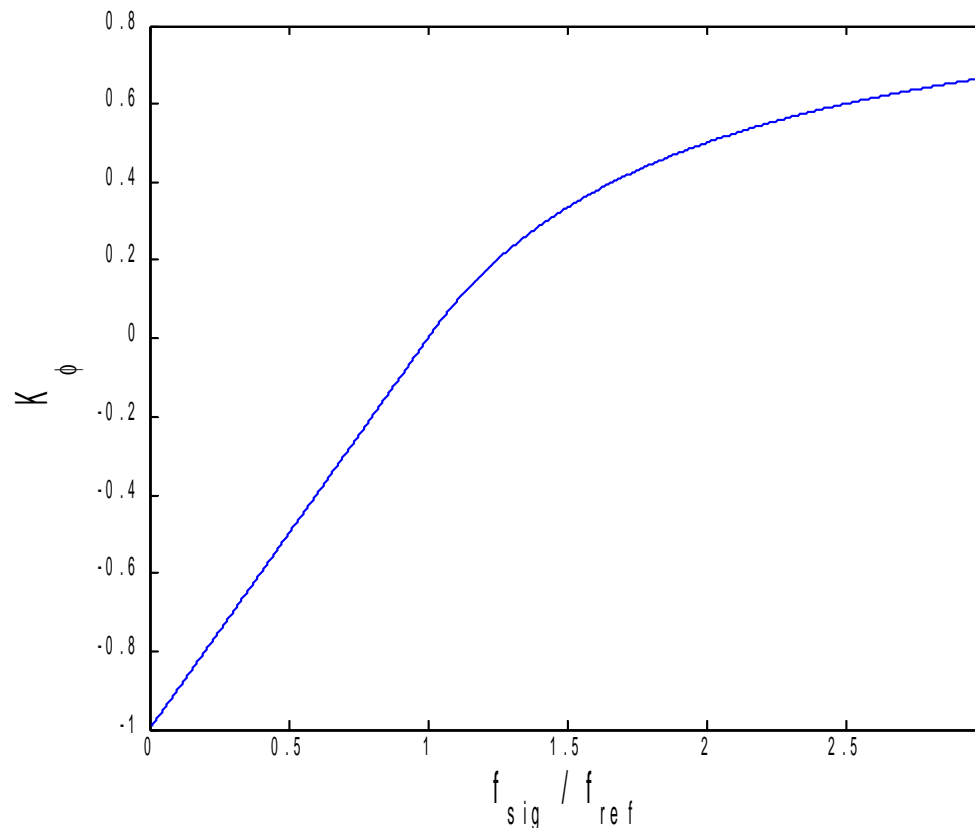
# Phase Frequency Detector

What about different frequencies?


$$\Delta\phi = (1 - f_{\text{sig}}/f_{\text{ref}}) \quad \text{for } f_{\text{sig}} < f_{\text{ref}}$$




Assumed initial phase relation  
(identically zero)

If relation varied, structure  
apparent = phase correlations

Initial  $\Delta\phi = \pi$

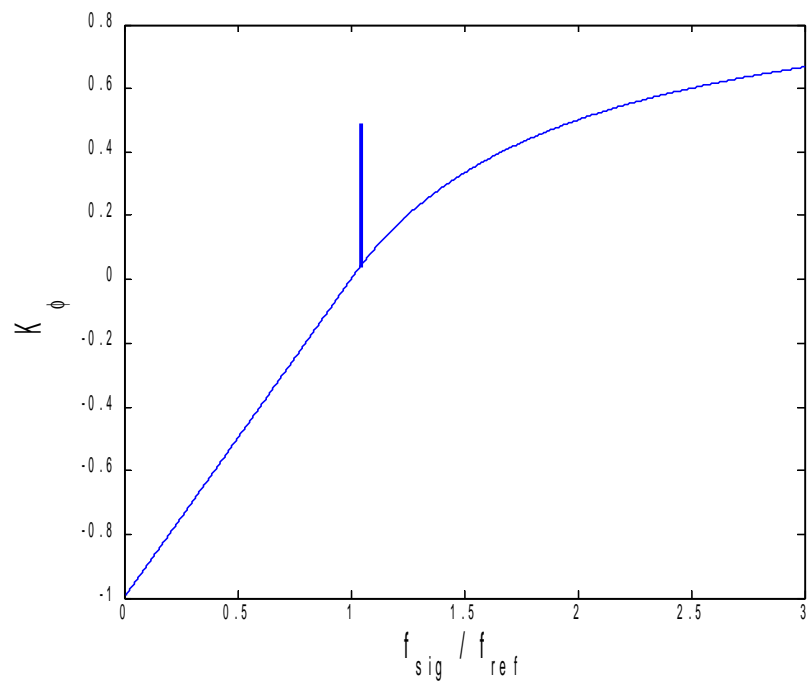


Initial  $\Delta\phi = -\pi$

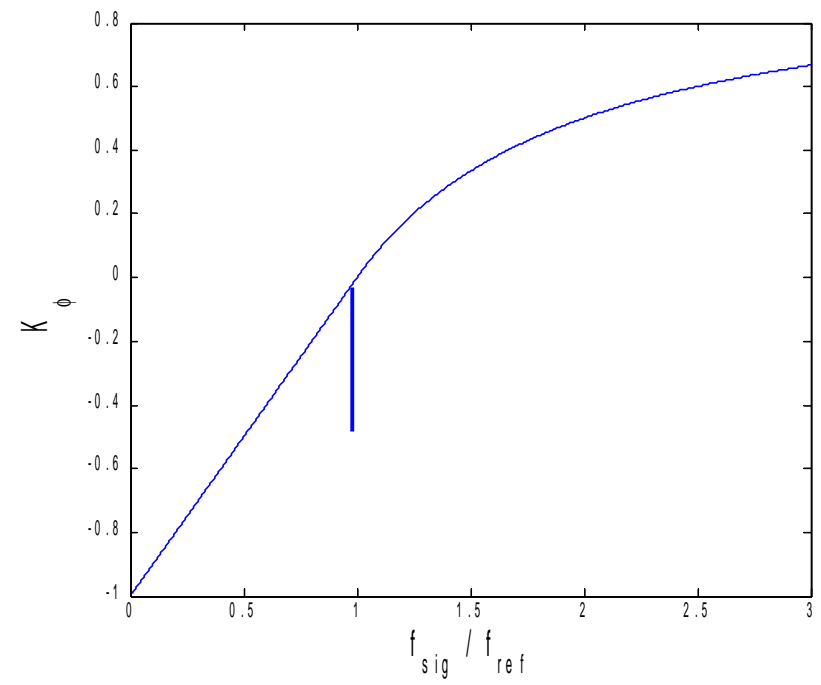

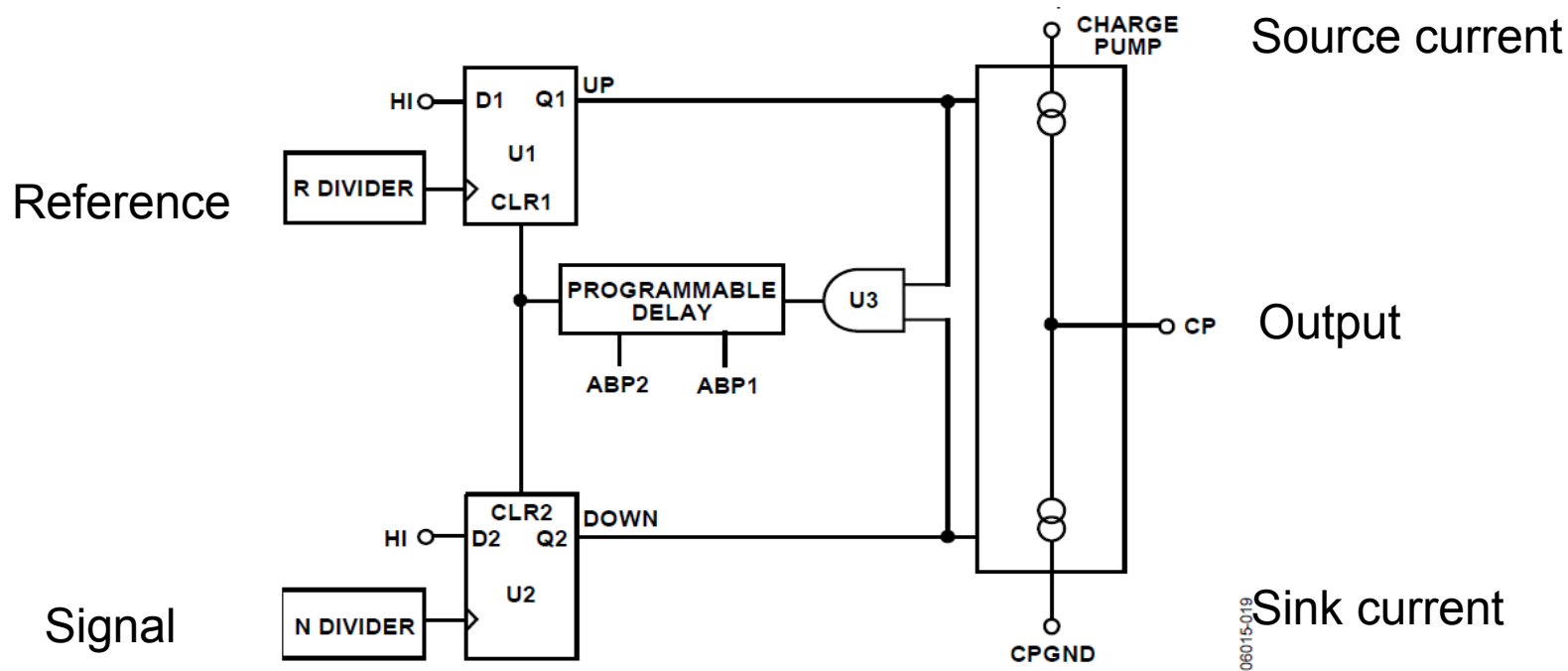
# Charge Current Pump

- Phase difference proportional to time average of current pulses



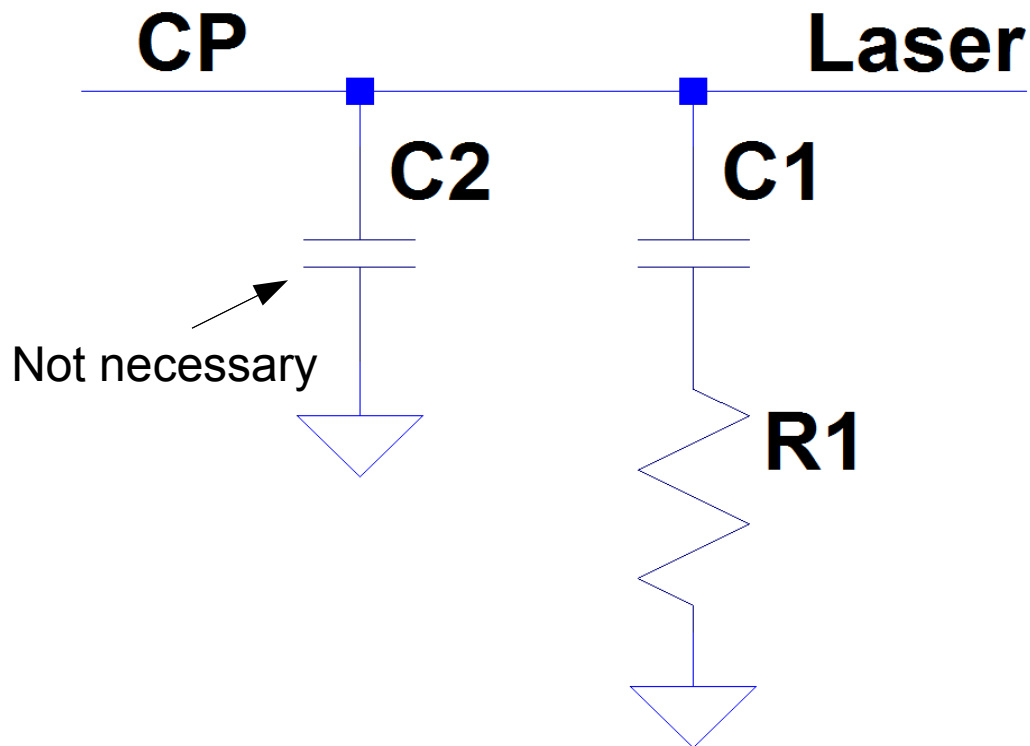
# Loop Filter



- Need to eliminate high-frequency component from charge pump current



Can use higher order filters as well

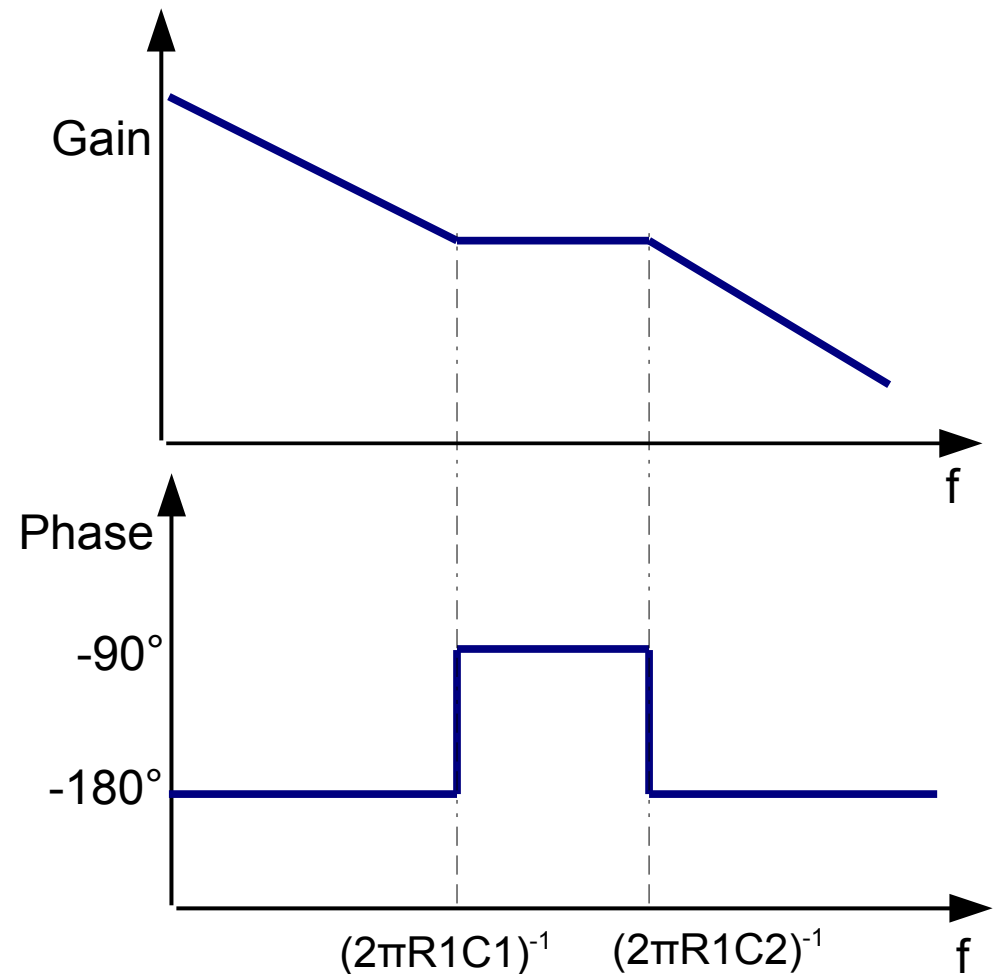


# PLL OL Transfer Function

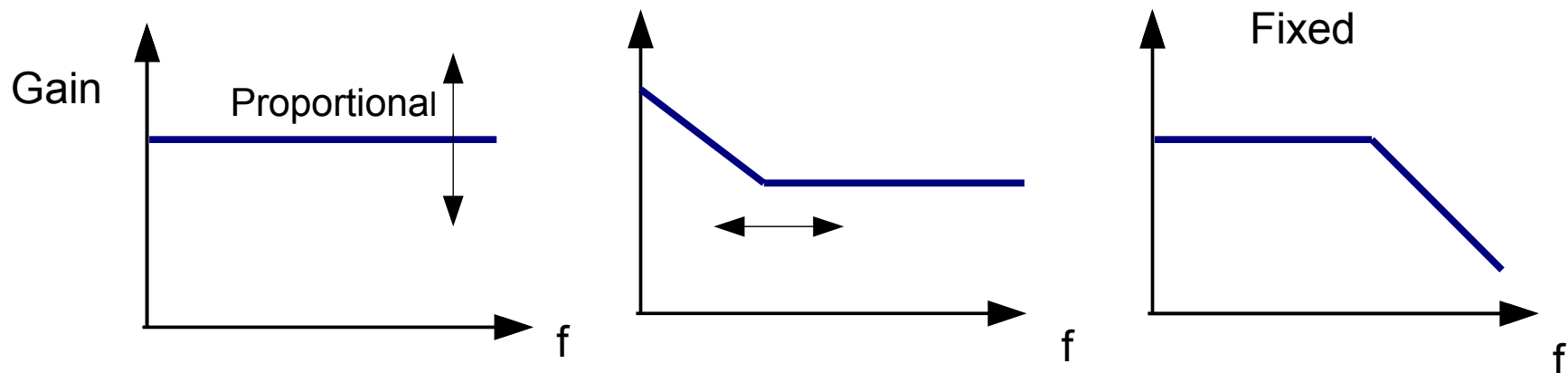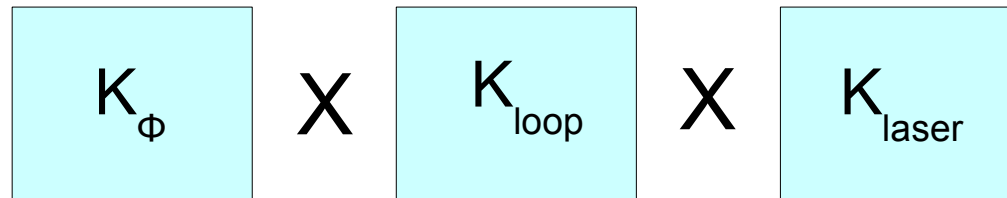

Closed Loop Gain

$$CL(s) = \frac{OL(s)}{1 + \frac{OL(s)}{N}}$$

# Implementation

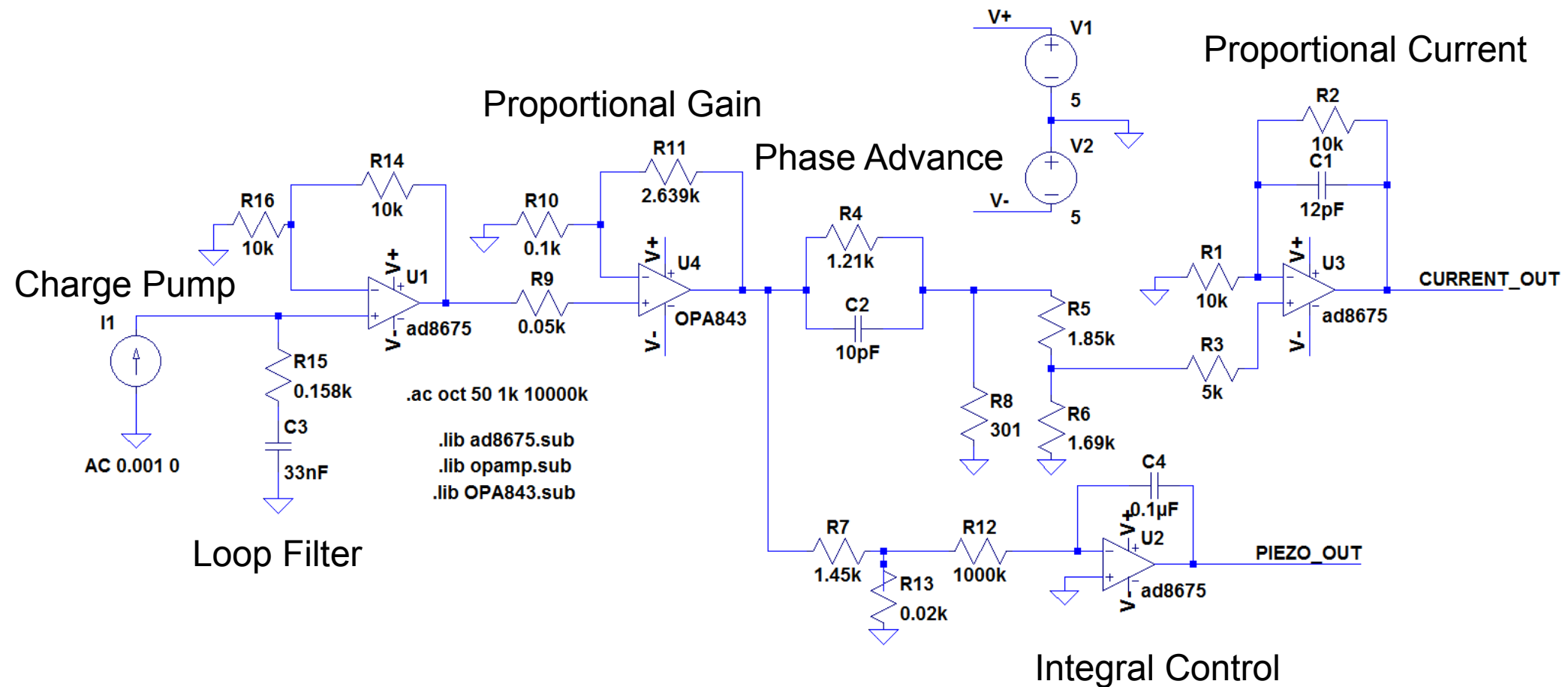





# Stability and Barkhausen Criteria

Open loop stability criteria, phase and gain margin

Phase margin:  $180^\circ + \phi$  at  $G = 0$  dB

Gain margin:  $-(G)$  at  $\phi = -180^\circ$



'Nominal' values = 15 dB GM,  $50^\circ$  PM

Intuitive, but not sufficient criteria for *instability*\*


Use Nyquist criteria:  $OL(j\omega)$  remains to right of  $OL(j\omega) = -1$  for increasing frequency. Rigorously Contour integration about  $-1$  related to number of OL poles in real positive plane

\* Nyquist criteria necessary and sufficient


# Transfer Function

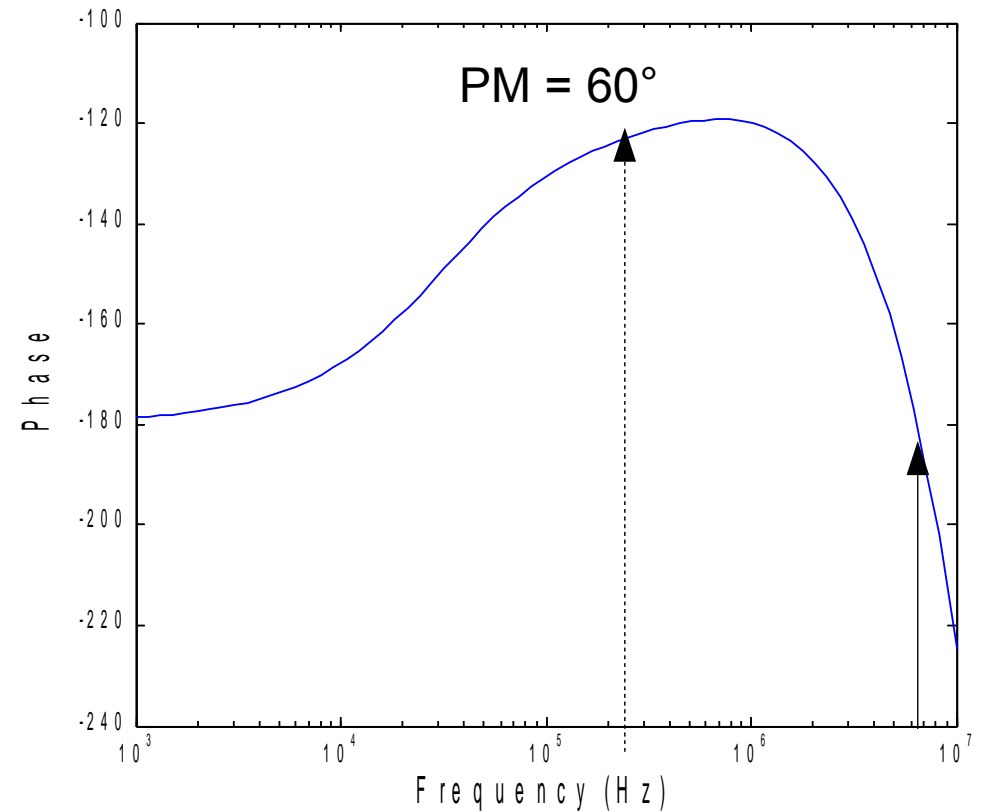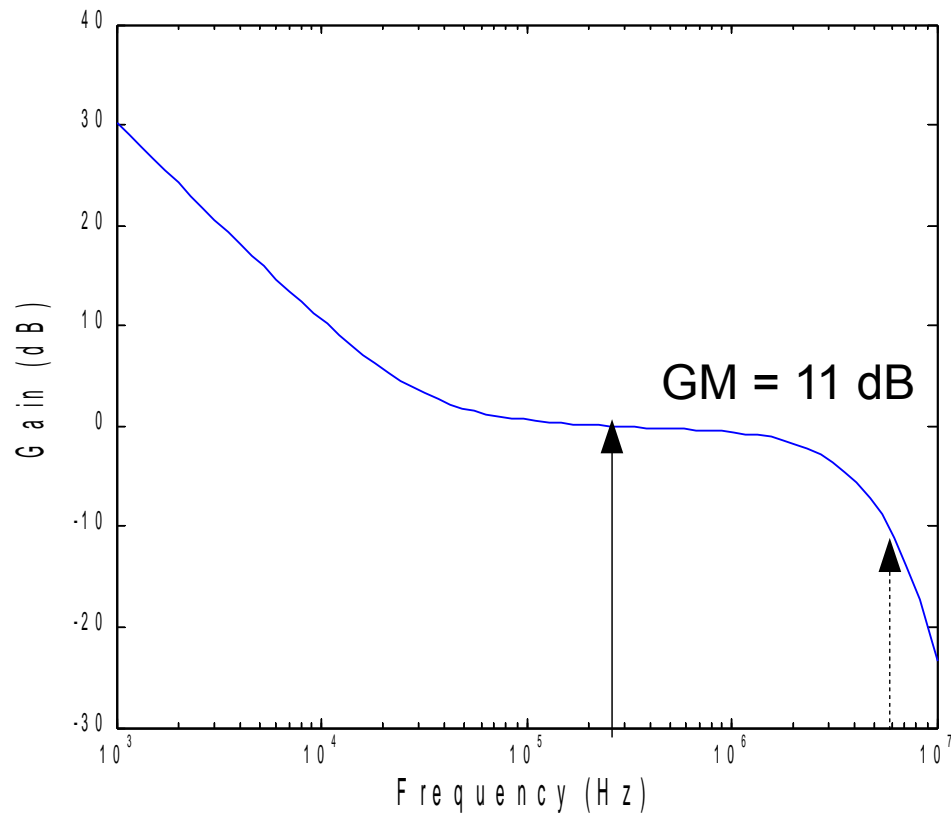

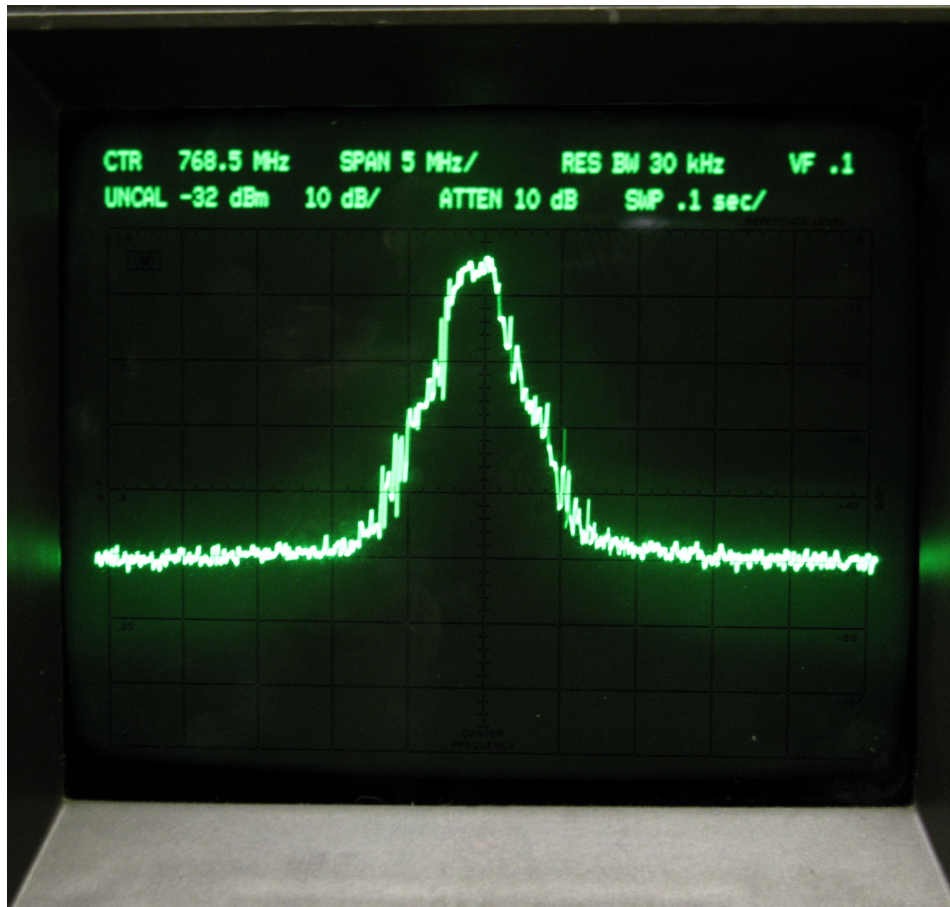Loop Filter + Servo control circuit + Laser Transfer Function  
Values above few MHz probably not reliable




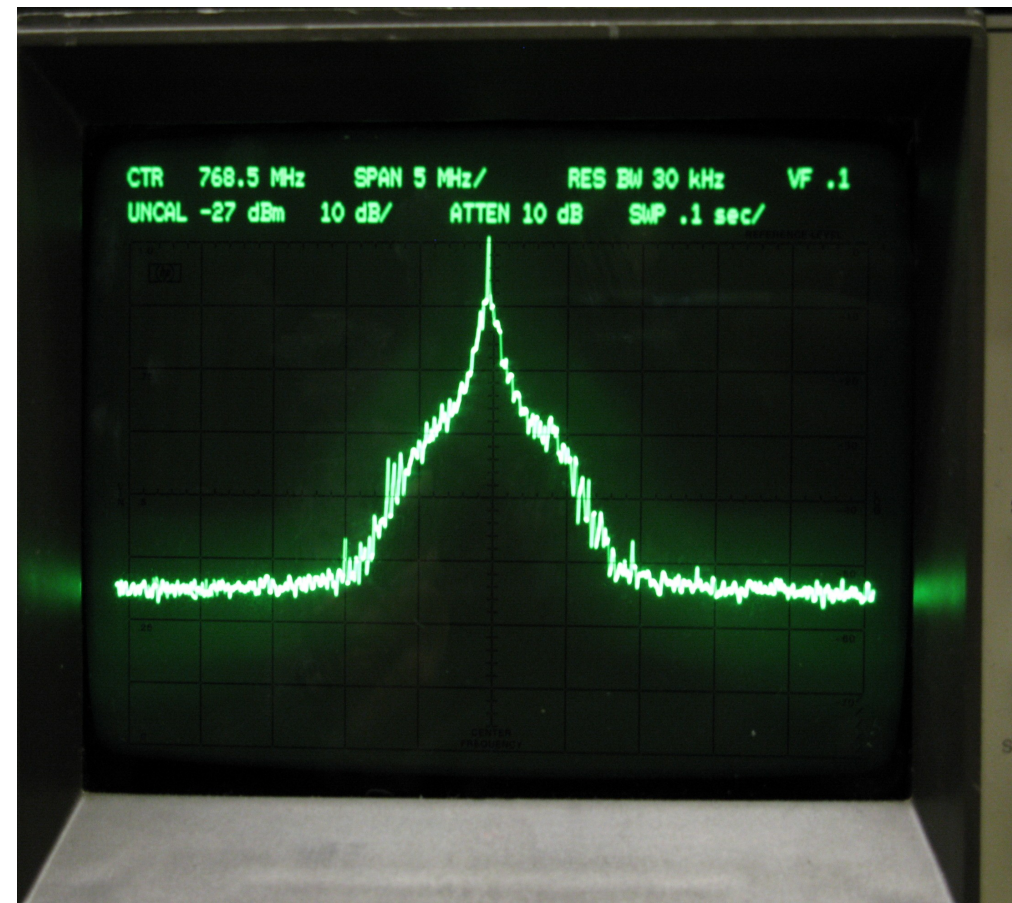**PIEZO Feedback only**, Span = 5 MHz/div  
Resolution BW = 30 kHz, 10dB/div




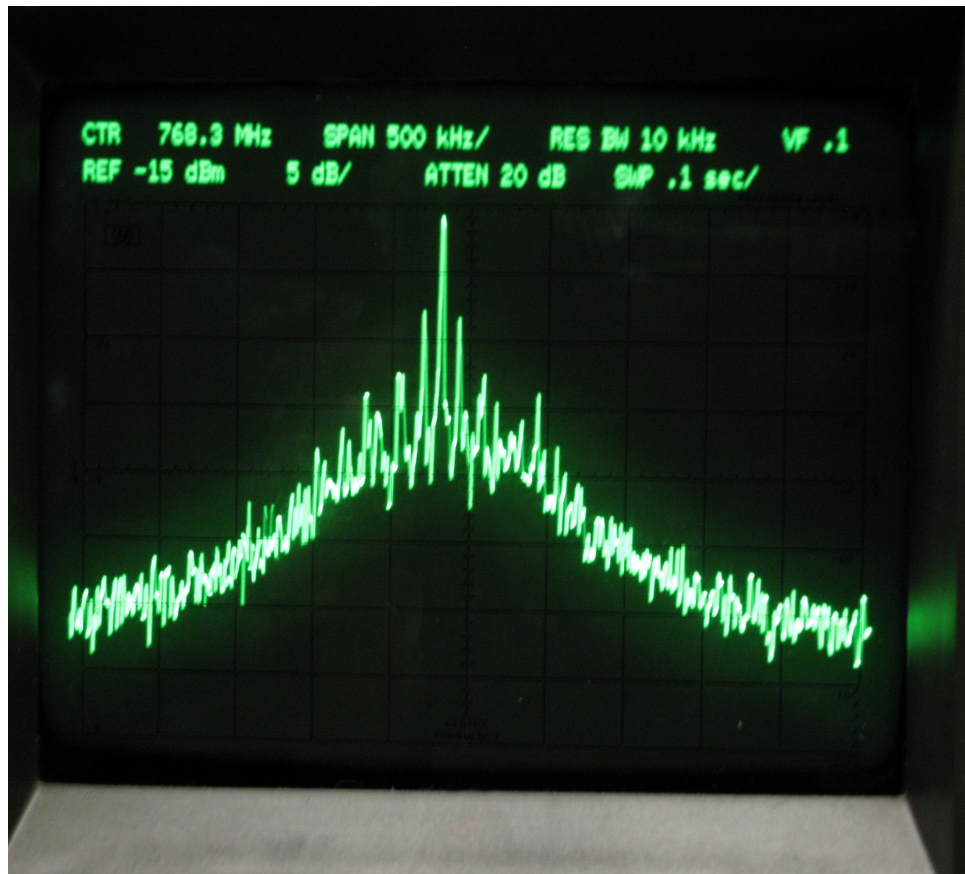**PIEZO + Current Feedback**, Span = 5 MHz/div  
Resolution BW = 30 kHz, 10dB/div





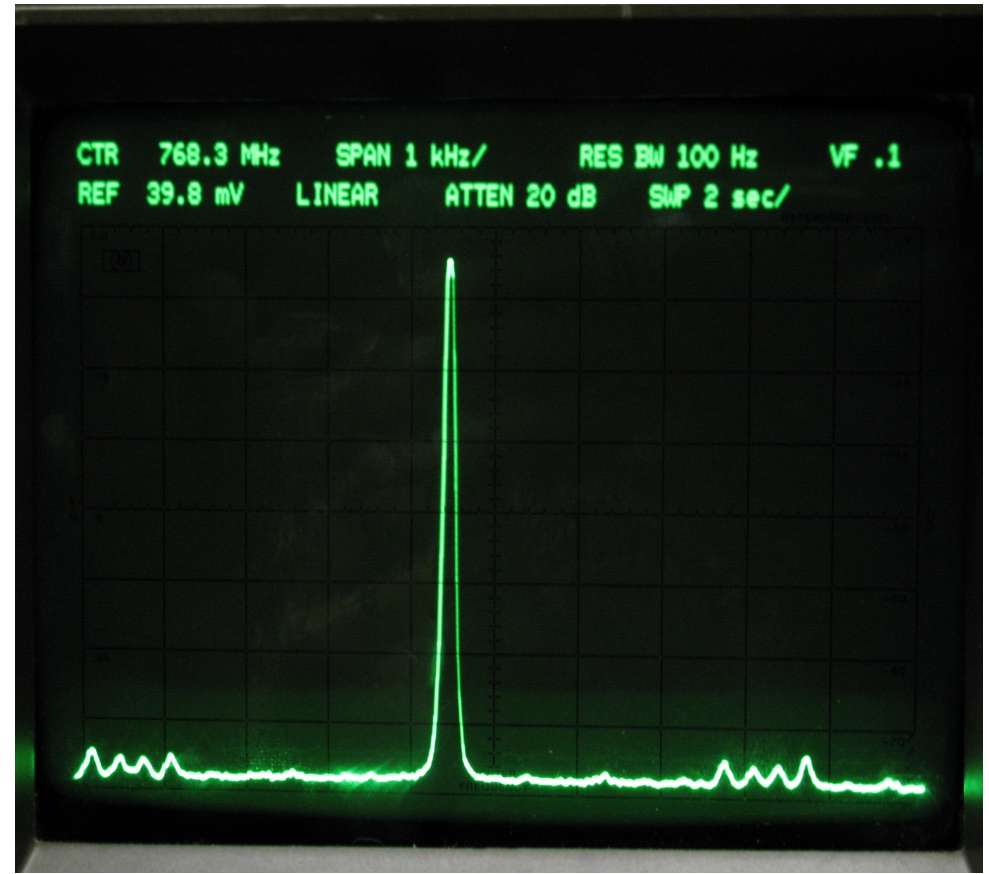**PIEZO + Current Feedback** , Span = 0.5 MHz/div, Resolution BW = 10 kHz



**PIEZO + Current Feedback**, Span = 1 kHz/div, Resolution BW = 100 Hz, **LINEAR**

# 110 kHz Spurs

Major problem for phase coherent exps.


Remaining considerations:

- Remove all switching power supplies
- Connect ground of laser to table
- Circuit instability, Replace op-amps
- Laser controller

Love to hear any other suggestions



# Error Signal Spectrum

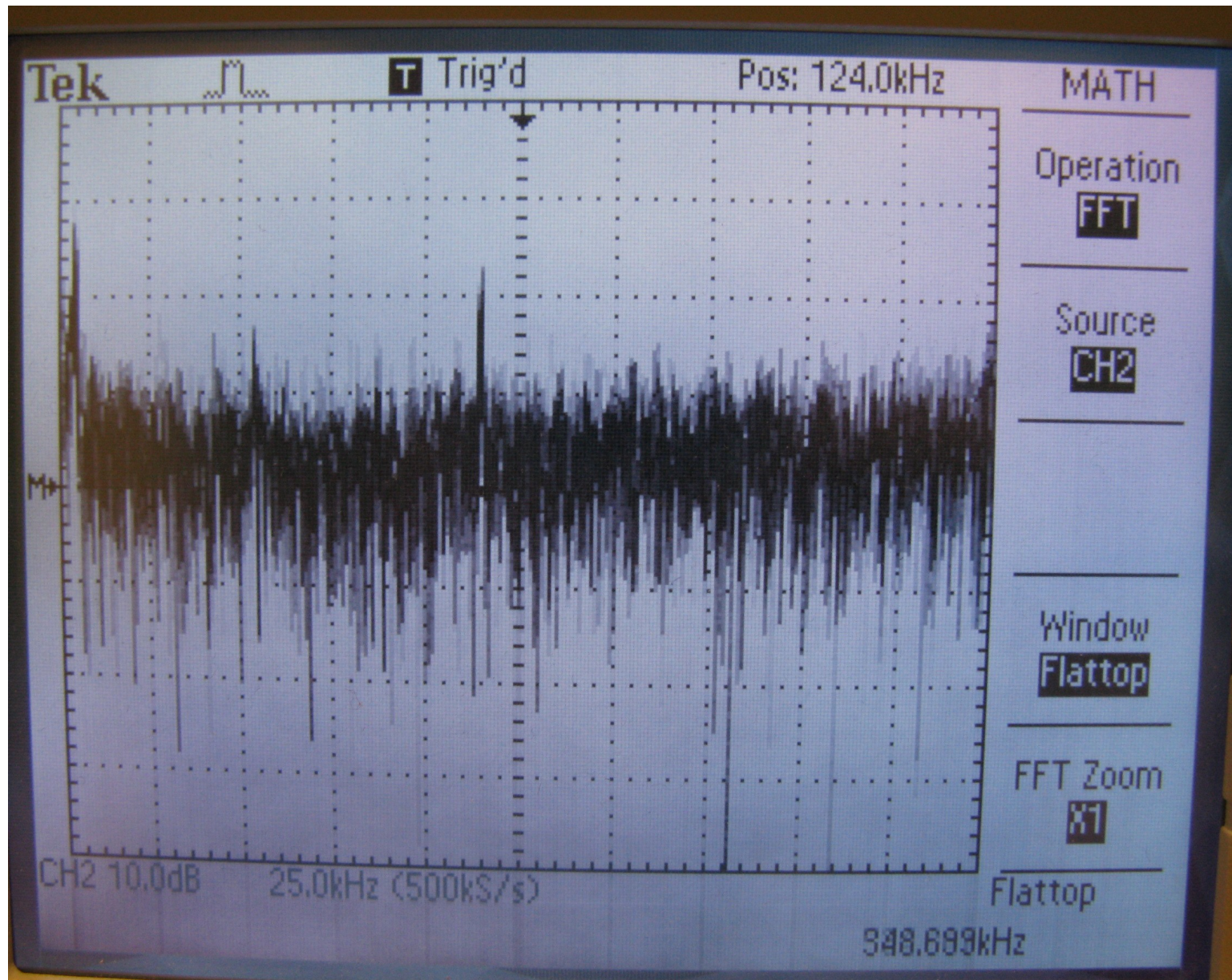

# Sweep Rate

- $\sim 10$  MHz / ms. Might not be fast enough.
- Limited by? Time constant of Piezo integrator
- Solution? Fix stability of Piezo path, other possibilities



# Practical Tips

- Be paranoid
- Mind grounding, switching power suppliers/converters, oscilloscopes etc..
- Don't try expect it to work on breadboard
- Make sure circuit is stable before building it, ie use Spice to estimate transfer function
- Use ADIsimPLL to get rough idea of desired transfer function (measure laser controller transfer function)

# Future Work

- New board, make Piezo arm stable.
- Filter method (probably not)
- 110 kHz sidelobes

# Thanks!

Jason, Alan

Alma, Dave, Dylan, Joseph, Joon, Karl, Lindsay, Matthias

## References

Banerjee D. PLL Performance, Simulation and Design. 4<sup>th</sup> Edition. 2006

Best RE. Phase Lock Loops. 5<sup>th</sup> Edition. McGraw Hill; New York 2007

Jacobs OLR. Introduction to Control Theory. 2<sup>nd</sup> Edition. Oxford University Press; Oxford 1993

Appel F. et al. Meas. Sci. Technol. **20** (2009) 055302

Analog Devices ADF4108 Manual.