

# PHY405-L08

“Fast” pulses, “High” voltage, & Digitization

# Logistics -- Final project

- 2 more regular labs to go, final project afterwards.
  - See the [project guidelines](#) for more information.
- Coordinate with [this OneNote page](#)
- We'll follow the steps of
  1. Conceptual design -- due **today**
    - a. Please discuss and come up with a project
  2. Technical design -- due Mar 13th
    - a. Try to use in-house components as much as possible
    - b. Part list finalized by the end of this day
    - c. Order will go out on Friday. Usually takes a week to get back
  3. Realization -- the two weeks following

# Project coordination

- New section with your name
- Add pages of
  - Conceptual design
  - Technical design
  - Part list
  - Etc.
- I'll collect part list by the end of Mar. 14

PHY405_2025_Final_project ▾	
Final project Guidelines	Final project guidelines
	Conceptual Design
	Technical Design
	Part List
	Part ordering status

## Final project guidelines

Tuesday, February 28, 2023 4:31 PM

<https://www.physics.utoronto.ca/apl/405/ProjectGuidelines.html>

We'll attempt to use this OneNote to coordinate the projects, especially the part lists in case new components need to be purchased.

Please create a new section with your names

Create pages like "conceptual design", "technical design", "part list", etc.

Timeline:

Mar. 6, Thursday : Conceptual design posted. Discussions and refinement is allowed in the week following.

Investigation of new parts needed, vs can we build the project with in-house components.

Mar. 13, Thursday: Technical design posted. Part list needs to be finalized by the end of the day.

Mar. 14, Friday: Purchase order sent out for parts required.

Mar. 21/24: Building final project

# Lab 7 – Fast Pulses


- Labs 5 and 6 were small complete systems, and Lab 7 is the most complex yet.
- Build voltage multiplier to convert 5V amplitude AC into almost 30V DC.
- Use this voltage to power a red LED working as a Single Photon Avalanche Detector (SPAD).
- Feed the SPAD pulses into a discriminator circuit that produces a digital output pulse when the input is large enough.
- Count these digital pulses with your Arduino.

# Fast Signals

- Many physics and communication signals are fast, i.e. very short or high frequency. Need to worry about
  - Capacitances
  - speed of light (foot/ns)
  - dispersion
  - digital processing speeds
  - ...
- Lab 7 looks at short pulses produced by single photons interacting in an LED.
- This requires higher voltages, so we will also need to build a voltage multiplier.

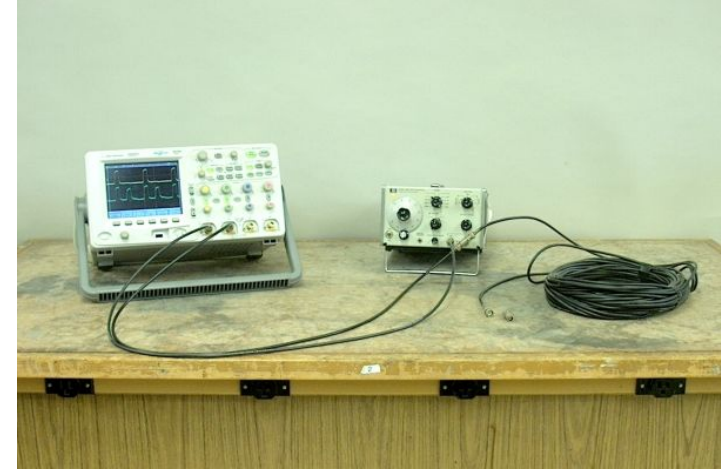
# Fast pulse in cables

- High frequency signals behave more like EM waves
- They take time to travel through the circuit.
  - Speed of light  $\sim 1$  ft/ns
  - Velocity factor in cable  $\sim 60\text{-}80\%$
- Cables have characteristic impedance
  - Signal will reflect if impedance mismatches
  - Short circuit reflects it flipped, open circuit reflects it in phase. Other impedances does something in between.



Source: UCSB  
physics [website](#)

# SuperKamiokande

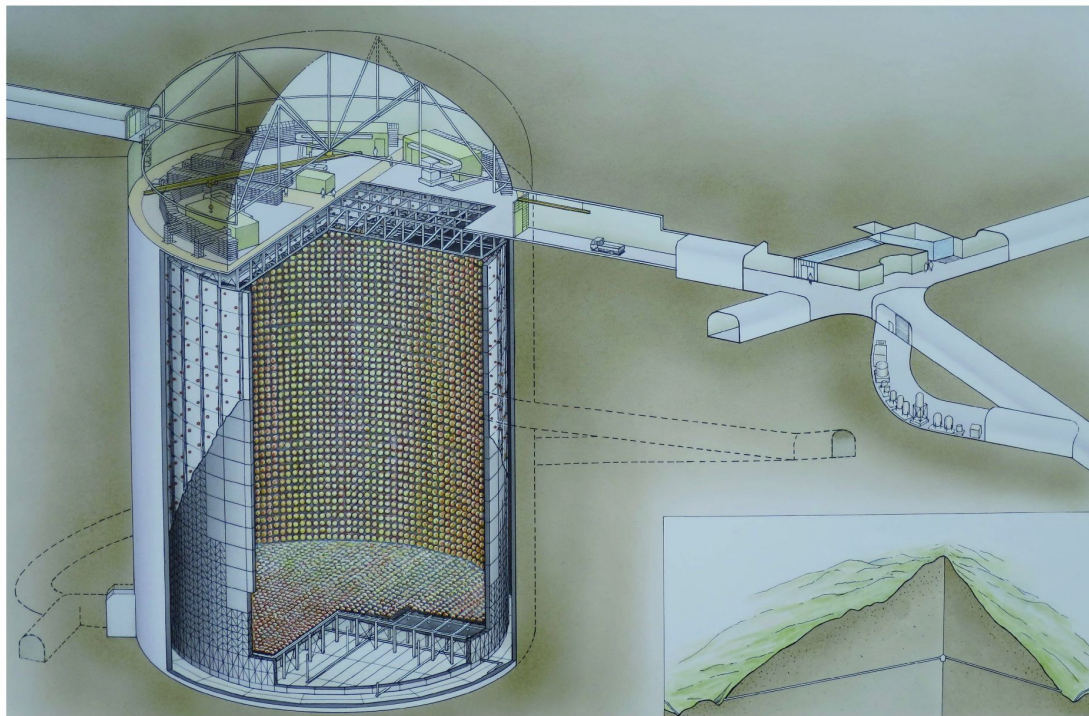


(C) 東京大学宇宙線研究所 神岡宇宙素粒子研究施設

SUPERKAMIOKANDE INSTITUTE FOR COSMIC RAY RESEARCH UNIVERSITY OF TOKYO

NIKKEI SOURCE

Super-Kamiokande neutrino and proton decay detector

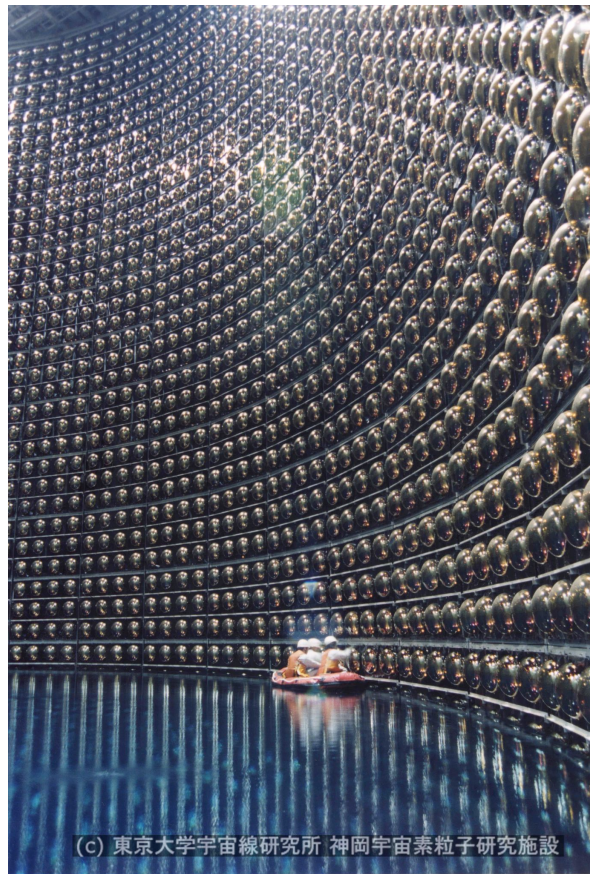
<https://www-sk.icrr.u-tokyo.ac.jp/en/sk/>



(c) 東京大学宇宙線研究所 神岡宇宙素粒子研究施設

SuperK interior




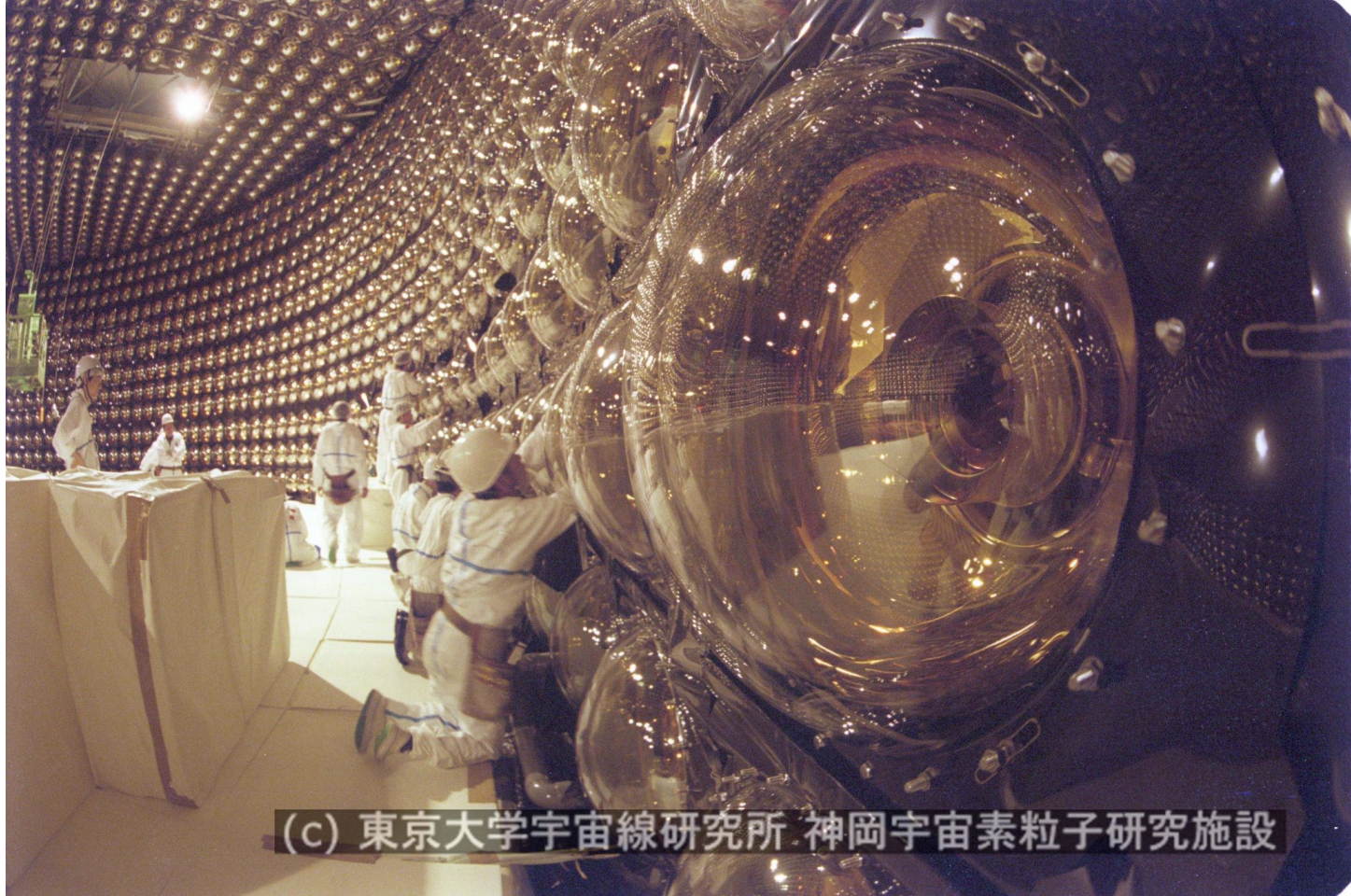


SuperK phototube installation (from [ICRR U. Tokyo](#))




# Photomultiplier Tube

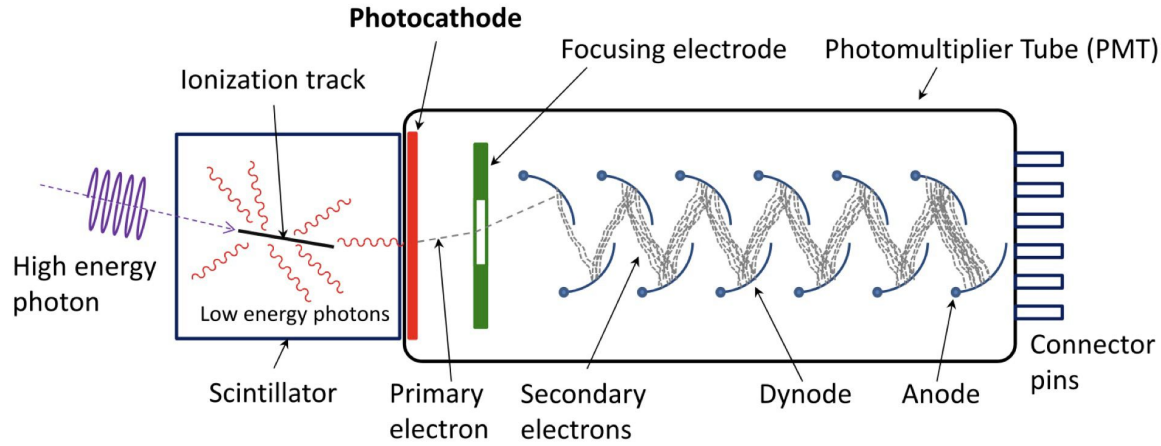

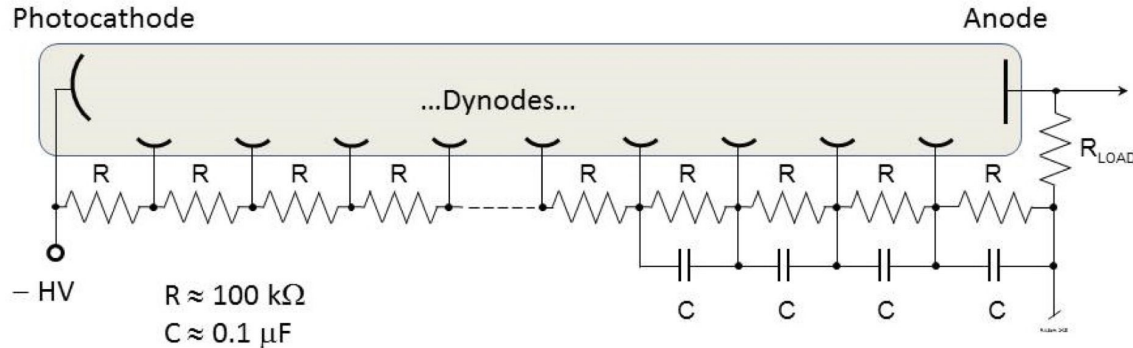Photomultiplier tube structure and circuit (from [wikipedia](https://en.wikipedia.org/wiki/Photomultiplier_tube))




# Photomultiplier Tube Pulse

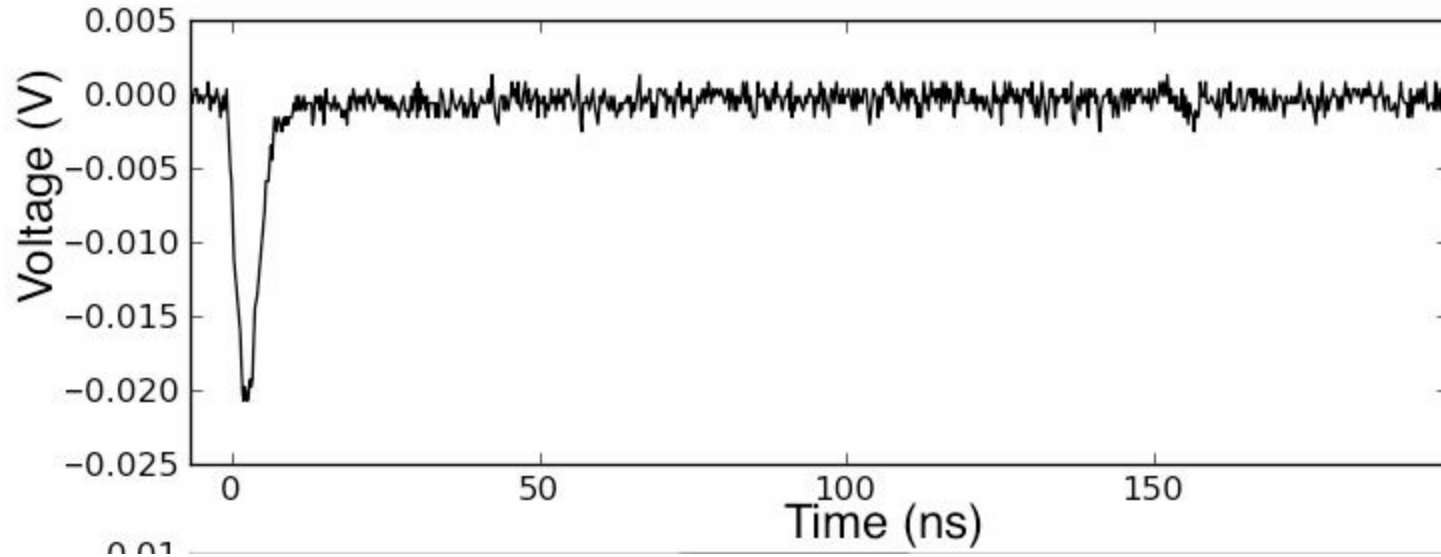


R11780 12 inch Hamamatsu1 photomultiplier tube pulse (from J. Brack et al.,  
Nucl. Instrum. Methods Phys. Res. 712A (2013) 162-173)
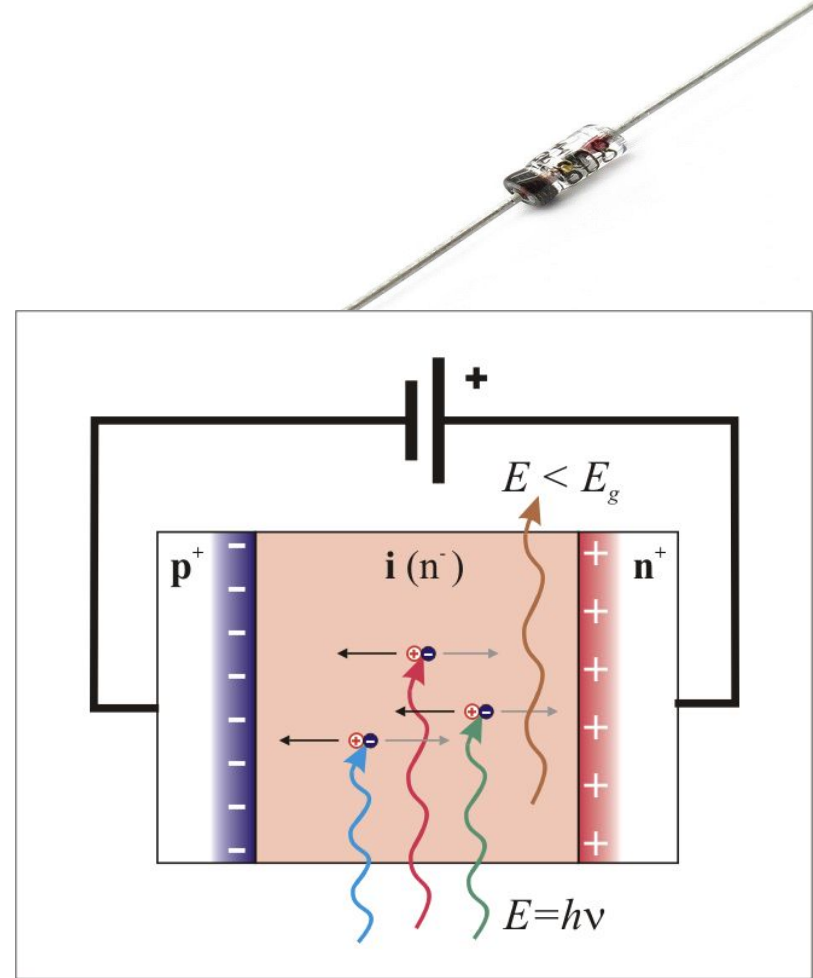
# PIN Photodiode

- PIN (p-type – intrinsic – n type) photodiode.
- When light produces electron hole pairs in the intrinsic region, a current flows. (source: [Wikipedia](https://en.wikipedia.org/wiki/PIN_diode)).
- Often used as a photon detector




# Avalanche Photodiodes (APD or SPAD)

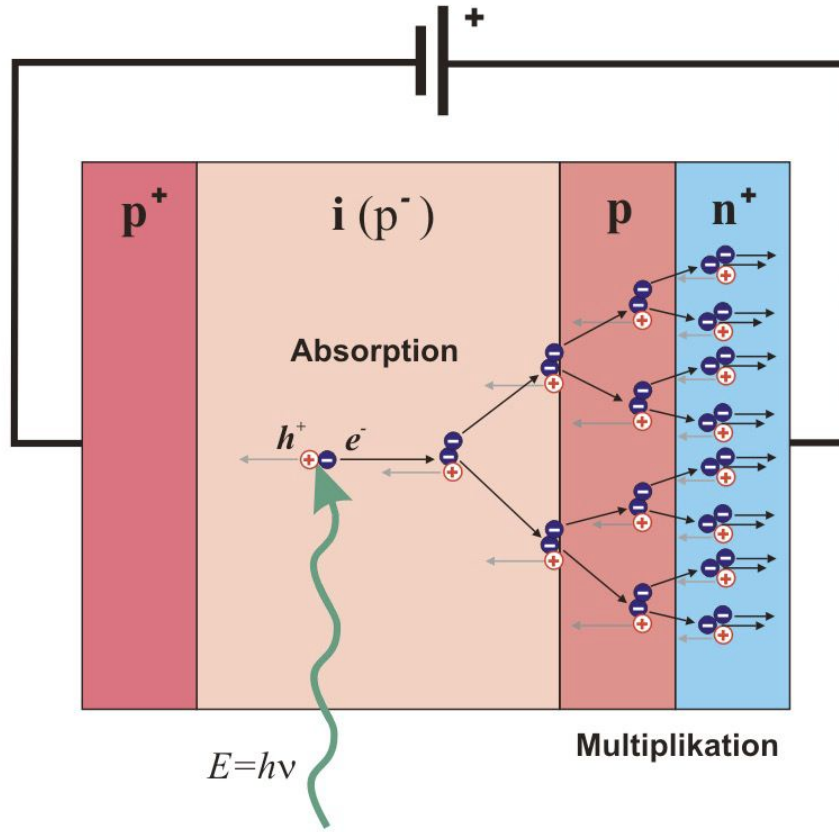

Photodiode Avalanche  
(from [wikipedia](https://en.wikipedia.org/wiki/Avalanche_photodiode))




# “SPAD” pulse from red LED

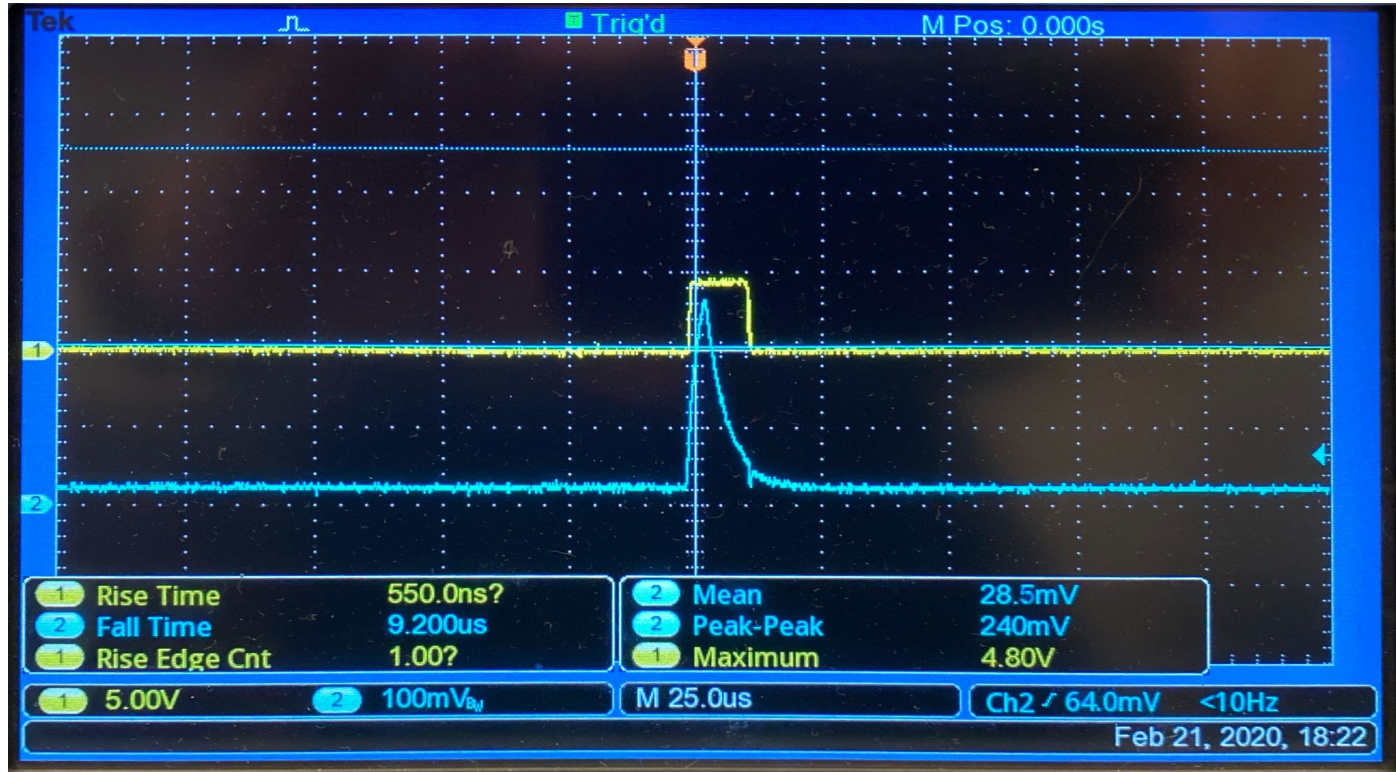


A single photon pulse from a reverse biased LLL-4223 2.5V / 10mA red LED.



# Silicon Photomultipliers

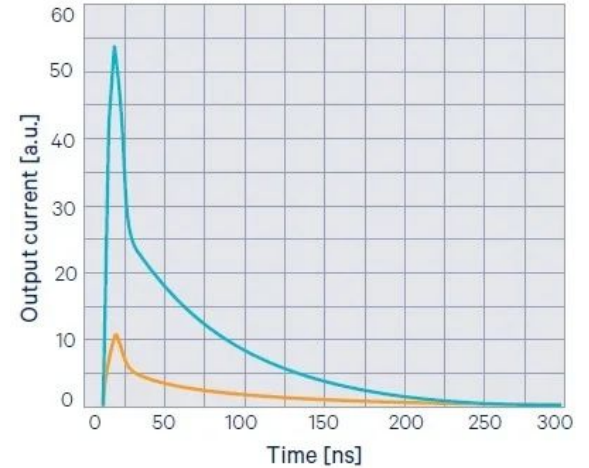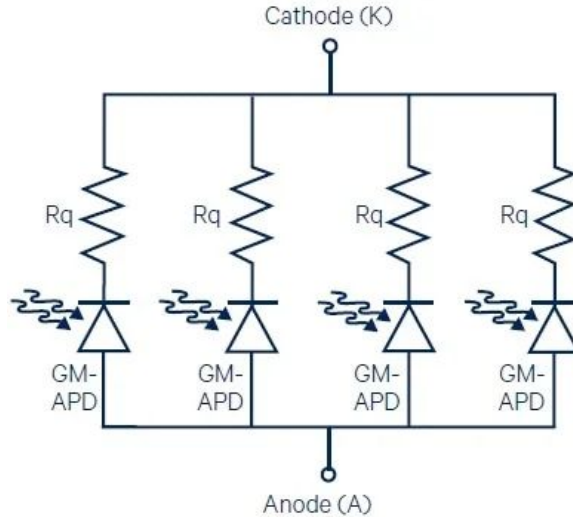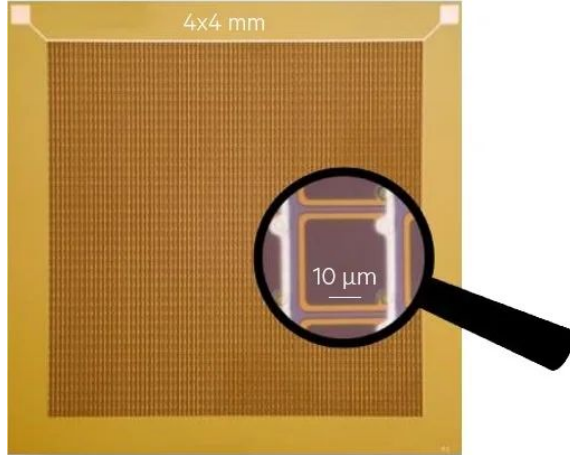

# SiPM Pulses

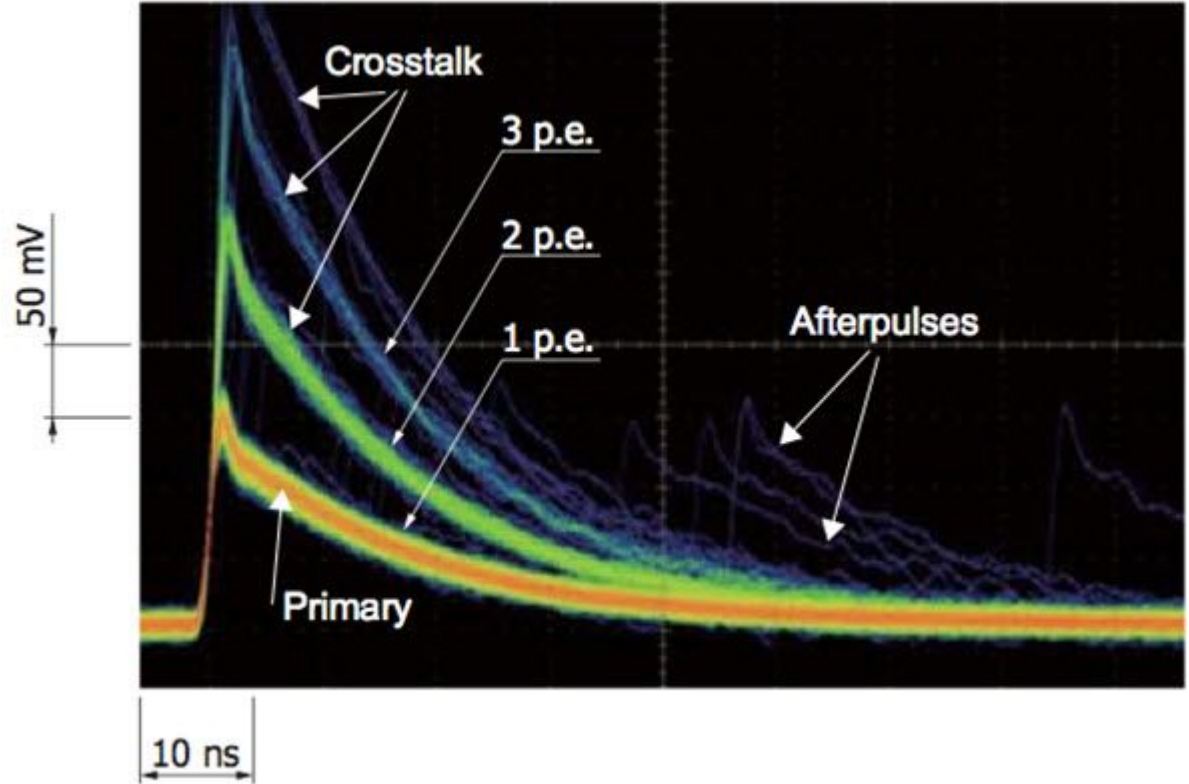


<https://hub.hamamatsu.com/us/en/technical-notes/mppc-sipms/what-is-an-SiPM-and-how-does-it-work.html>

# Photon Detectors

- Always have a dark current - an output even when there are no photons - caused by thermal excitations, quantum tunnelling....
- Afterpulsing is when an initial real photon causes additional correlated output pulses from a detector
  - e.g. because photons are produced in an avalanche and these interact and trigger a new avalanche.
- Continuous breakdown occurs at high enough voltages.
  - Zener diodes are essentially fine-tuned avalanche diodes that break down at well-defined low voltages.

# Cockcroft-Walton Voltage Multiplier

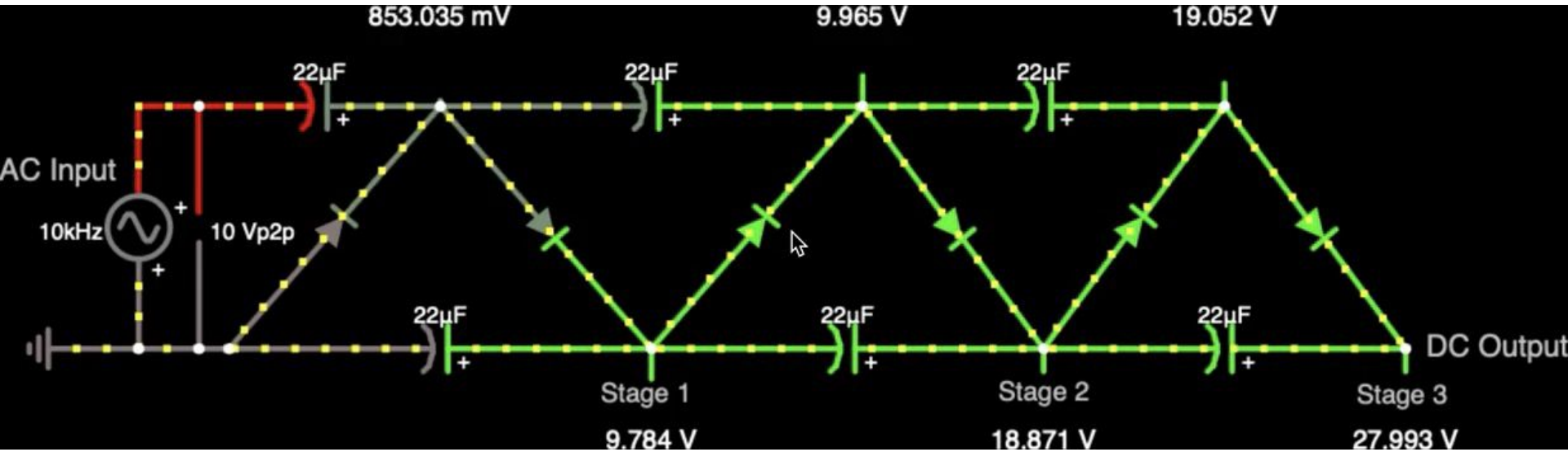

## Key principles

- diodes only conduct one way
- capacitors block DC and pass AC
- capacitors hold their charge

# 600 kV Cockcroft Walton@CERN vs. 870 kV @ PSI





# Arduino ADC


- Arduino Uno has one 10-bit Analog-to-Digital Converter (ADC) that is multiplexed to its 6 analog input pins (A0-A5).
  - It takes 13 ADC clock cycles to digitize an input voltage.
    - Except takes 25 cycles when ADC first initialized
  - Each ADC clock cycle is 128 Arduino clock cycles.
  - The Arduino Uno default clock speed is 16 MHz
- So ADC digitizes at  $16\text{MHz}/128/13 = 9615 \text{ Hz}$ .

# Arduino ADC


- Why so slow?
- Arduino ADC works by [successive approximation](#).
  - Takes at least  $N_{\text{bits}} + 1$  ADC clock cycles
  - ADC clock cycle == many processor cycles because of processing involved.
  - e.g. [4-bit example \(from \[wikipedia\]\)](#)
- Much deadtime at high rates
  - Dead time is the fraction ( $DT$ ) of time that a detector is unavailable to record new data, because it is processing previous data or needs to reset a voltage or ....
  - If the true rate is  $R_{\text{true}}$ , and each detected event makes the detector unavailable for a time  $\tau_{\text{busy}}$ , then in the simplest approximation the deadtime

$$DT = \frac{R_{\text{true}}}{1 + R_{\text{true}} \tau_{\text{busy}}}$$

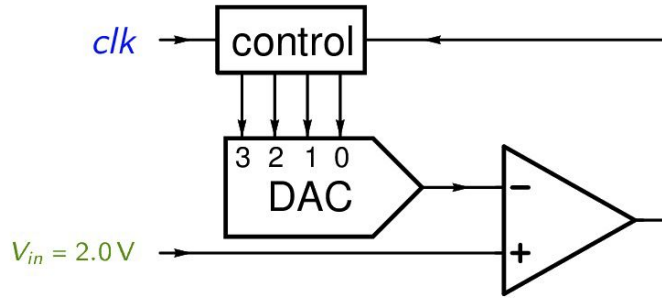
# 4-bit ADC Successive Approximation - Step 1



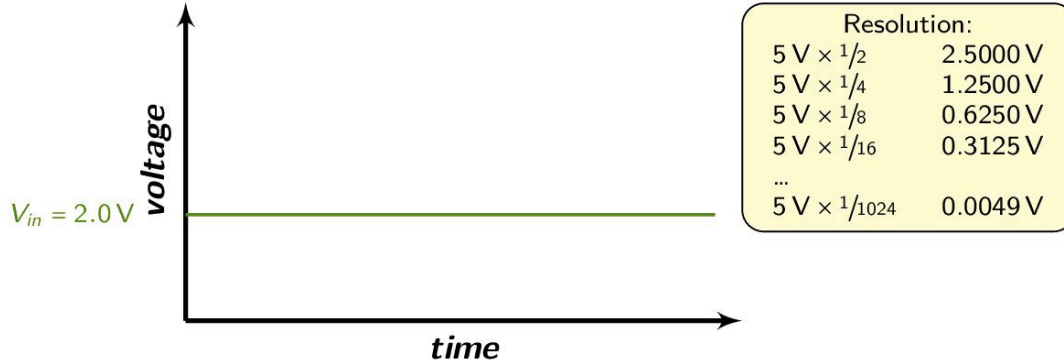
Step 1: 2.0 V input voltage on ADC input. (from [wikipedia](https://en.wikipedia.org/wiki/Successive-approximation_register))



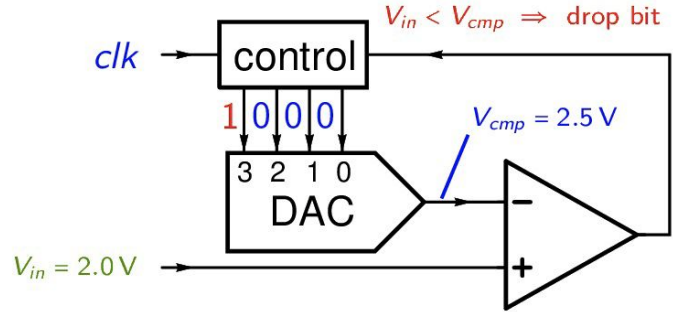
# 4-bit ADC Successive Approximation - Step 2



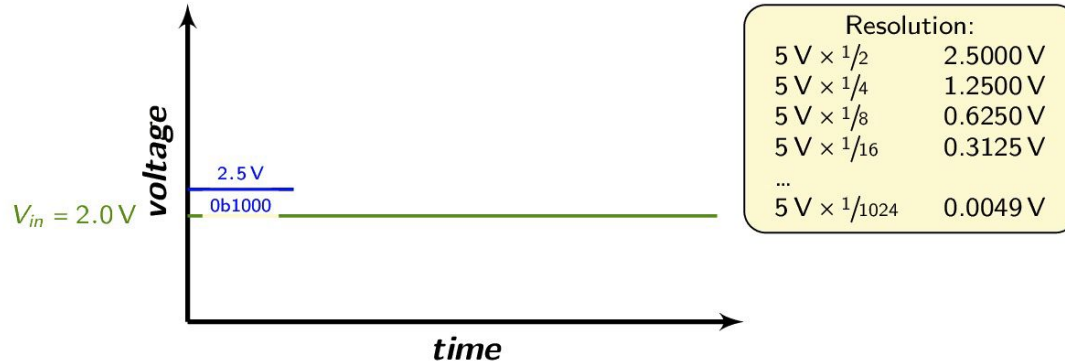
Step 2: Control Register sets highest bit (3) on 5V Digital-to-Analog Converter (DAC), which outputs 2.5 V. Both Input and DAC voltages are input to a comparator whose output determines whether the Register keeps the bit set. In this case, no.


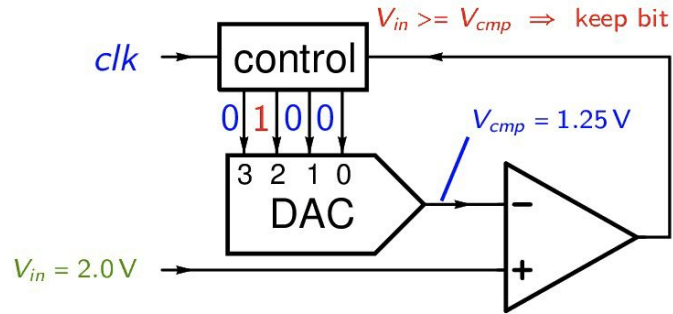
# 4-bit ADC Successive Approximation - Step 3




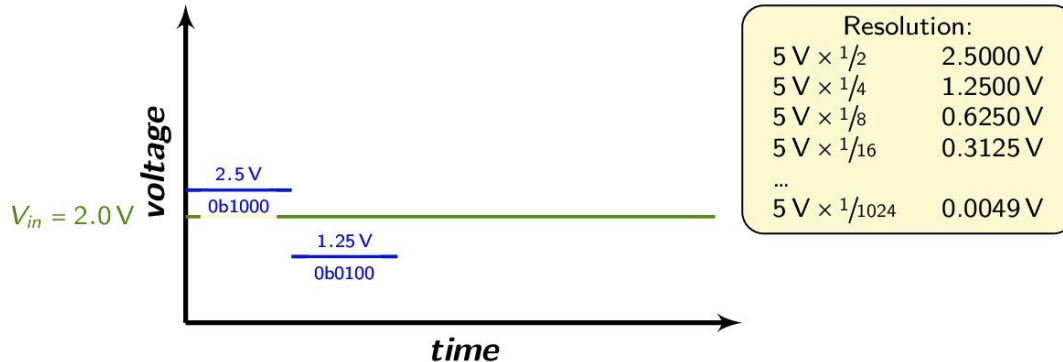Step 3: DAC bit 3 is turned off and bit 2 turned on and DAC output compared. This time the bit is kept.






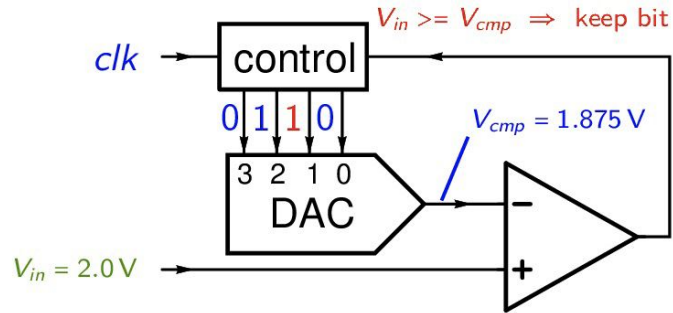
# 4-bit ADC Successive Approximation - Step 4



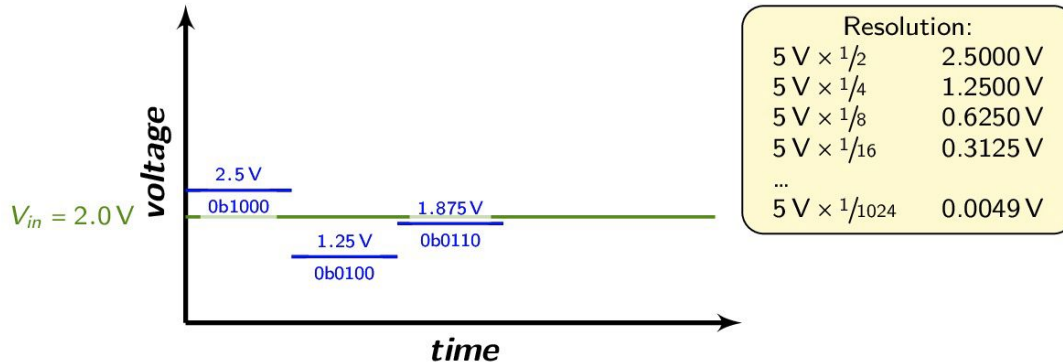
Step 4: DAC bit 2 kept; bit 1 turned on and compared.



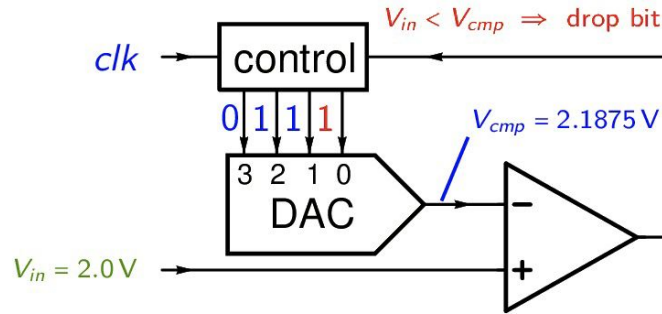
# 4-bit ADC Successive Approximation - Step 5



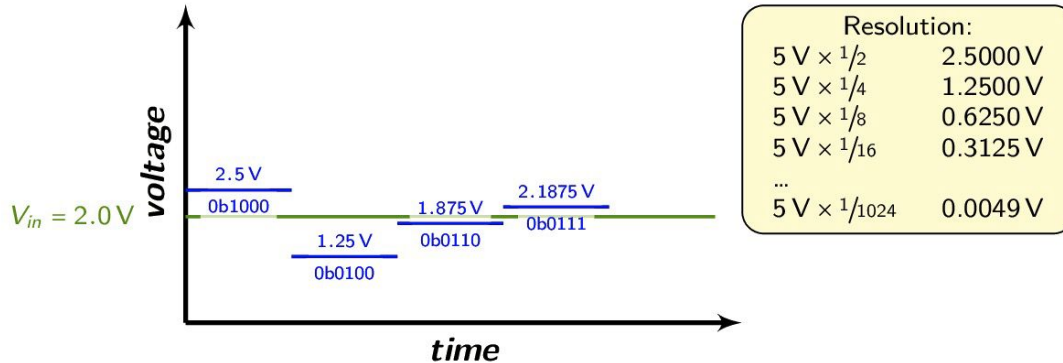
Step 5: DAC bit 1 kept; bit 0 turned on and compared.


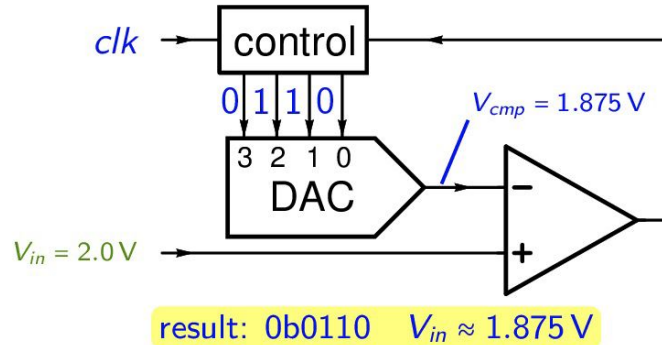
# 4-bit ADC Successive Approximation - Step 2






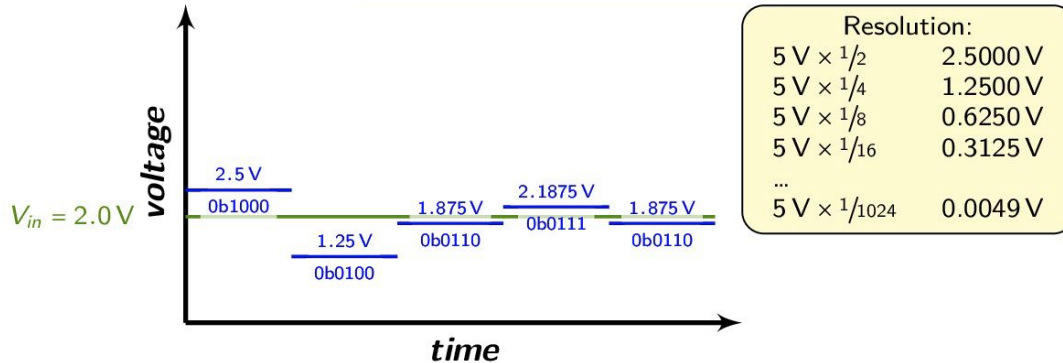Step 6: DAC bit 0 turned off, and final result set.


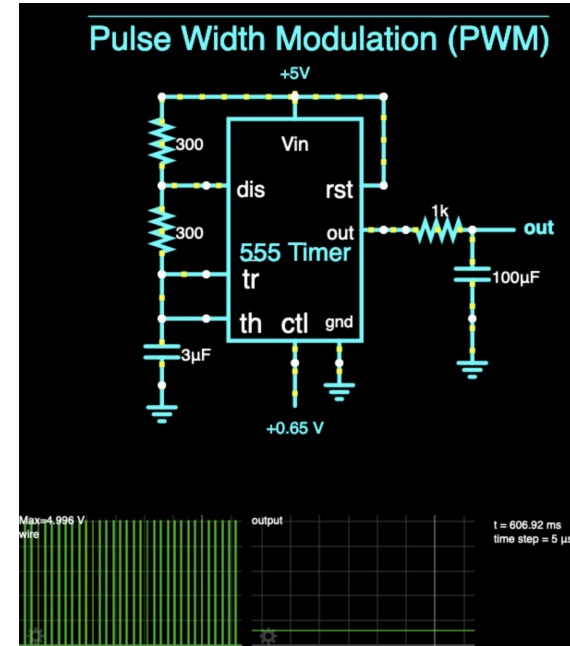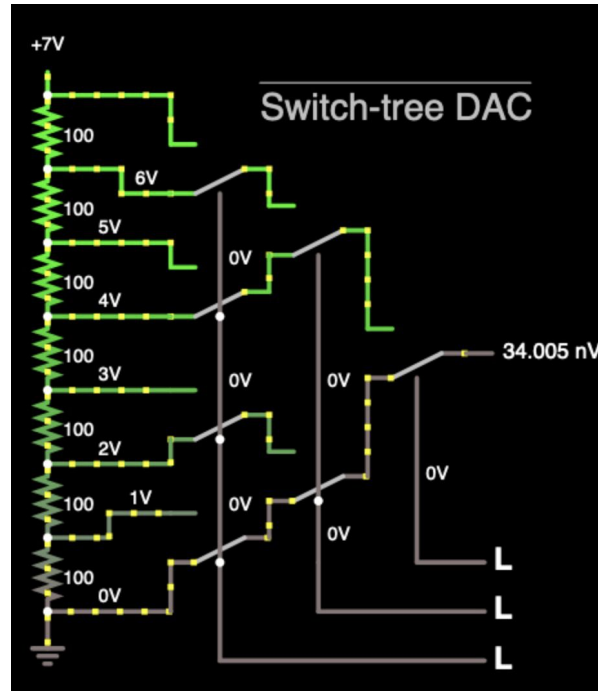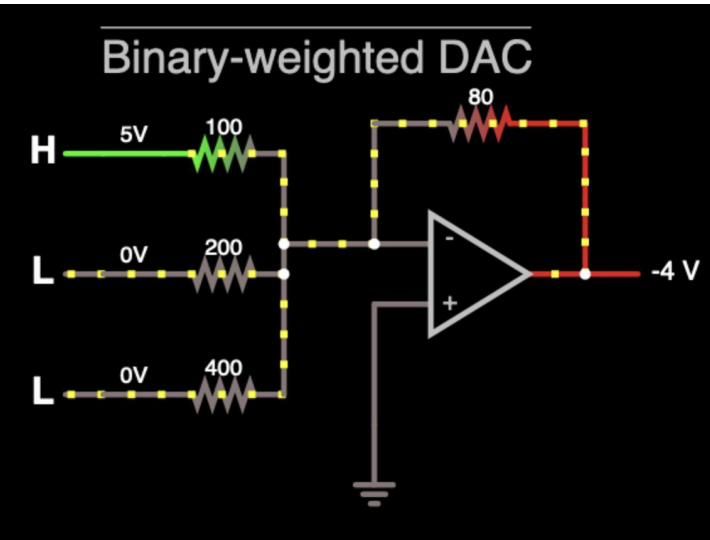
# Digital to Analog Converter (DAC)

Converts input digital value (i.e. an integer) into an output voltage.



# Arduino Digital Pins

- Digital reads are much faster than analog reads
  - processor just needs to know whether the signal is ON or OFF.
- Arduino digitalRead
  - ~ 50 (16 MHz) clock cycles,  $3.125\mu\text{ s}$ ,
    - potentially up to 320 kHz.
  - Accessing the digital ports directly can read/write to the digital pins even faster
    - as little as 2 clock cycles  $\rightarrow$  8 MHz



# Higher digitization rate



**InfiniiVision Real-Time  
Oscilloscopes**

50 MHz to 6 GHz



**Infinium Real-Time  
Oscilloscopes**

500 MHz to 110 GHz



**DCA Equivalent-Time  
(Sampling) Oscilloscopes**

10 GHz to >100 GHz



**Handheld, Modular, and USB  
Oscilloscopes**

100 MHz to 1 GHz

Or... design it yourself...

# Questions?

